


# M3 – ALU Design

# Module Outline

- Integer Arithmetic
  - Adder, Subtractor, Multiplier, Divider
- Arithmetic and Logical Unit Design
  - ALU Design in SystemC
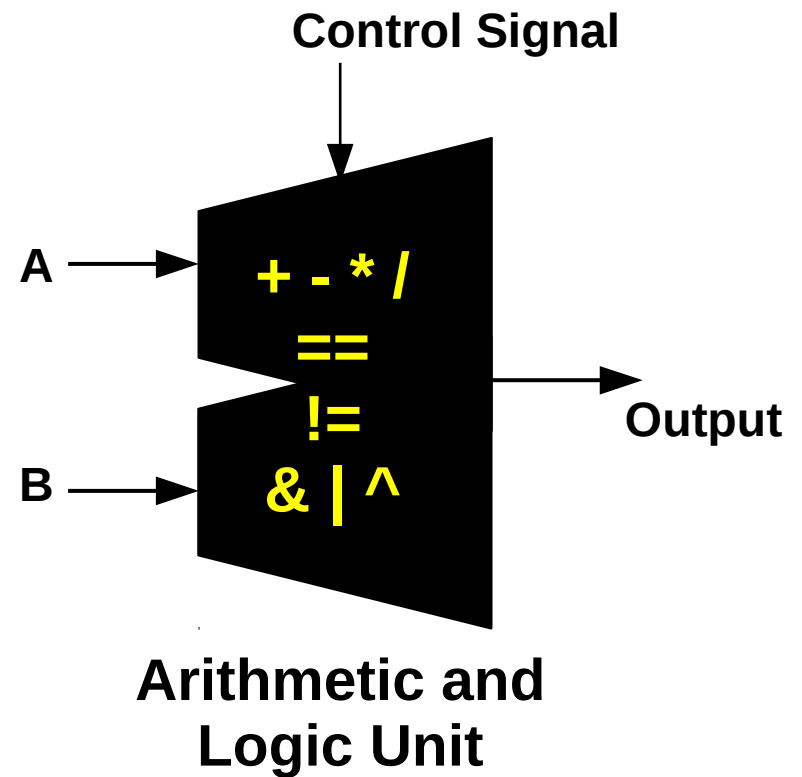
# Arithmetic Logic Unit

- Arithmetic operations
- Logic operations
- Comparison (Equal)



# ALU

- Start with the simplest operations.

# ALU

- Start with the simplest operations.
  - AND, OR
  - Control signal

# ALU

- Start with the simplest operations.
  - AND, OR
  - Control signal
- Incrementally add functionality and control

# ALU


- Start with the simplest operations.
  - AND, OR
  - Control signal
- Incrementally add functionality and control
- Start with a 1-bit ALU

# ALU

- Start with the simplest operations.
  - AND, OR
  - Control signal
- Incrementally add functionality and control
- Start with a 1-bit ALU
- Modify design for a n-bit ALU




# Basic ALU Design

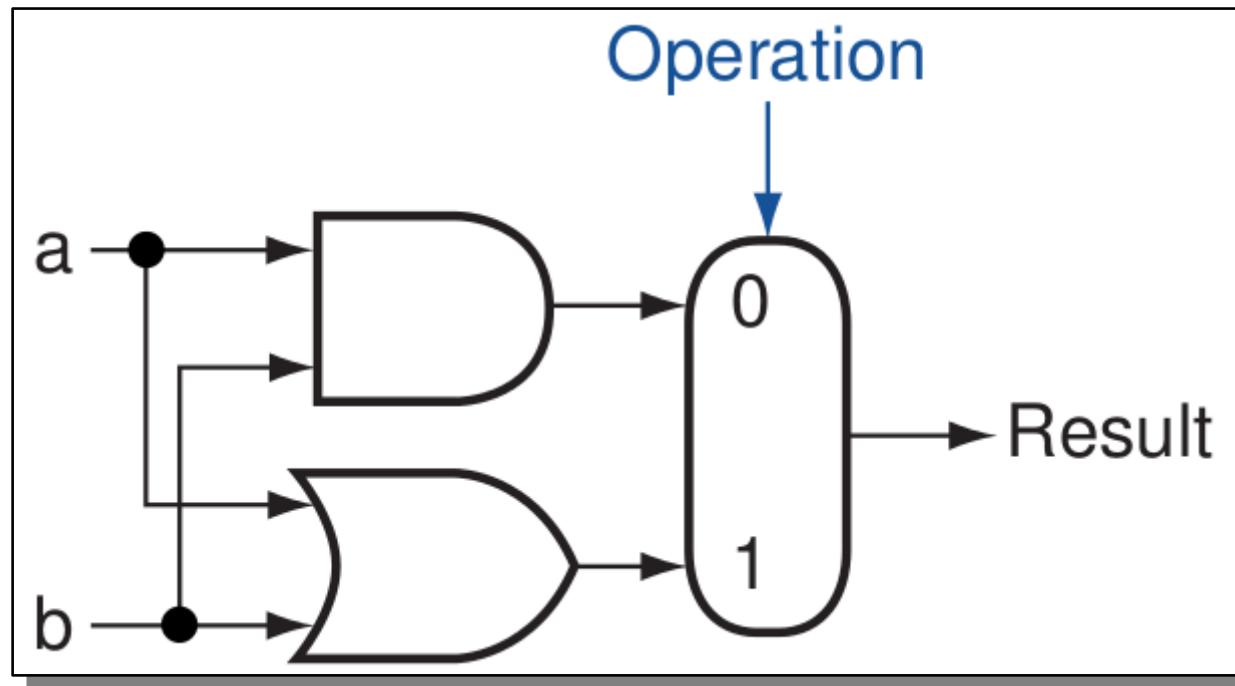


**AND, OR**

# Basic ALU Design

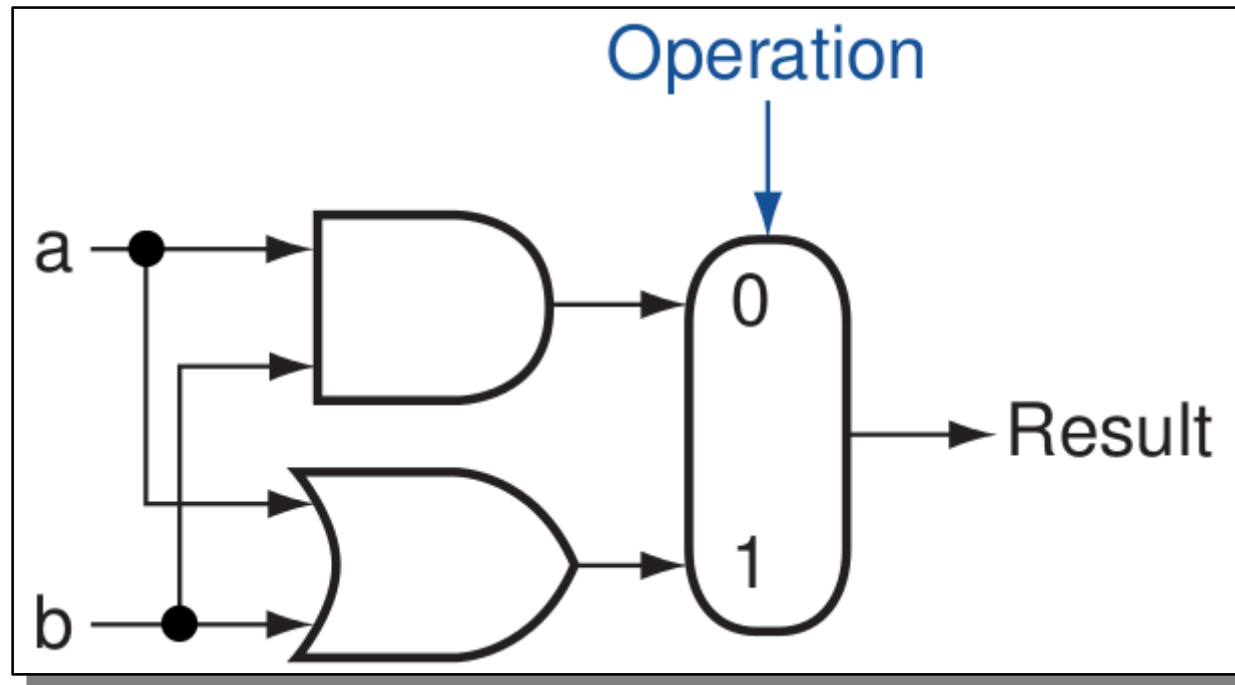


Include a Full Adder

# Basic ALU Design

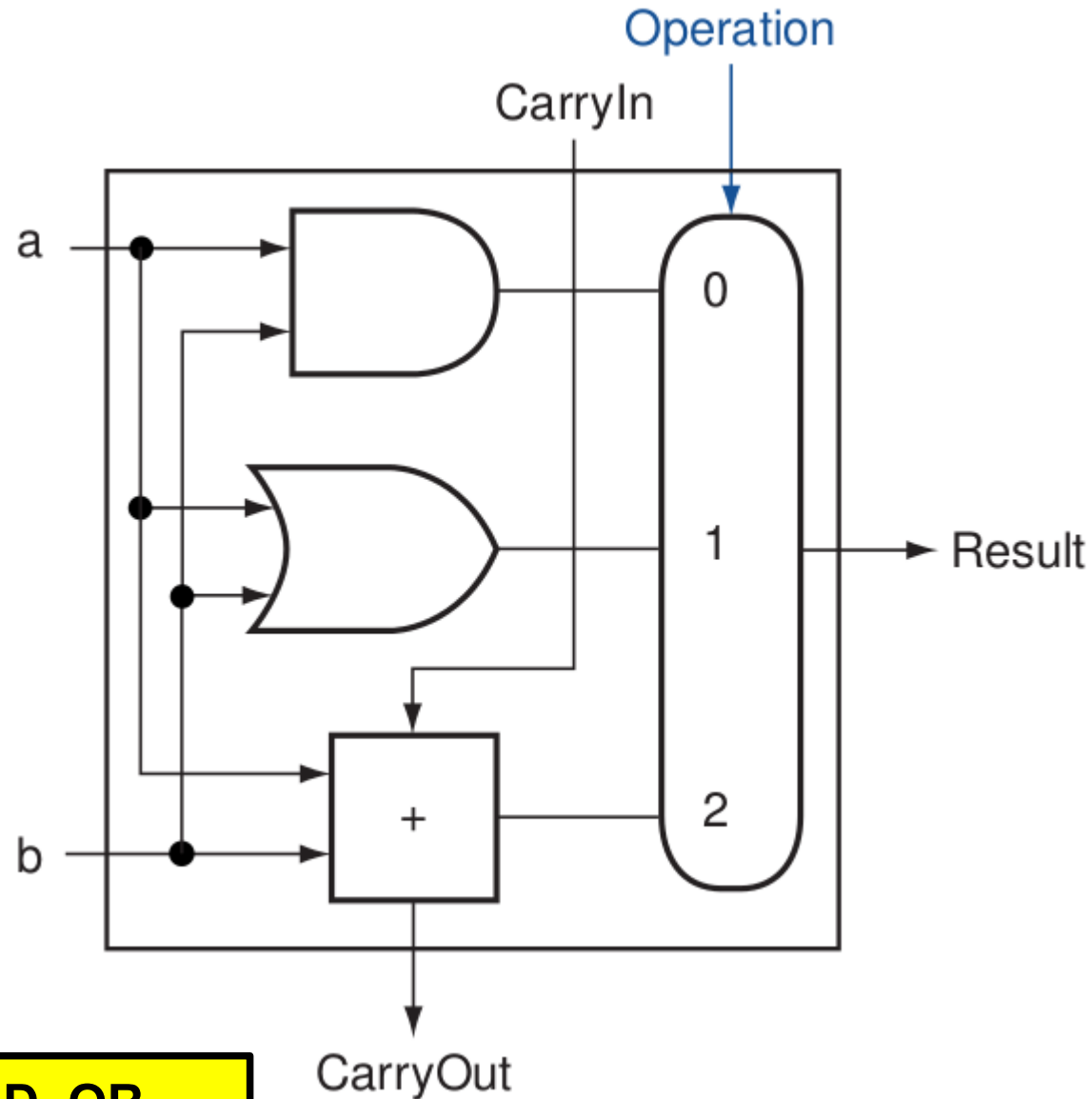

**ADDER, AND, OR**


# Basic ALU Design

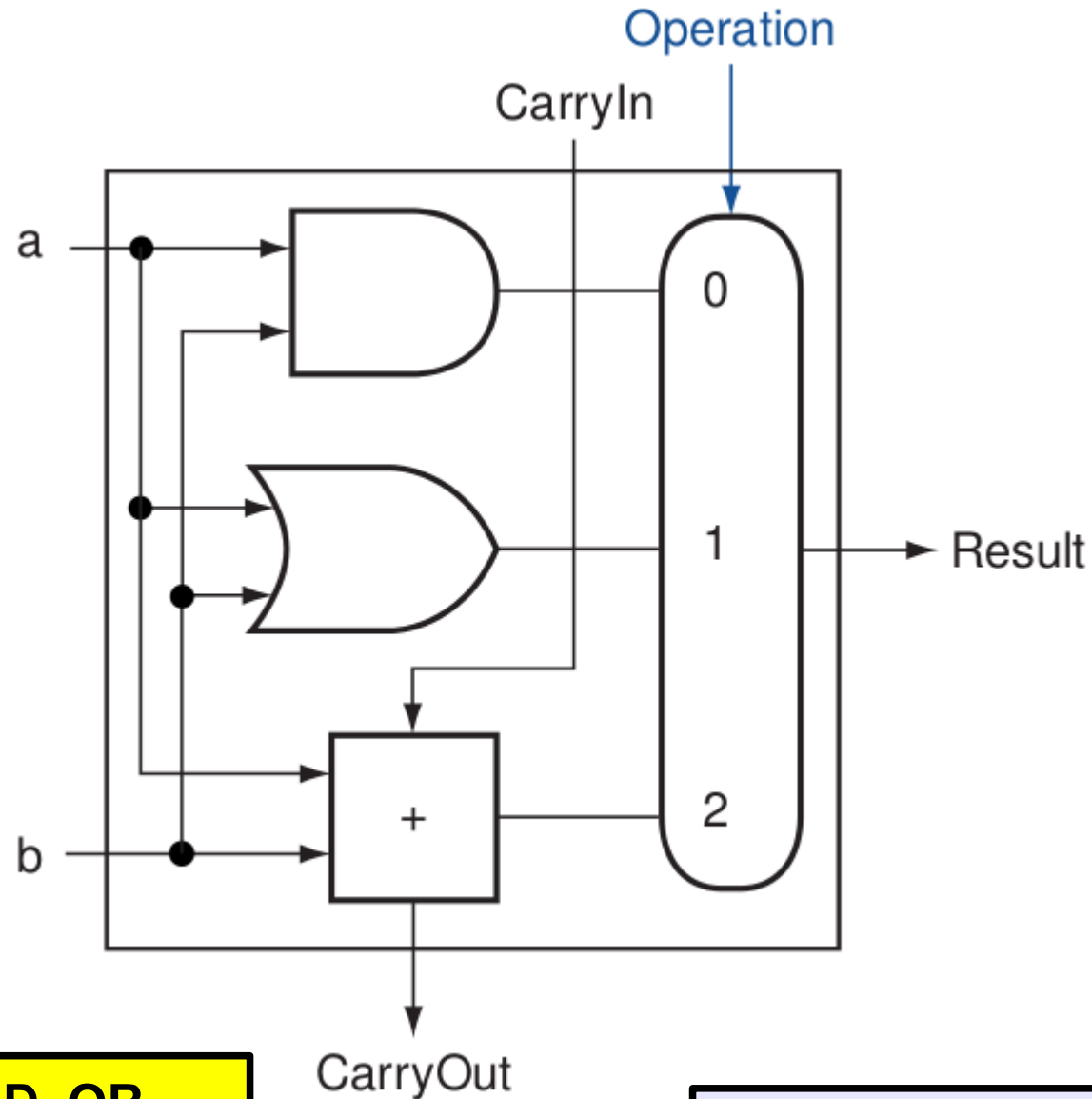



**ADDER, AND, OR**

**Subtraction?**



# Adder/Subtractor

 

# Adder/Subtractor

  


# Adder/Subtractor

  

$$-b = \bar{b} + 1$$

**$A \pm B$ , AND, OR**

# ALU Design

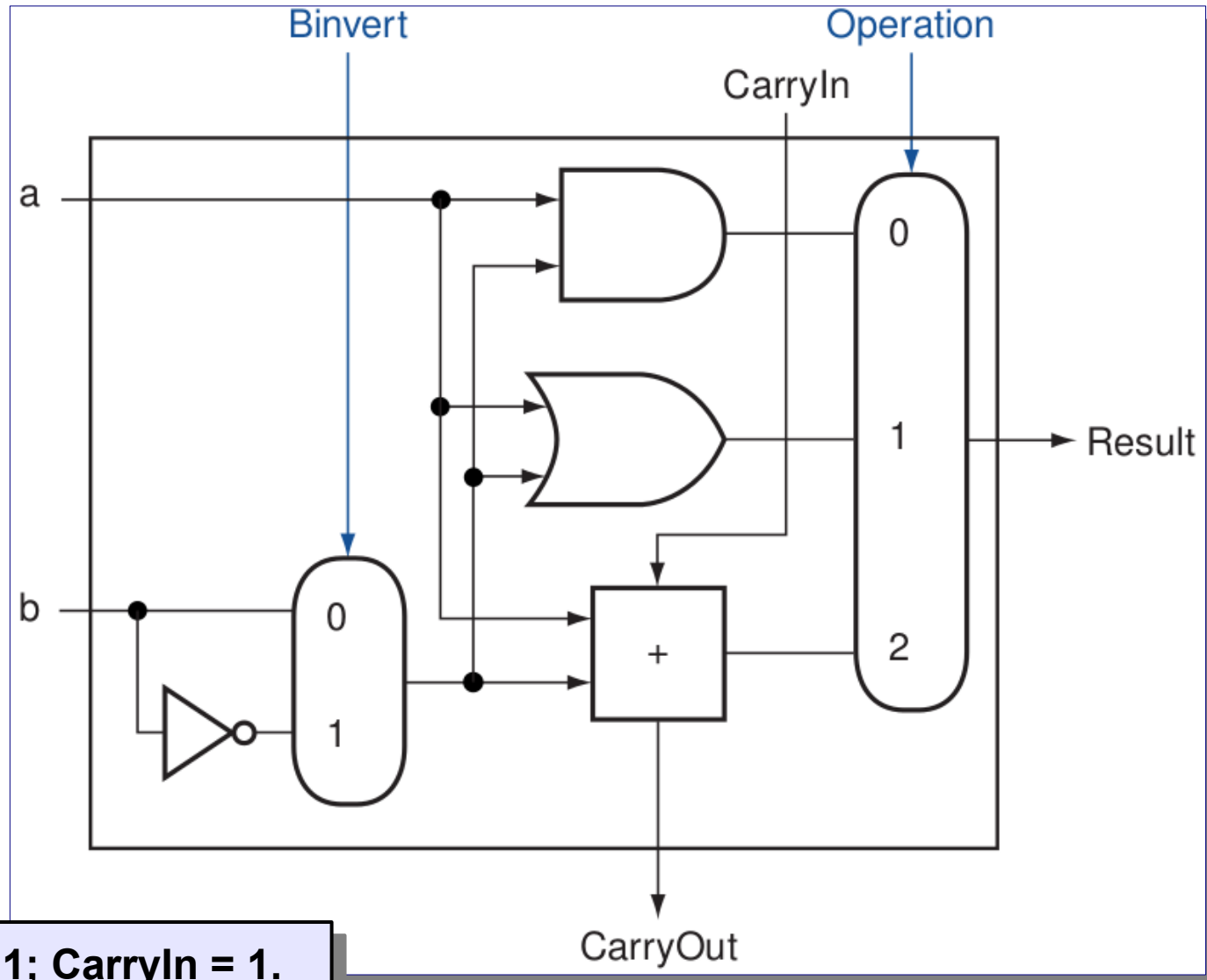


**A-B: Binvert = 1; CarryIn = 1.  
A+B: Binvert = 0; CarryIn = 0.**



**A±B, AND, OR**

# ALU Design

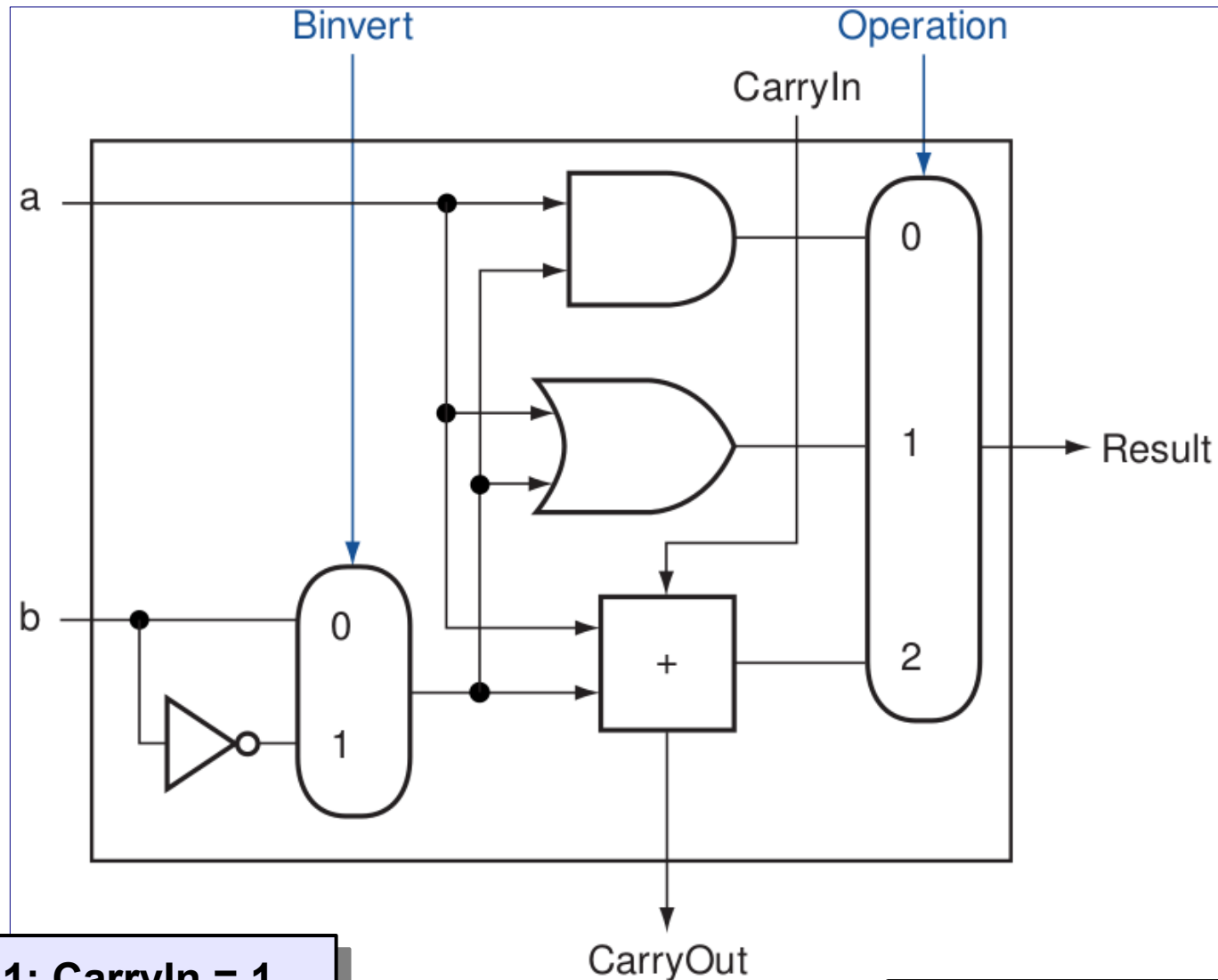

**A-B: Binvert = 1; CarryIn = 1.  
A+B: Binvert = 0; CarryIn = 0.**


**NAND, NOR?**

# NAND, NOR, NOT

$$\begin{aligned} A \text{ NAND } B &= \overline{(A \text{ AND } B)} \\ &= \overline{A} \text{ OR } \overline{B} \end{aligned}$$


$$\begin{aligned} A \text{ NOR } B &= \overline{(A \text{ OR } B)} \\ &= \overline{A} \text{ AND } \overline{B} \end{aligned}$$

# ALU Design

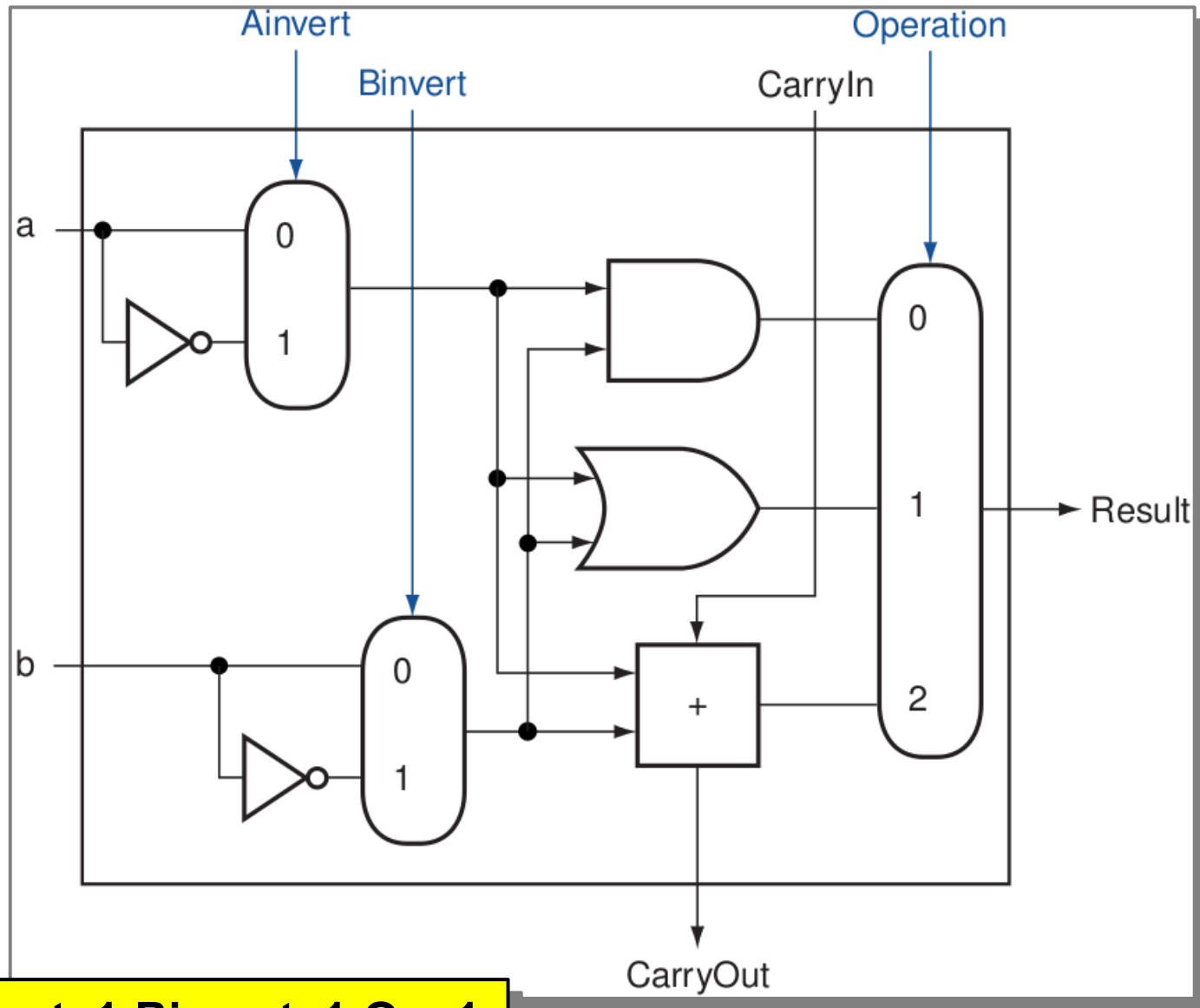


**a NAND b: Ainvert=1;Binvert=1;Op=1**

# ALU Design

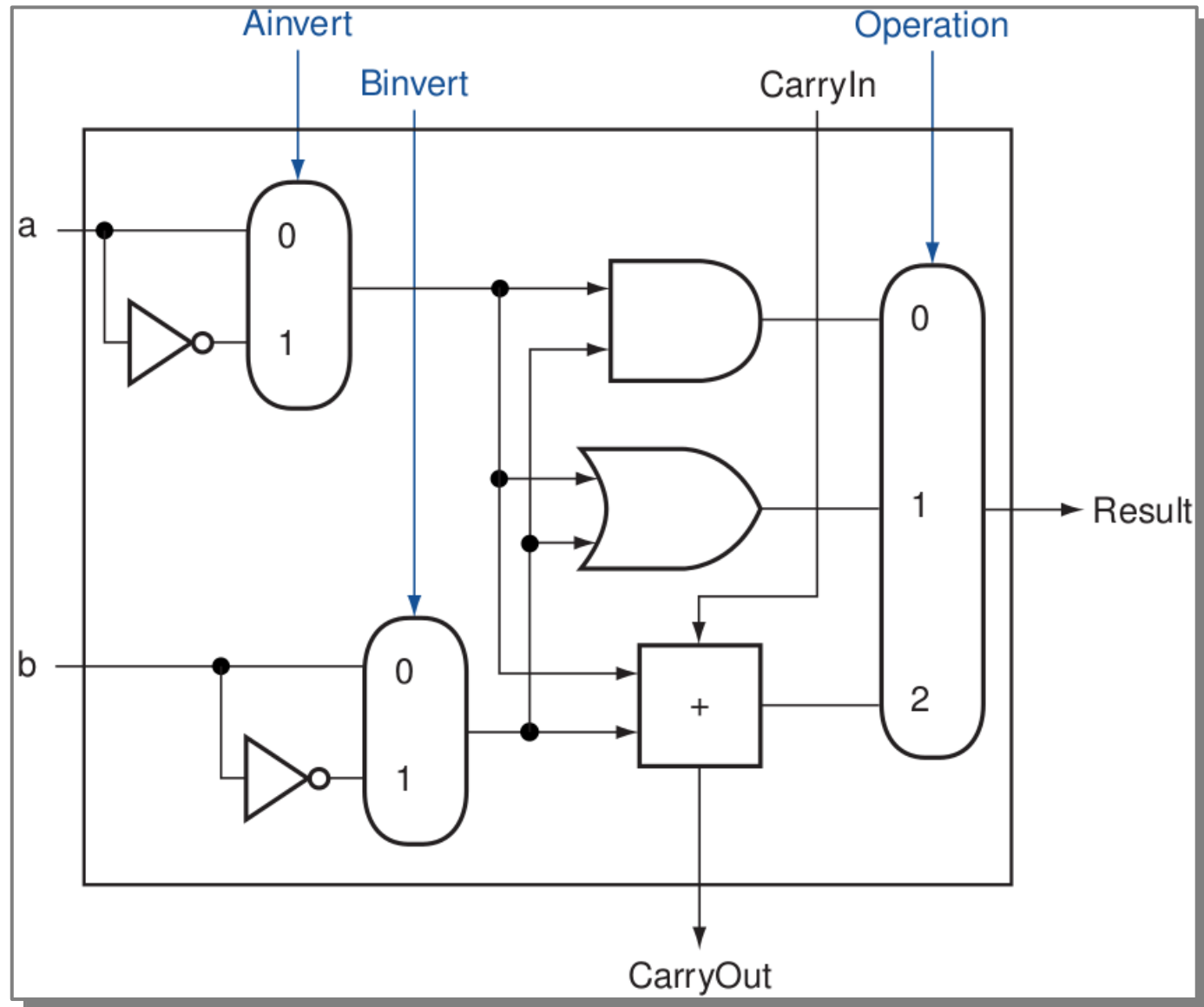

**$A \pm B$ , AND, OR, NOR, NAND**

# ALU Design

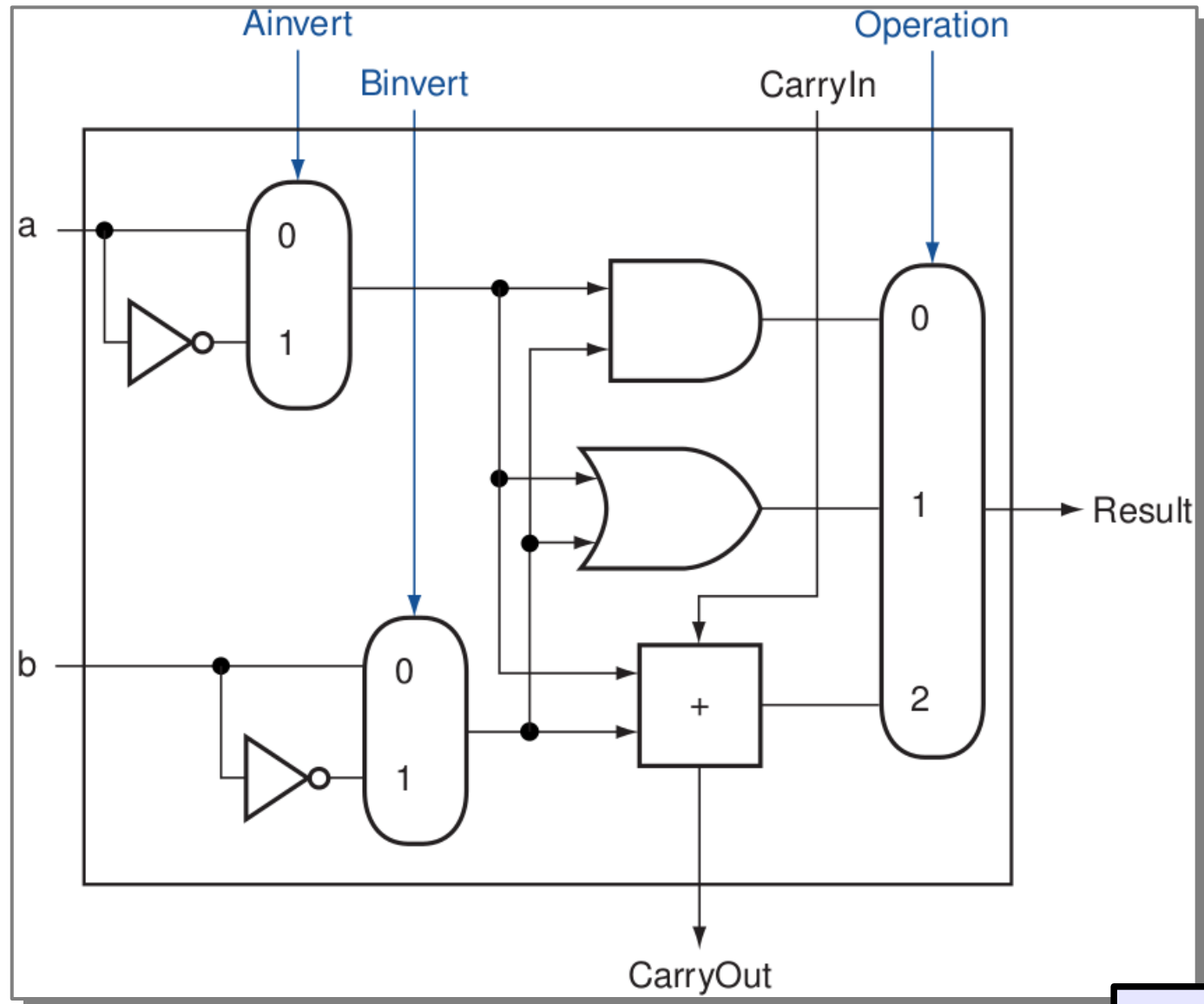


SLT?

# Set Less Than


- Set a status bit if  $(a < b)$
- If  $(a < b)$ ;  $(a - b)$  is -ve
- Calculate  $(a - b)$ . Observe sign bit of the result

# ALU Design

 

**slt(a,b): Binvert=1; CarryIn=1; Operation=3;**


# ALU Design

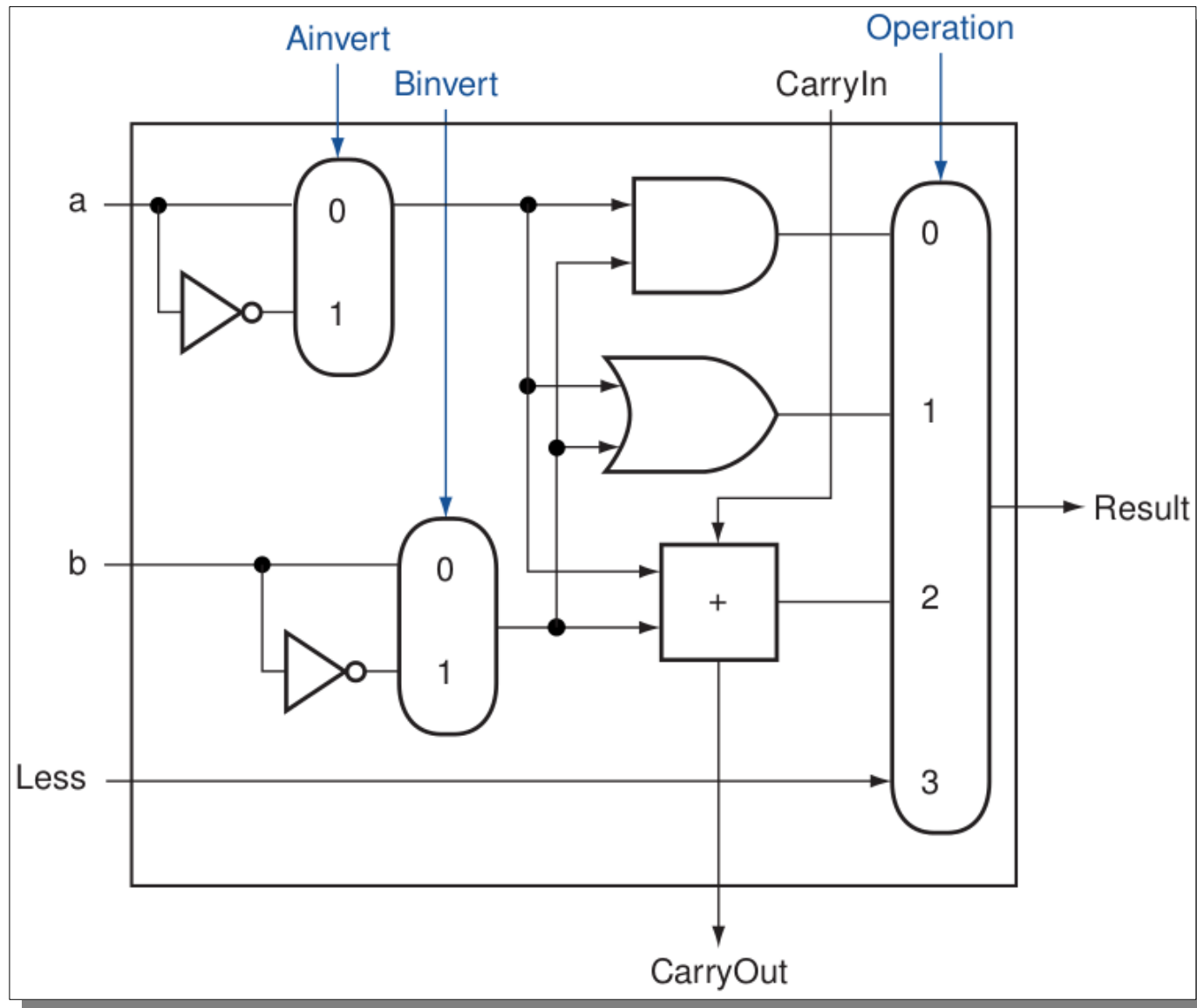

**$A \pm B$ , AND, OR, NOR, NAND, SLT**




# ALU Design

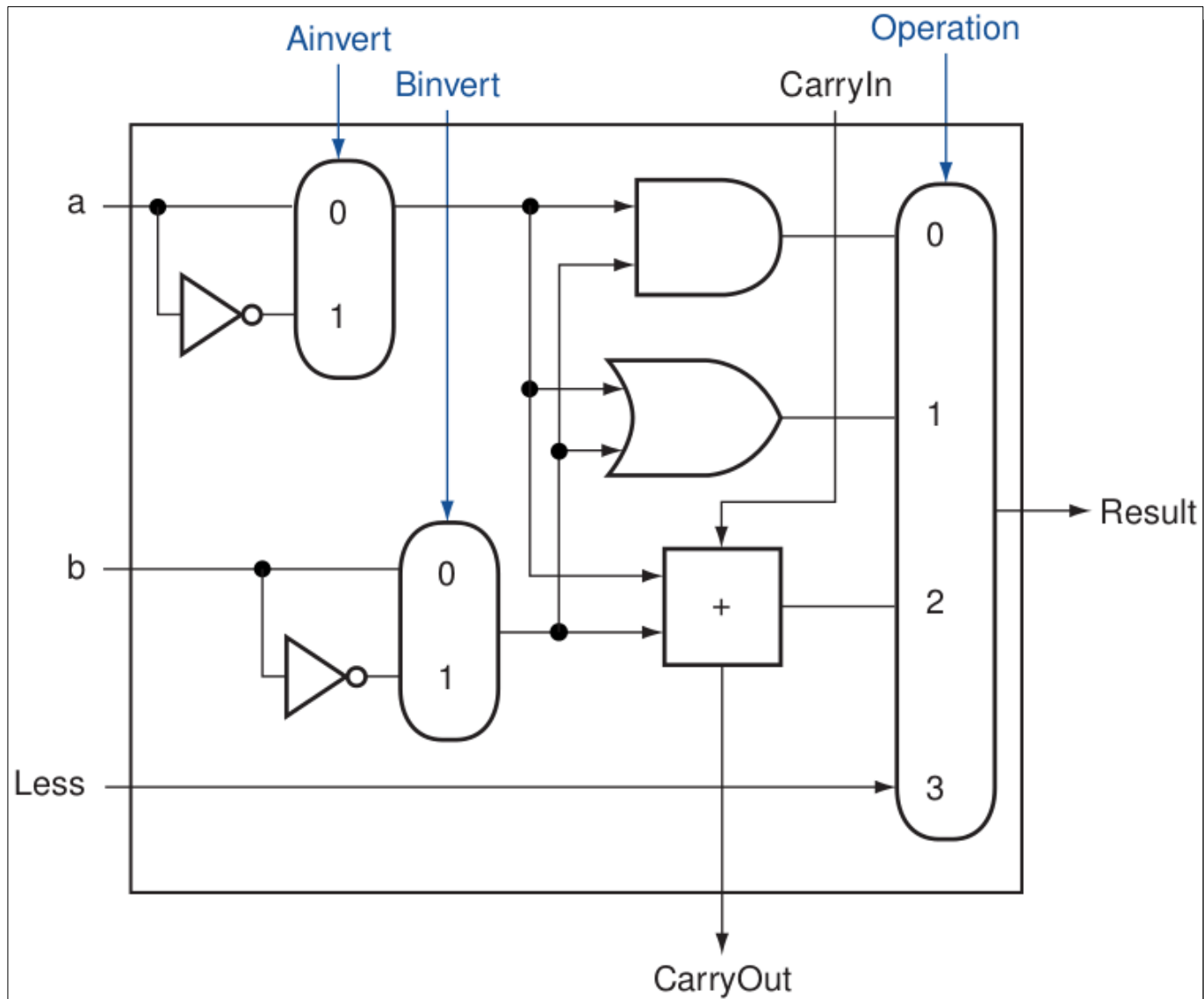

**$A \pm B$ , AND, OR, NOR, NAND, SLT**




**Overflow?**

# ALU Design

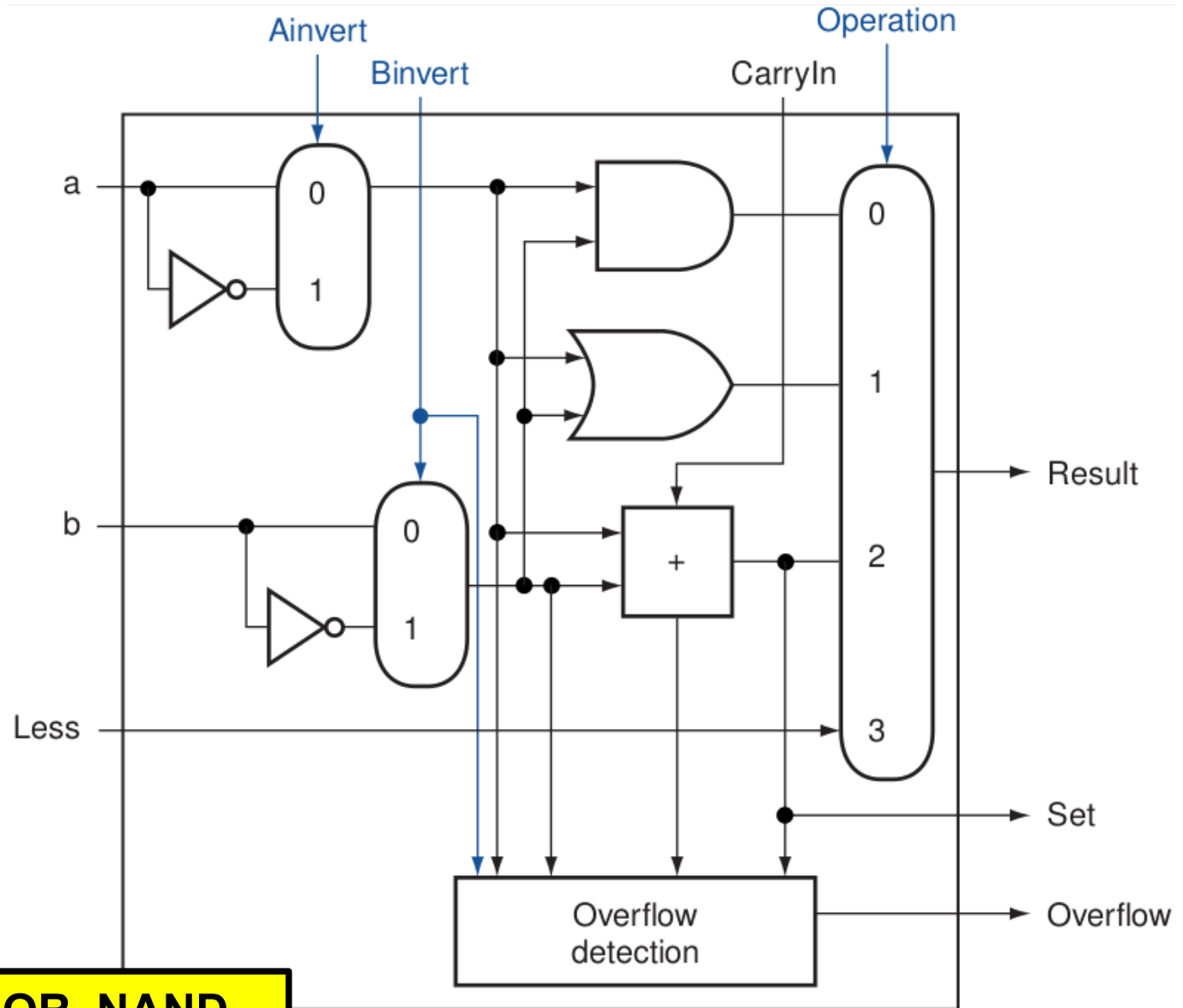


**$A \pm B$ , AND, OR, NOR, NAND,  
SLT, Overflow detection**

# ALU Design

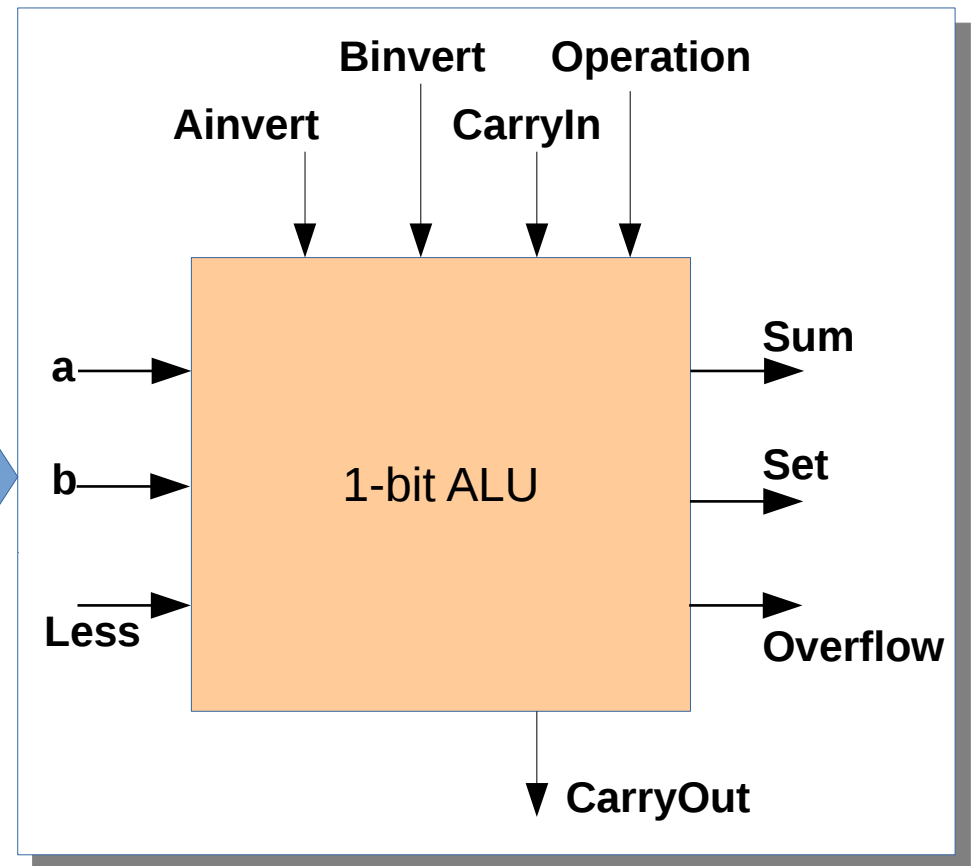 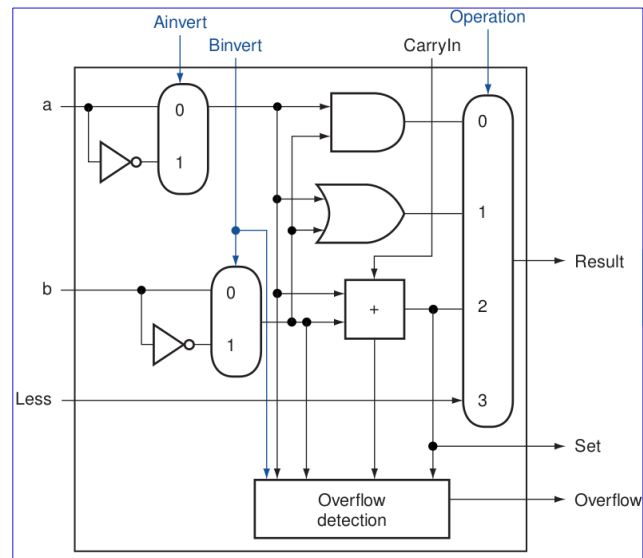


# 32-bit ALU

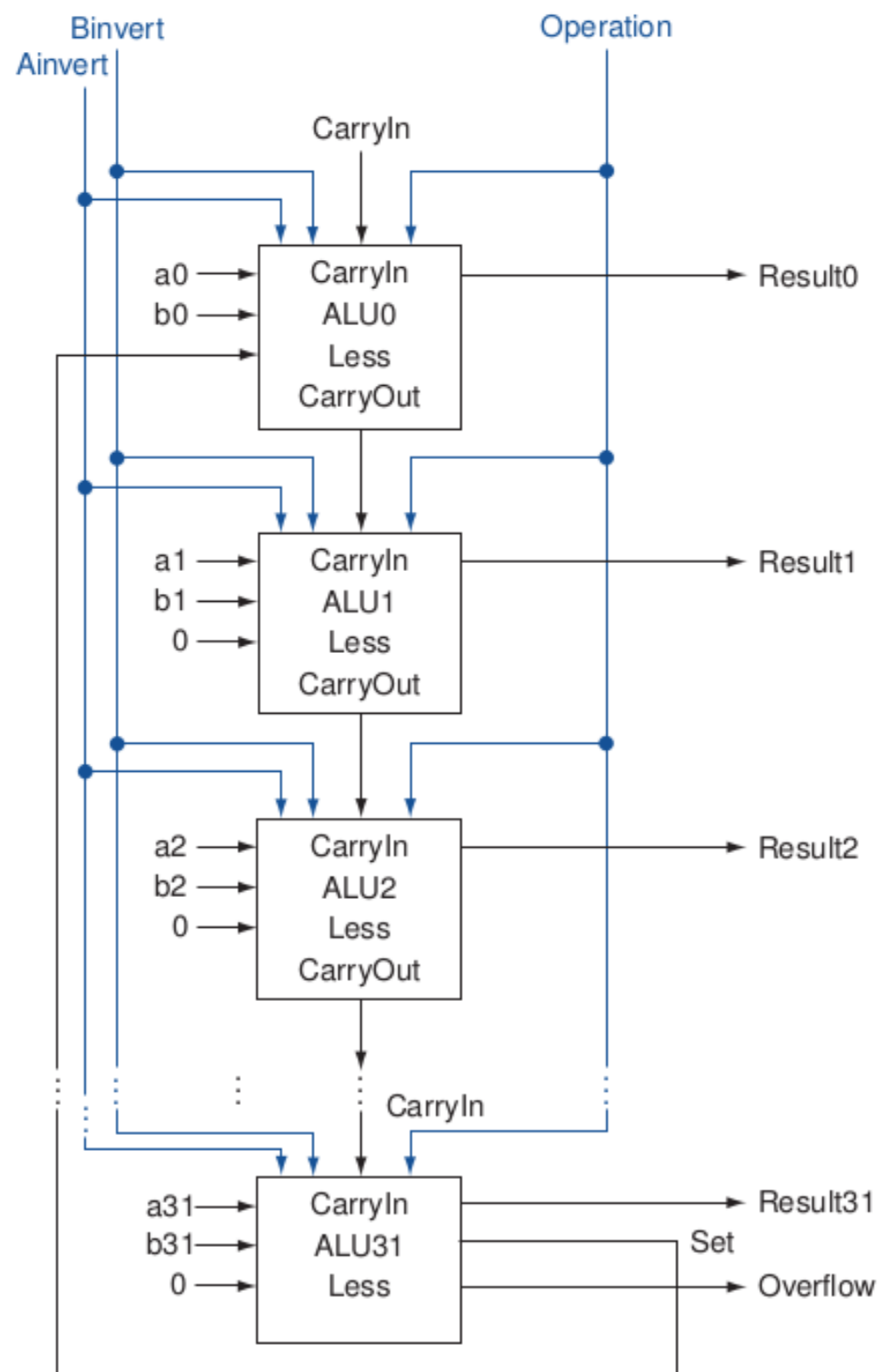


Zero detection?

# 32-bit ALU

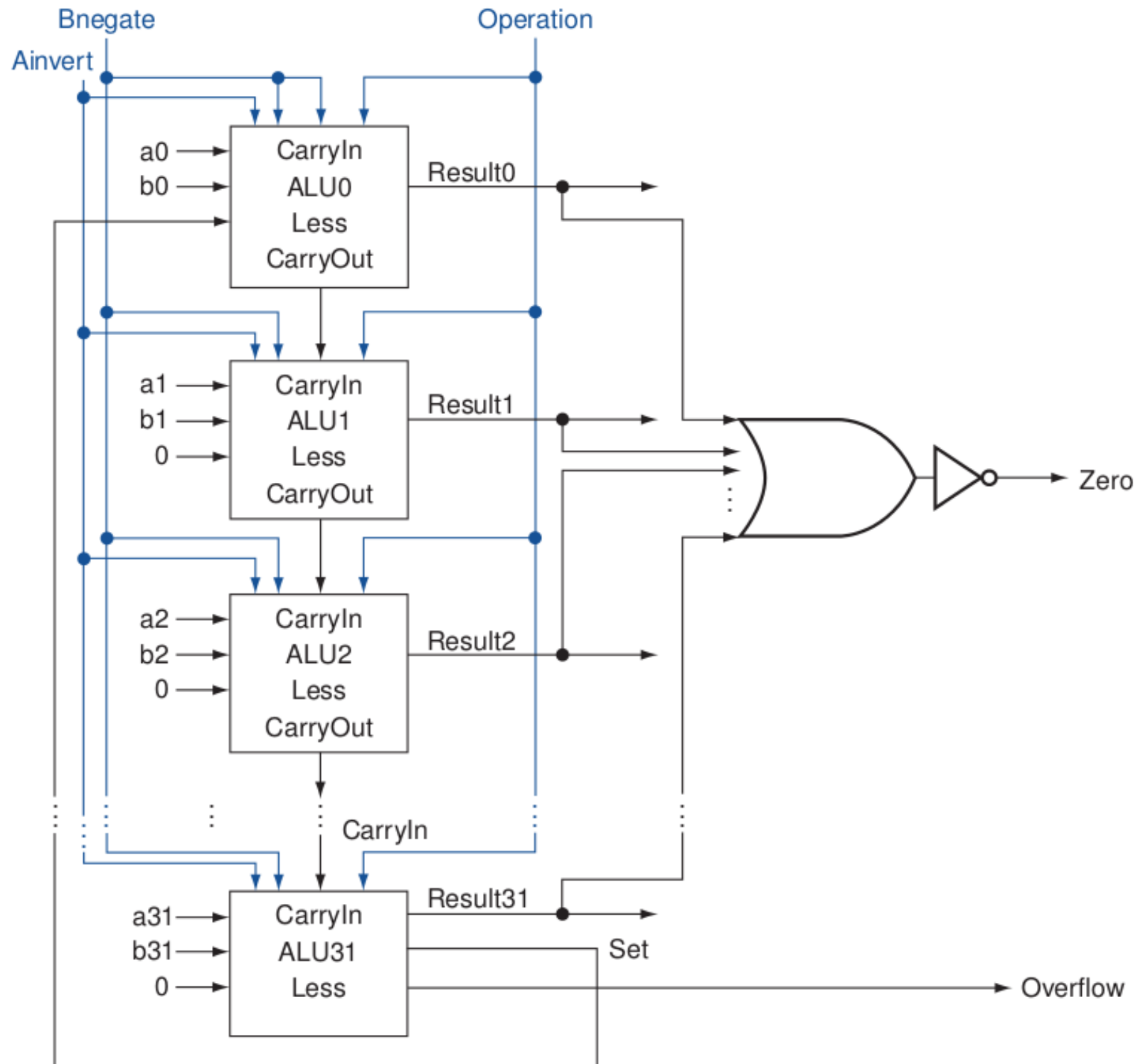


# ALU

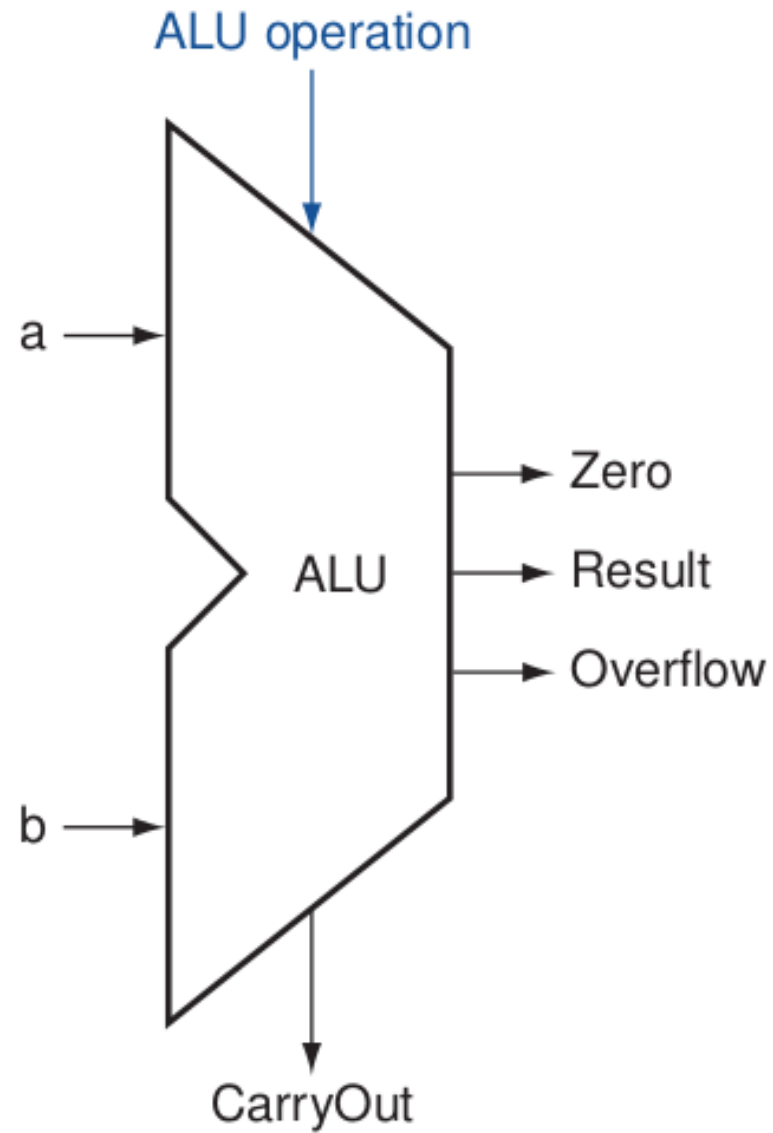


# ALU – Control Signals

	Ainvert	Binvert	CarryIn	Operation
AND				
OR				
ADD				
SUB				
NAND				
NOR				
SLT				

 

# ALU – Control Signals


	Ainvert	Binvert	CarryIn	Operation
<b>AND</b>	0	0	0	00
<b>OR</b>				
<b>ADD</b>				
<b>SUB</b>				
<b>NAND</b>				
<b>NOR</b>				
<b>SLT</b>				

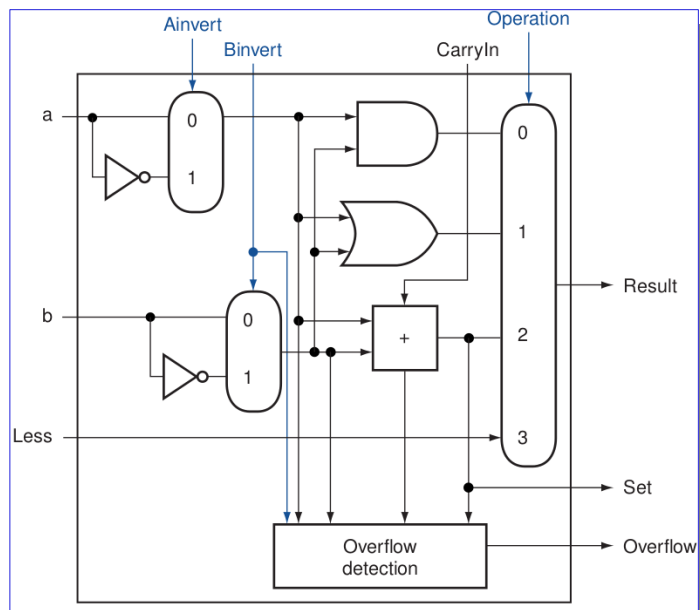




# ALU – Control Signals

	Ainvert	Binvert	CarryIn	Operation
<b>AND</b>	0	0	0	00
<b>OR</b>	0	0	0	01
<b>ADD</b>				
<b>SUB</b>				
<b>NAND</b>				
<b>NOR</b>				
<b>SLT</b>				

 


# ALU – Control Signals

	Ainvert	Binvert	CarryIn	Operation
<b>AND</b>	0	0	0	00
<b>OR</b>	0	0	0	01
<b>ADD</b>	0	0	0	10
<b>SUB</b>	0	1	1	10
<b>NAND</b>				
<b>NOR</b>				
<b>SLT</b>				

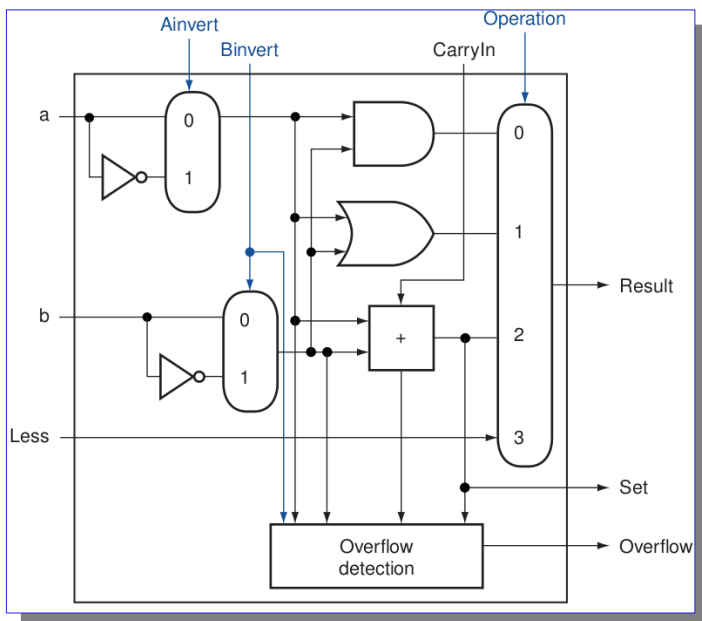


# ALU – Control Signals

	Ainvert	Binvert	CarryIn	Operation
<b>AND</b>	0	0	0	00
<b>OR</b>	0	0	0	01
<b>ADD</b>	0	0	0	10
<b>SUB</b>	0	1	1	10
<b>NAND</b>	1	1	0	01
<b>NOR</b>	1	1	0	00
<b>SLT</b>				

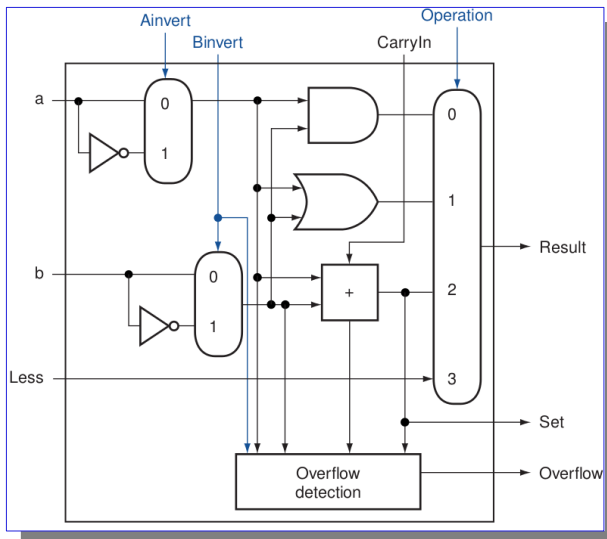


# ALU – Control Signals

	Ainvert	Binvert	CarryIn	Operation
<b>AND</b>	0	0	0	00
<b>OR</b>	0	0	0	01
<b>ADD</b>	0	0	0	10
<b>SUB</b>	0	1	1	10
<b>NAND</b>	1	1	0	01
<b>NOR</b>	1	1	0	00
<b>SLT</b>	0	1	1	11

 

# ALU – Control Signals

	Ainvert	Binvert	CarryIn	Operation
<b>AND</b>	0	0	0	00
<b>OR</b>	0	0	0	01
<b>ADD</b>	0	0	0	10
<b>SUB</b>	0	1	1	10
<b>NAND</b>	1	1	0	01
<b>NOR</b>	1	1	0	00
<b>SLT</b>	0	1	1	11

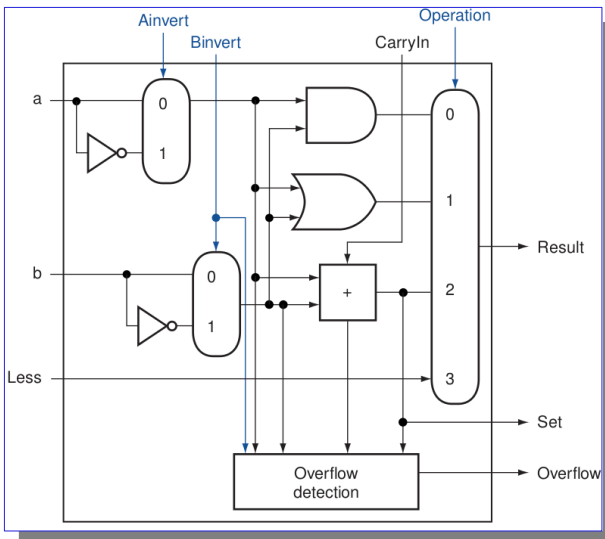


Ignore the effect of CarryIn during NAND and NOR execution. **Binvert == CarryIn.**


# ALU – Control Signals

	$\overline{A}BOp$
AND	0000
OR	0001
ADD	0010
SUB	0110
NAND	1101
NOR	1100
SLT	0111

# ALU Control

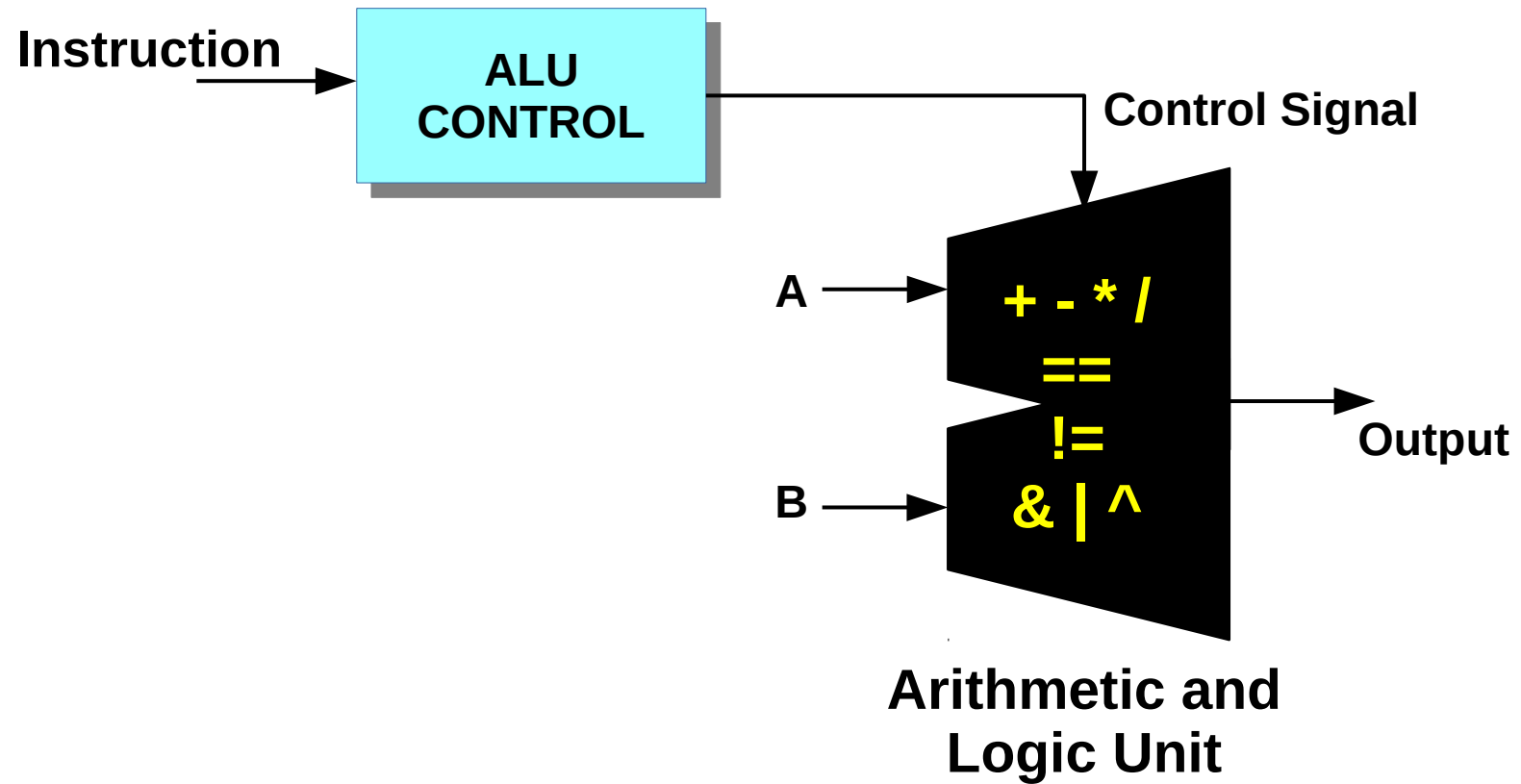

# ALU Control – AND Instruction

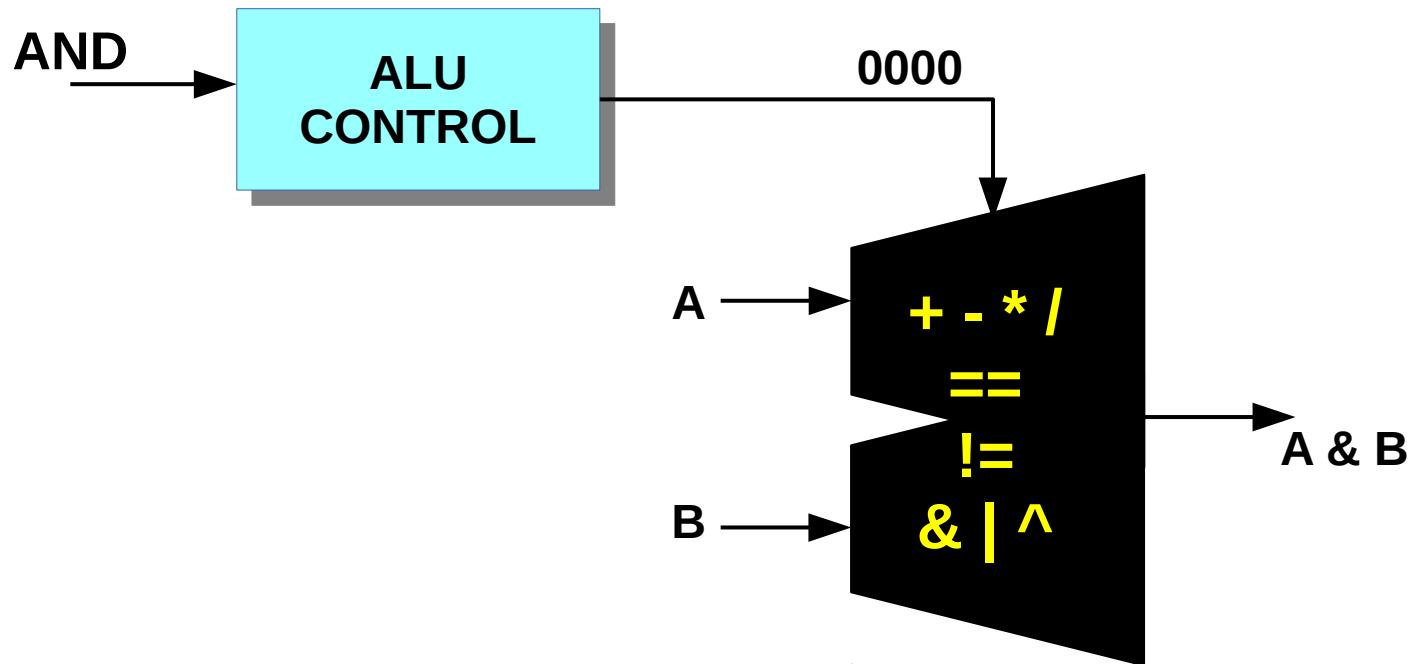



# Instructions using the ALU

- Arithmetic and Logic Instructions
  - R-type and I-type
- Memory transfer instructions
  - Effective address calculation
  - I-type
- Branch instructions (BEQ)
  - For Zero detection
  - I-type

# ALU – Control Signals


	$\overline{A}BOp$
AND	0000
OR	0001
ADD	0010
SUB	0110
NAND	1101
NOR	1100
SLT	0111

Which control signals for  
LW, SW, BEQ?


# ALU – Control Signals

Input to ALU CU	Output Control Signals $\overline{A}BOp$
AND	0000
OR	0001
ADD, LW, SW	0010
SUB, BEQ	0110
NAND	1101
NOR	1100
SLT	0111


# ALU Control – AND Instruction

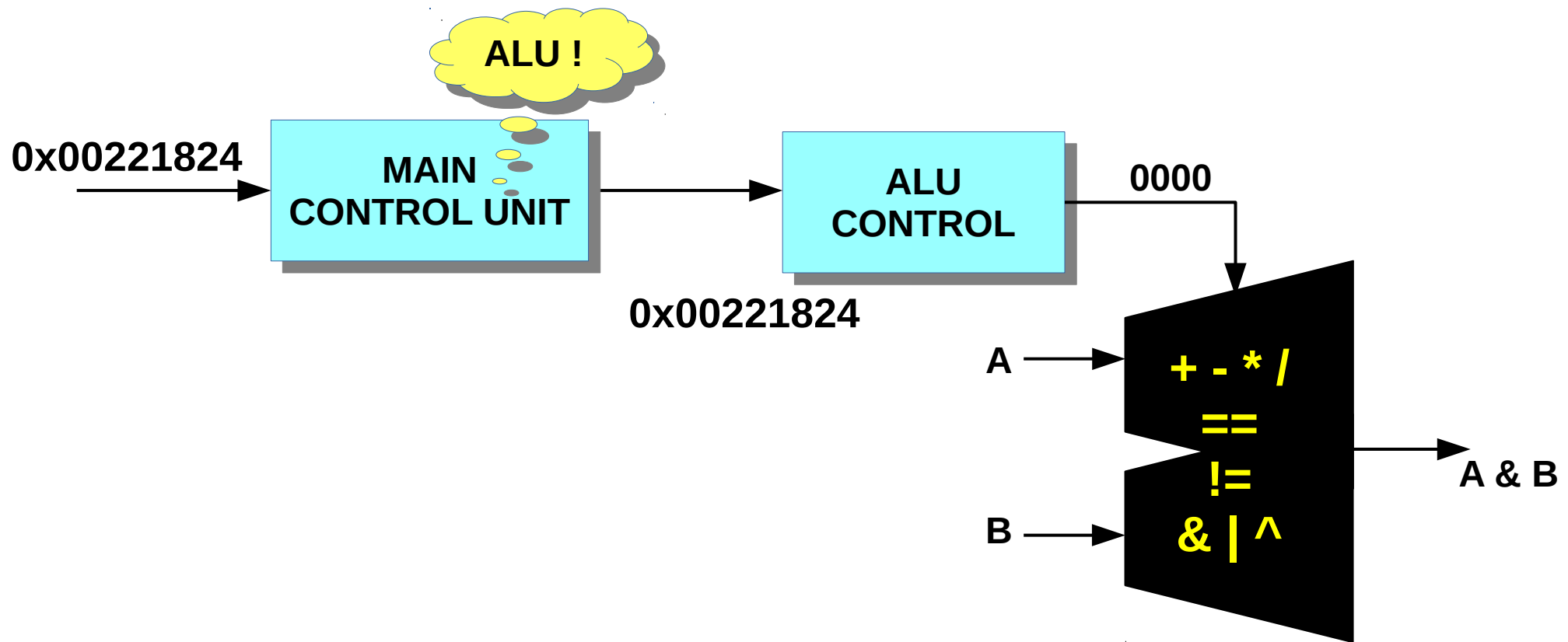


# ALU Control – AND Instruction

 

# ALU Control – AND Instruction

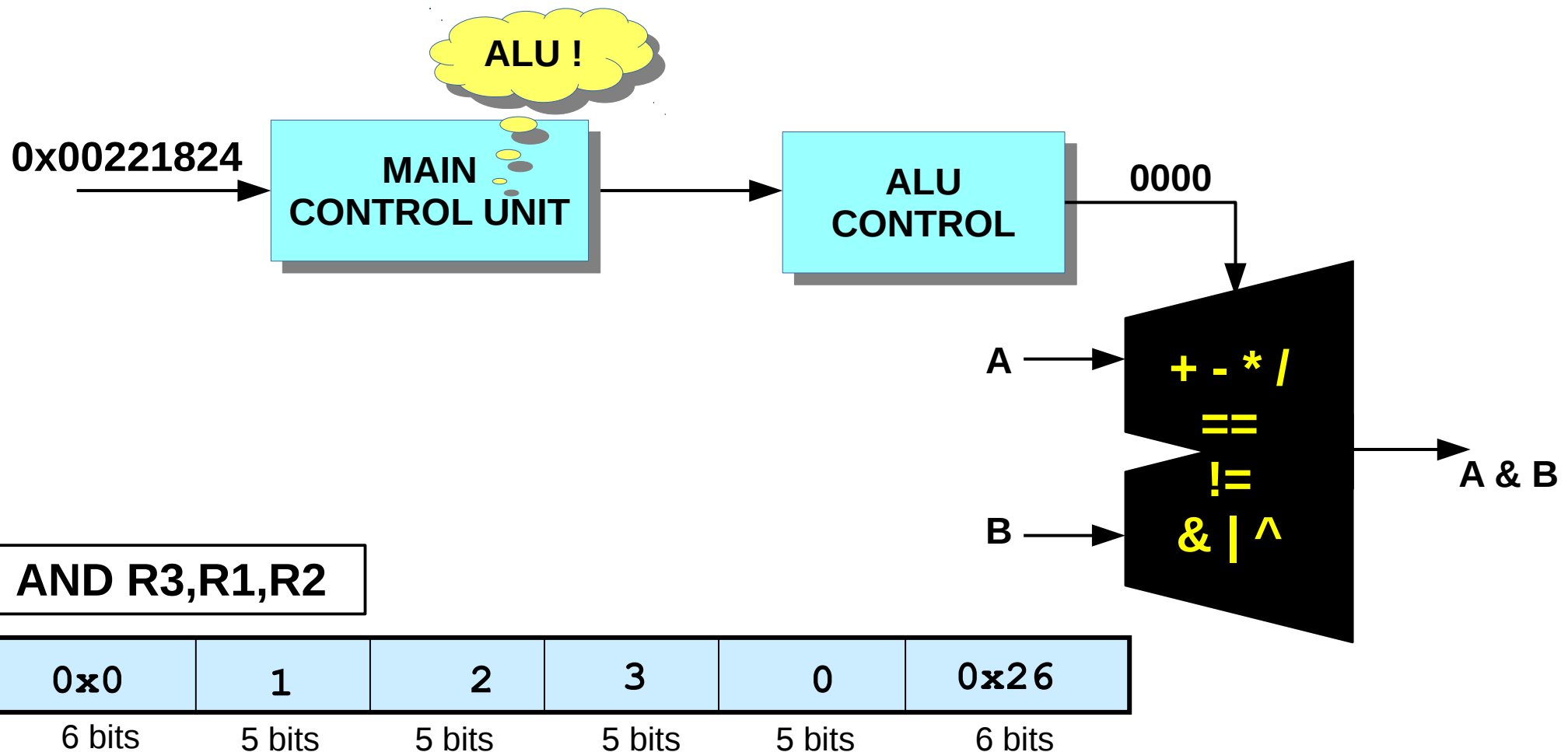

# ALU Control – AND (R-type)

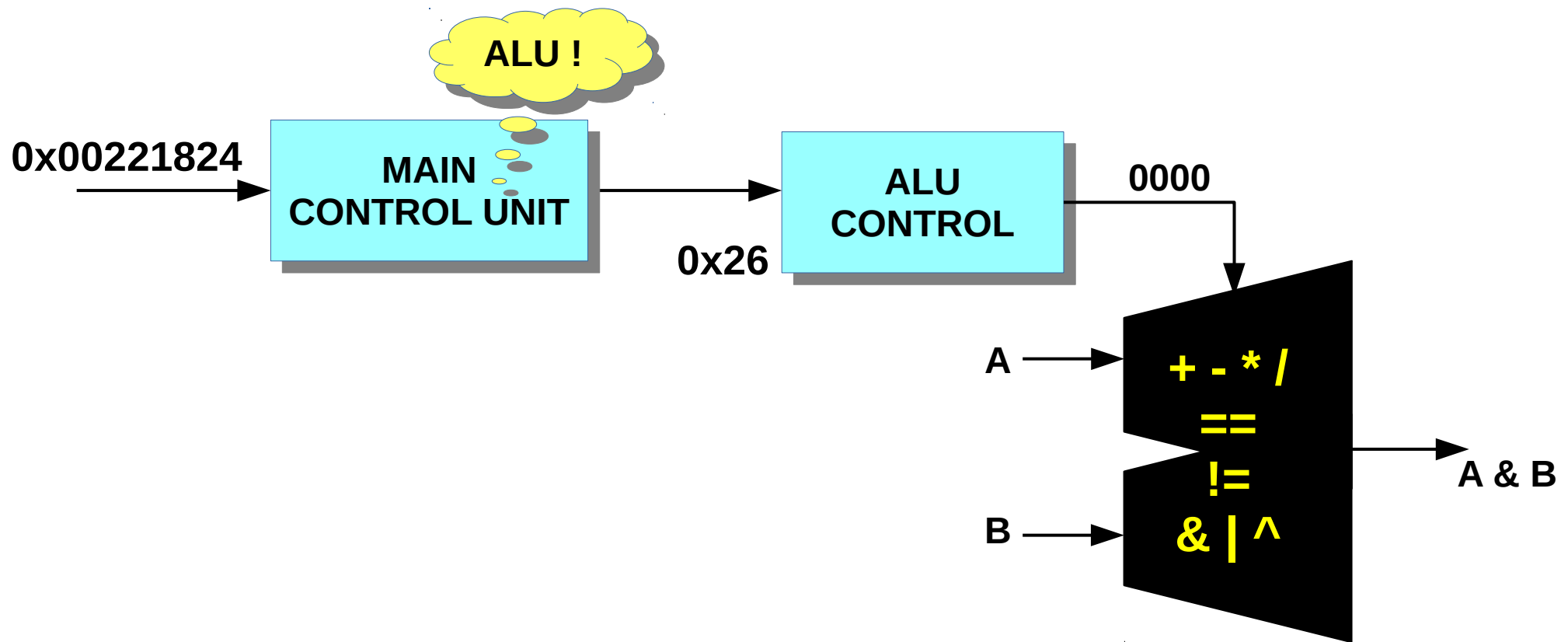

# Truth Table of the ALU CU

Instruction	ALU action	Type	Funct field	Control Signal
LW				
SW				
BEQ				
ALU instruction				
ALU Immediate				



# Truth Table of the ALU CU

Instruction	ALU action	Type	Funct field	Control Signal
LW				
SW				
BEQ				
ALU instruction				
ALU Immediate				

**Main Control Unit  
Identifies the instruction**

**Inputs to the ALU CU**

**Output of ALU CU**

# Truth Table of the ALU CU

Instruction	ALU action	Type	Funct field	Control Signal
LW	add	I-type	Invalid	0010
SW				
BEQ				
ALU instruction				
ALU Immediate				

**Main Control Unit  
Identifies the instruction**

**Inputs to the ALU CU**

**Output of ALU CU**

# Truth Table of the ALU CU

Instruction	ALU action	Type	Funct field	Control Signal
LW	add	I-type	Invalid	0010
SW	add	I-type	Invalid	0010
BEQ				
ALU instruction				
ALU Immediate				

**Main Control Unit  
Identifies the instruction**

**Inputs to the ALU CU**

**Output of ALU CU**

# Truth Table of the ALU CU

Instruction	ALU action	Type	Funct field	Control Signal
LW	add	I-type	Invalid	0010
SW	add	I-type	Invalid	0010
BEQ	sub	I-type	Invalid	0110
ALU instruction				
ALU Immediate				

**Main Control Unit  
Identifies the instruction**

**Inputs to the ALU CU**

**Output of ALU CU**

# Truth Table of the ALU CU

Instruction	ALU action	Type	Funct field	Control Signal
LW	add	I-type	Invalid	0010
SW	add	I-type	Invalid	0010
BEQ	sub	I-type	Invalid	0110
ALU instruction	As in instruction	R-type	Unique per instruction	As per instruction
ALU Immediate				

**Main Control Unit  
Identifies the instruction**

**Inputs to the ALU CU**

**Output of ALU CU**

# Truth Table of the ALU CU

Instruction	ALU action	Type	Funct field	Control Signal
LW	add	I-type	Invalid	0010
SW	add	I-type	Invalid	0010
BEQ	sub	I-type	Invalid	0110
ALU instruction	As in instruction	R-type	Unique per instruction	As per instruction
ALU Immediate	As in instruction	I-type	Invalid	As in instruction

**Main Control Unit  
Identifies the instruction**

**Inputs to the ALU CU**

**Output of ALU CU**

# Truth Table of the ALU CU


Instruction opcode	ALUOp	Instruction operation	Func field	Desired ALU action	ALU control input
LW	00	load word	XXXXXX	add	0010
SW	00	store word	XXXXXX	add	0010
Branch equal	01	branch equal	XXXXXX	subtract	0110
R-type	10	add	100000	add	0010
R-type	10	subtract	100010	subtract	0110
R-type	10	AND	100100	AND	0000
R-type	10	OR	100101	OR	0001
R-type	10	set on less than	101010	set on less than	0111

# Truth Table of the ALU CU

ALUOp		Funct field						Operation
ALUOp1	ALUOp0	F5	F4	F3	F2	F1	F0	
0	0	X	X	X	X	X	X	0010
X	1	X	X	X	X	X	X	0110
1	X	X	X	0	0	0	0	0010
1	X	X	X	0	0	1	0	0110
1	X	X	X	0	1	0	0	0000
1	X	X	X	0	1	0	1	0001
1	X	X	X	1	0	1	0	0111



# ALU Control Unit

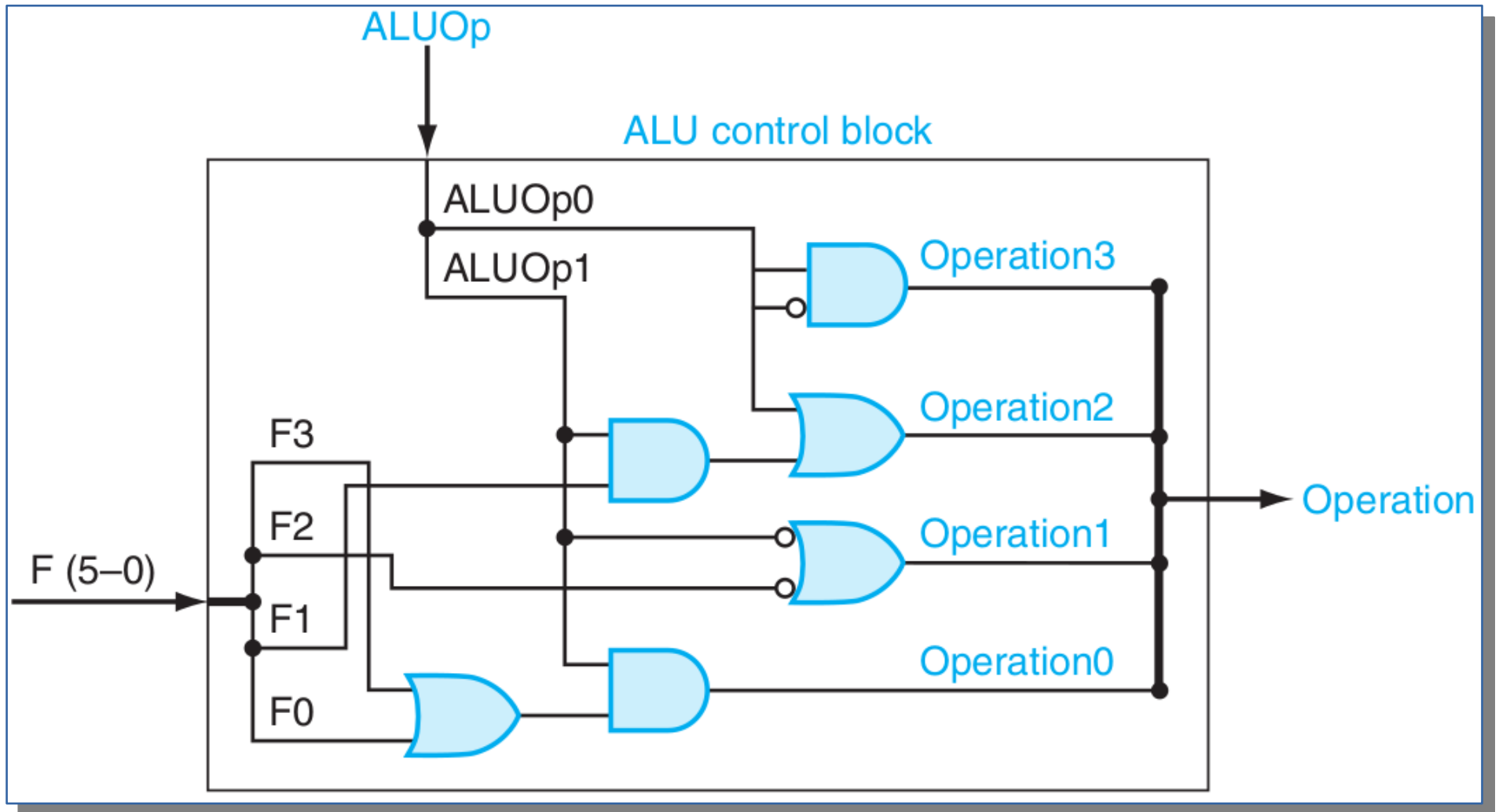


# Module Outline


- Integer Arithmetic
  - Adder, Subtractor, Multiplier, Divider
- Arithmetic and Logical Unit Design
  - ALU Design in SystemC

# Backup


# ALU Control – AND Instruction

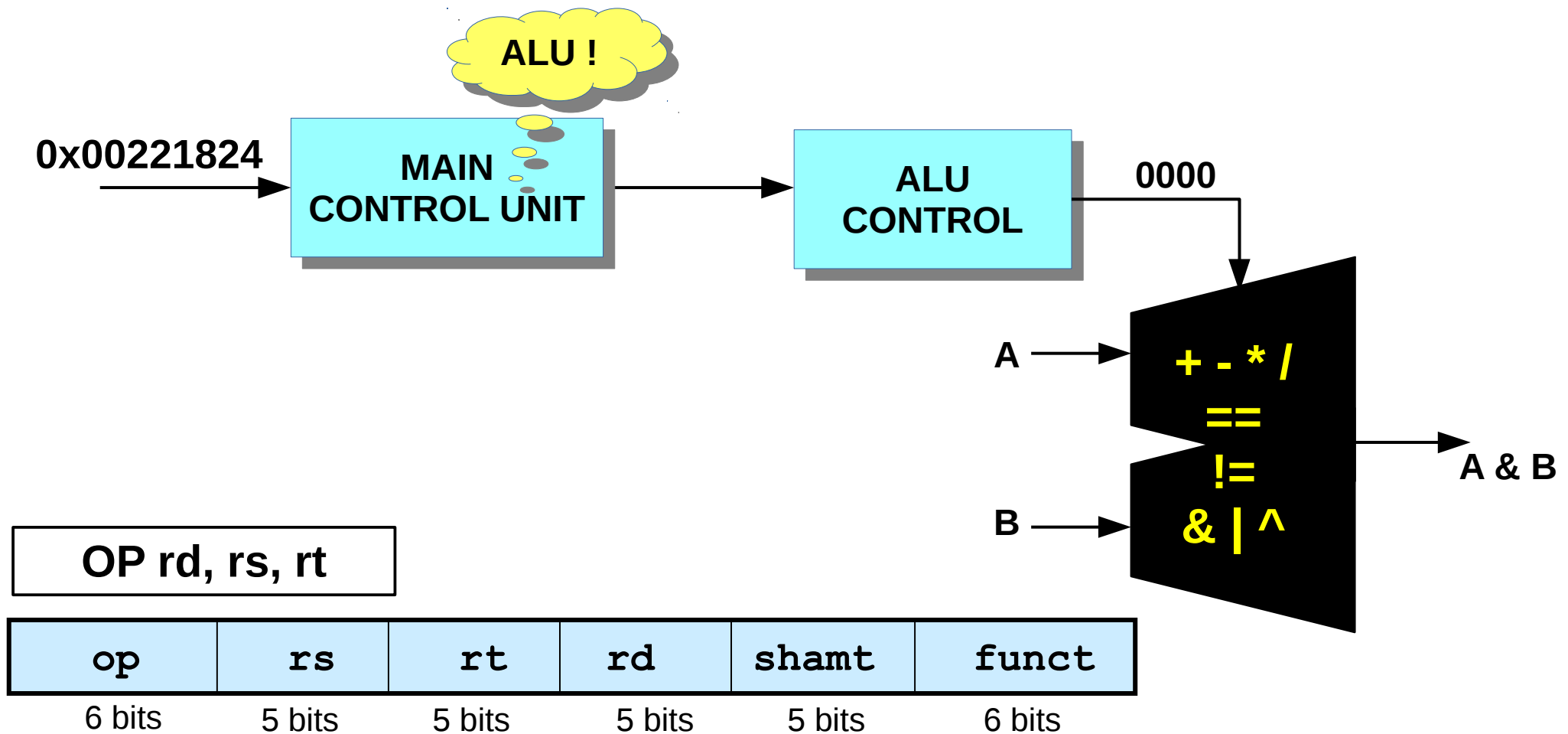


# ALU Control – AND Instruction

 

# ALU Control – AND Instruction

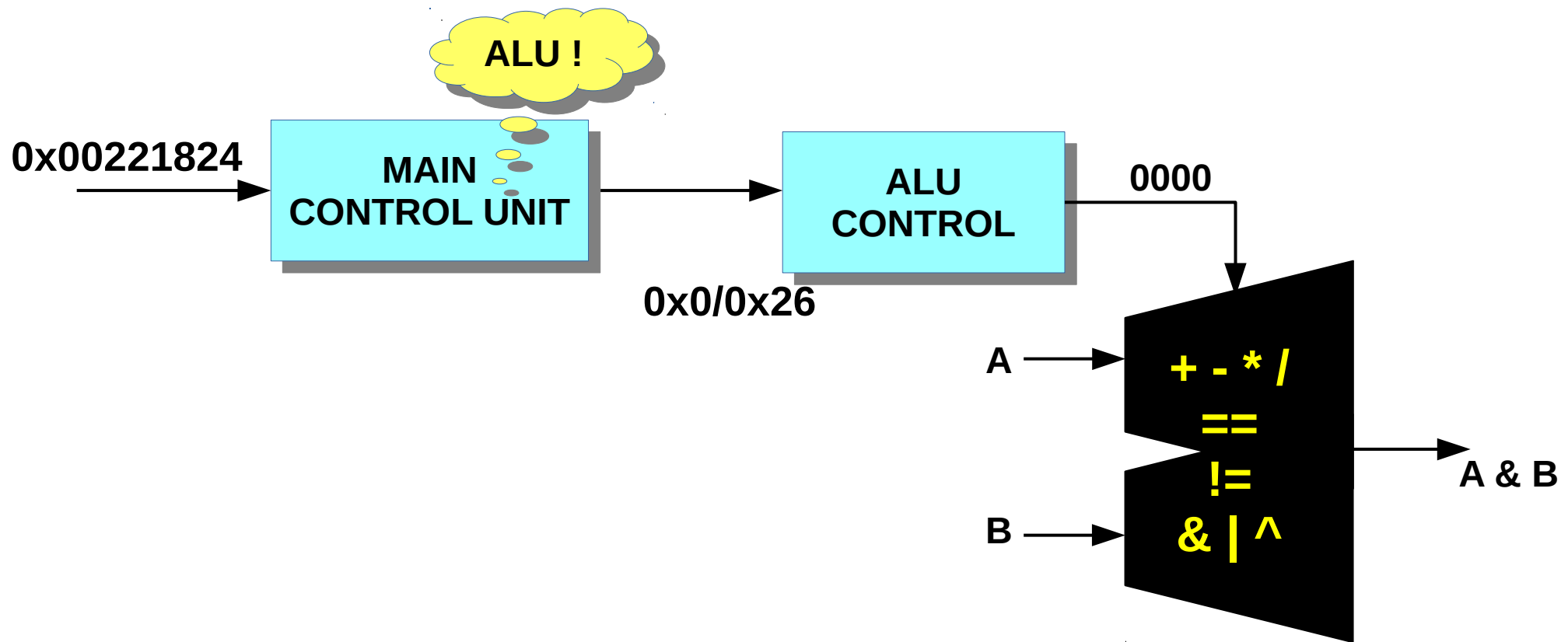


# ALU Control

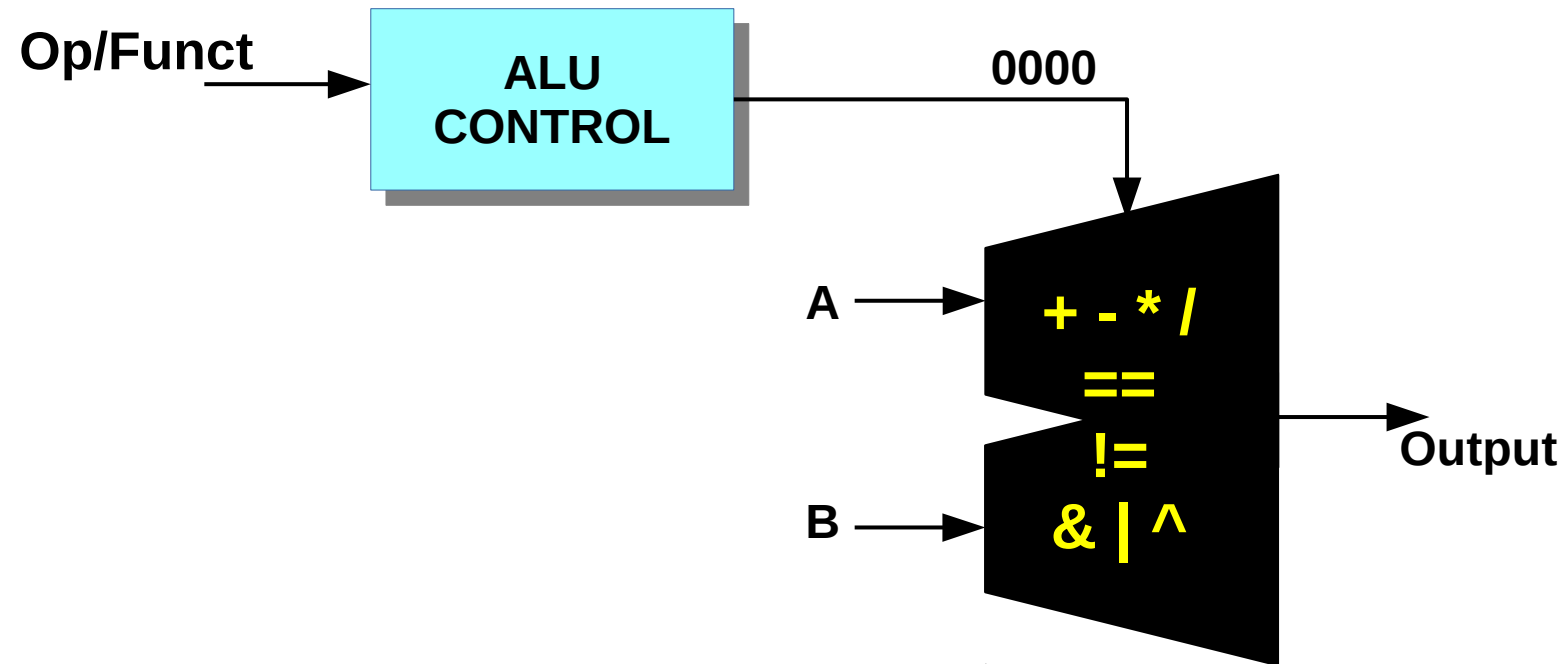

# ALU Instructions

- ALU instructions (R type), Memory Transfer (effective address calculation), Branches (BEQ)


- R-type

 

**OP rd, rs, rt**

**op:** Opcode (class of instruction). Eg. ALU  
**funct:** Which subunit of the ALU to activate?

- I-type

 

**OP rt, rs, IMM**




# ALU Instructions

- ALU instructions (R type), Memory Transfer (effective address calculation), Branches (BEQ)
- Identified by Opcode fields and Funct fields

# ALU Instructions

- ALU instructions (R type), Memory Transfer (effective address calculation), Branches (BEQ)


- R-type

 

**OP rd, rs, rt**

**op:** Opcode (class of instruction). Eg. ALU  
**funct:** Which subunit of the ALU to activate?

- I-type

 

**OP rt, rs, IMM**

# ALU Control – LW (I-type)

