

# The MIPS Processor Datapath

# Module Outline

- MIPS datapath implementation
  - Register File, Instruction memory, Data memory
- Instruction interpretation and execution.
- Combinational control
- Assignment: Datapath design and Control Unit design using SystemC.

# Logic Design Fundamentals

- Information encoded in binary
  - Low voltage = 0, High voltage = 1
  - One wire per bit
  - Multi-bit data encoded on multi-wire buses

# Logic Design Fundamentals

- Information encoded in binary
  - Low voltage = 0, High voltage = 1
  - One wire per bit
  - Multi-bit data encoded on multi-wire buses
- Combinational element
  - 
  -
- State (sequential) elements
  -

# Logic Design Fundamentals

- Information encoded in binary
  - Low voltage = 0, High voltage = 1
  - One wire per bit
  - Multi-bit data encoded on multi-wire buses
- Combinational element
  - Operate on data
  - Output is a function of input
- State (sequential) elements
  -


# Logic Design Fundamentals

- Information encoded in binary
  - Low voltage = 0, High voltage = 1
  - One wire per bit
  - Multi-bit data encoded on multi-wire buses
- Combinational element
  - Operate on data
  - Output is a function of input
- State (sequential) elements
  - Store information

# Combinational Elements


- AND-gate

- $Y = A \& B$

 


- Adder

- $Y = A + B$

 


- Multiplexer

- $Y = S ? I1 : I0$

 

- Arithmetic/Logic Unit

- $Y = F(A, B)$

 



# Sequential Elements

- Register: stores data in a circuit
  - Uses a clock signal to determine when to update the stored value
  - Edge-triggered: update when Clk changes from 0 to 1


  
# Sequential Elements

- Register: stores data in a circuit
  - Uses a clock signal to determine when to update the stored value
  - Edge-triggered: update when Clk changes from 0 to 1





# Sequential Elements

- Register with write control
  - Only updates on clock edge when write control input is 1
  - Used when stored value is required later
  
# Sequential Elements

- Register with write control
  - Only updates on clock edge when write control input is 1
  - Used when stored value is required later



# Clocking Methodology


- Combinational logic transforms data during clock cycles
  -

# Clocking Methodology

- Combinational logic transforms data during clock cycles
  - Between clock edges
  - Input from state elements, output to state element
  -

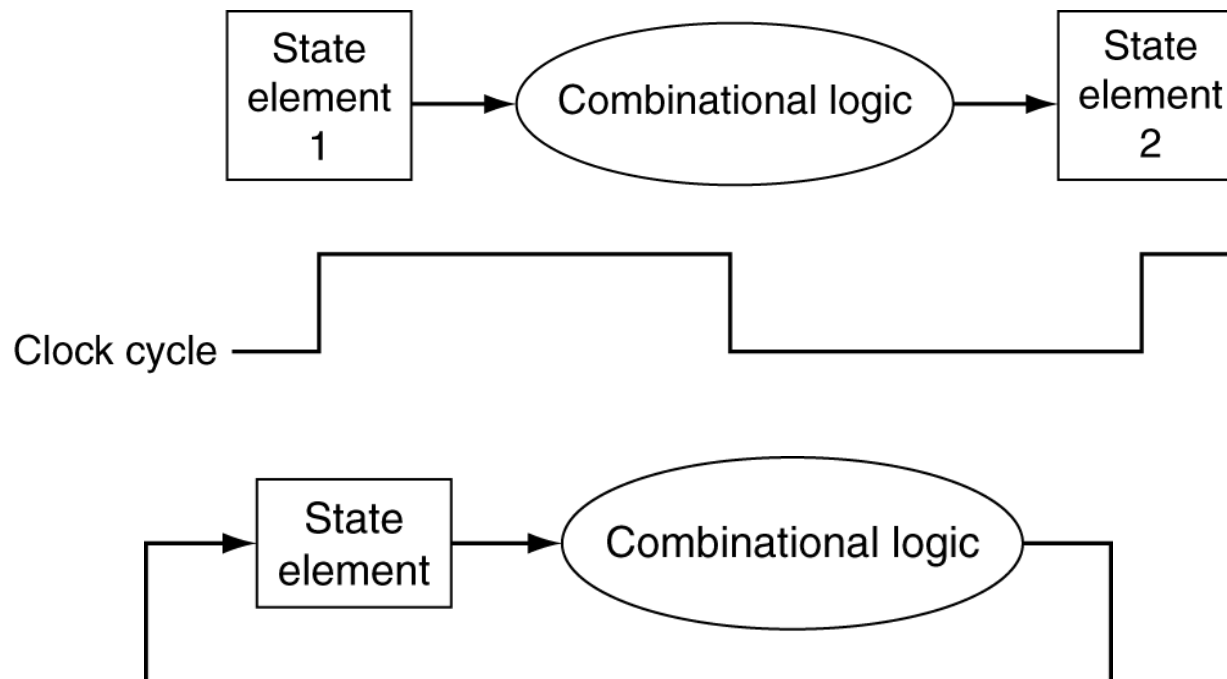
# Clocking Methodology

- Combinational logic transforms data during clock cycles
  - Between clock edges
  - Input from state elements, output to state element
  -


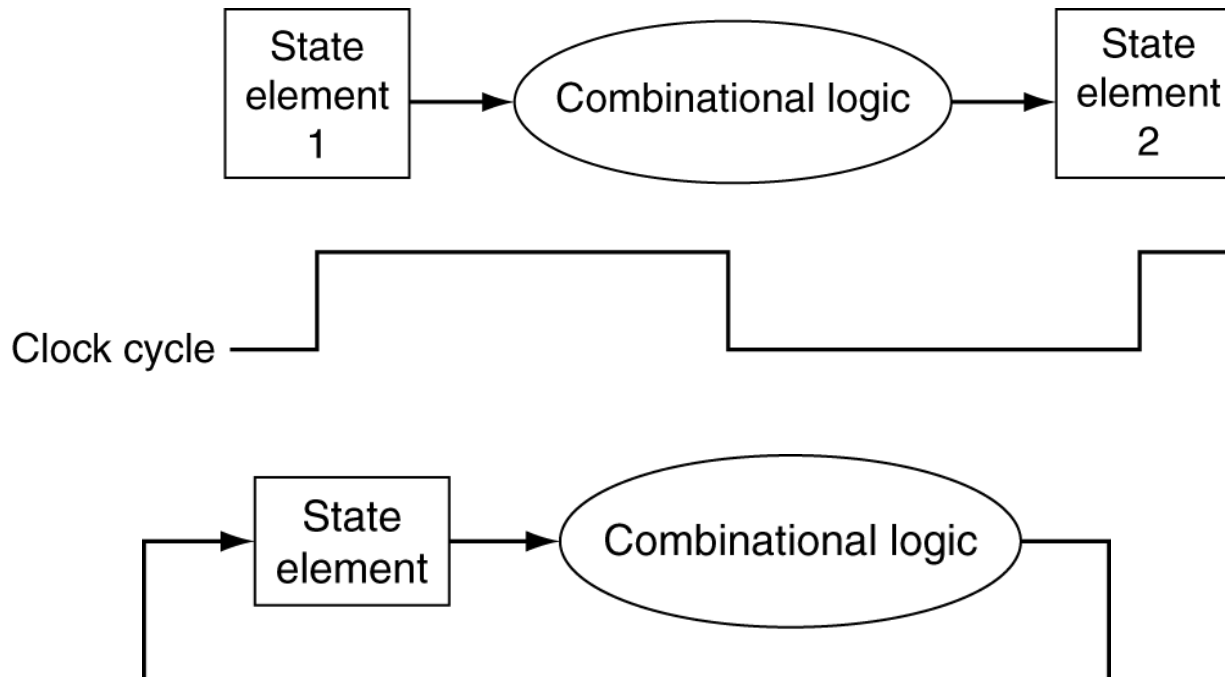
# Clocking Methodology

- Combinational logic transforms data during clock cycles
  - Between clock edges
  - Input from state elements, output to state element
  - Longest delay determines clock period



# Building a Datapath

- Datapath

-



# Building a Datapath

- Datapath
  - Elements that process data and addresses in the CPU
    -
-

# Building a Datapath

- Datapath
  - Elements that process data and addresses in the CPU
    - Registers, ALUs, muxes, memories, ...
-

# Building a Datapath

- Datapath
  - Elements that process data and addresses in the CPU
    - Registers, ALUs, muxes, memories, ...
- We will build a MIPS datapath incrementally

# A Basic MIPS Implementation

- Memory-reference instructions – Load Word (lw) and Store Word (sw)
- ALU instructions – add, sub, AND, OR and slt
- Branch on equal (beq)

# Instruction Execution – Steps

# Instruction Execution – Steps

- Instruction Fetch

# Instruction Execution – Steps

- Instruction Fetch
- Instruction Decode/Register Fetch

# Instruction Execution – Steps

- Instruction Fetch
- Instruction Decode/Register Fetch
- Execute
  - ALU
  - Effective Address Calculation



# Instruction Execution – Steps

- Instruction Fetch
- Instruction Decode/Register Fetch
- Execute
  - ALU
  - Effective Address Calculation
- Memory Access

# Instruction Execution – Steps

- Instruction Fetch
- Instruction Decode/Register Fetch
- Execute
  - ALU
  - Effective Address Calculation
- Memory Access
- Write back (Update RF)

# Instruction Fetch – Actions

# Instruction Fetch – Actions

- Read Program Counter

# Instruction Fetch – Actions




- Read Program Counter
- Fetch instruction from Instruction memory pointed to by the PC

# Instruction Fetch – Actions

- Read Program Counter
- Fetch instruction from Instruction memory pointed to by the PC
- Increment PC


# Instruction Fetch – Elements

# Instruction Fetch – Elements

 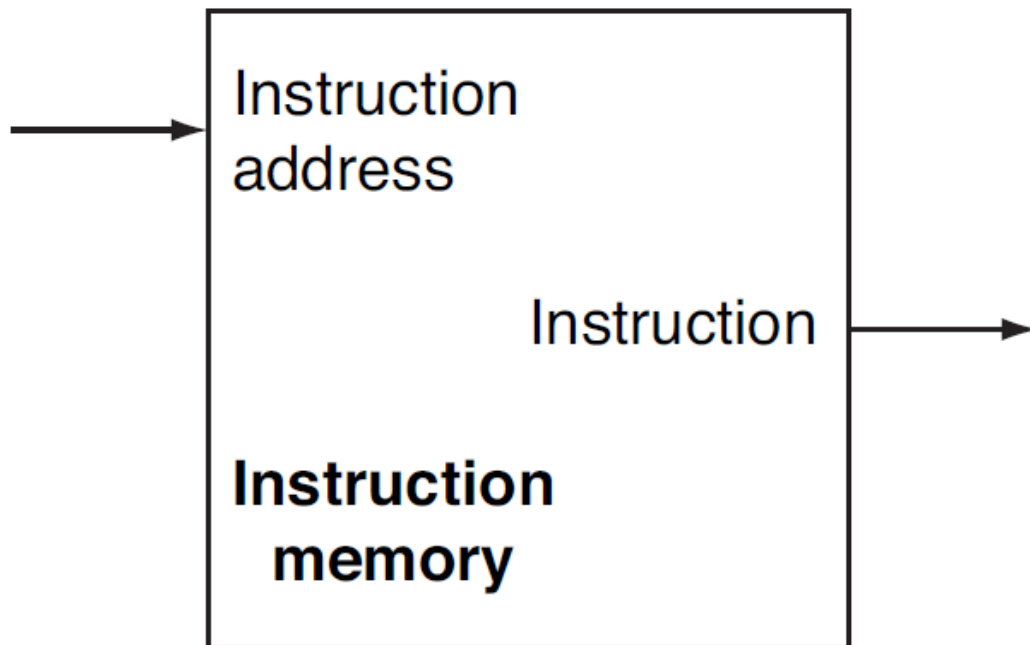 



# Instruction Fetch

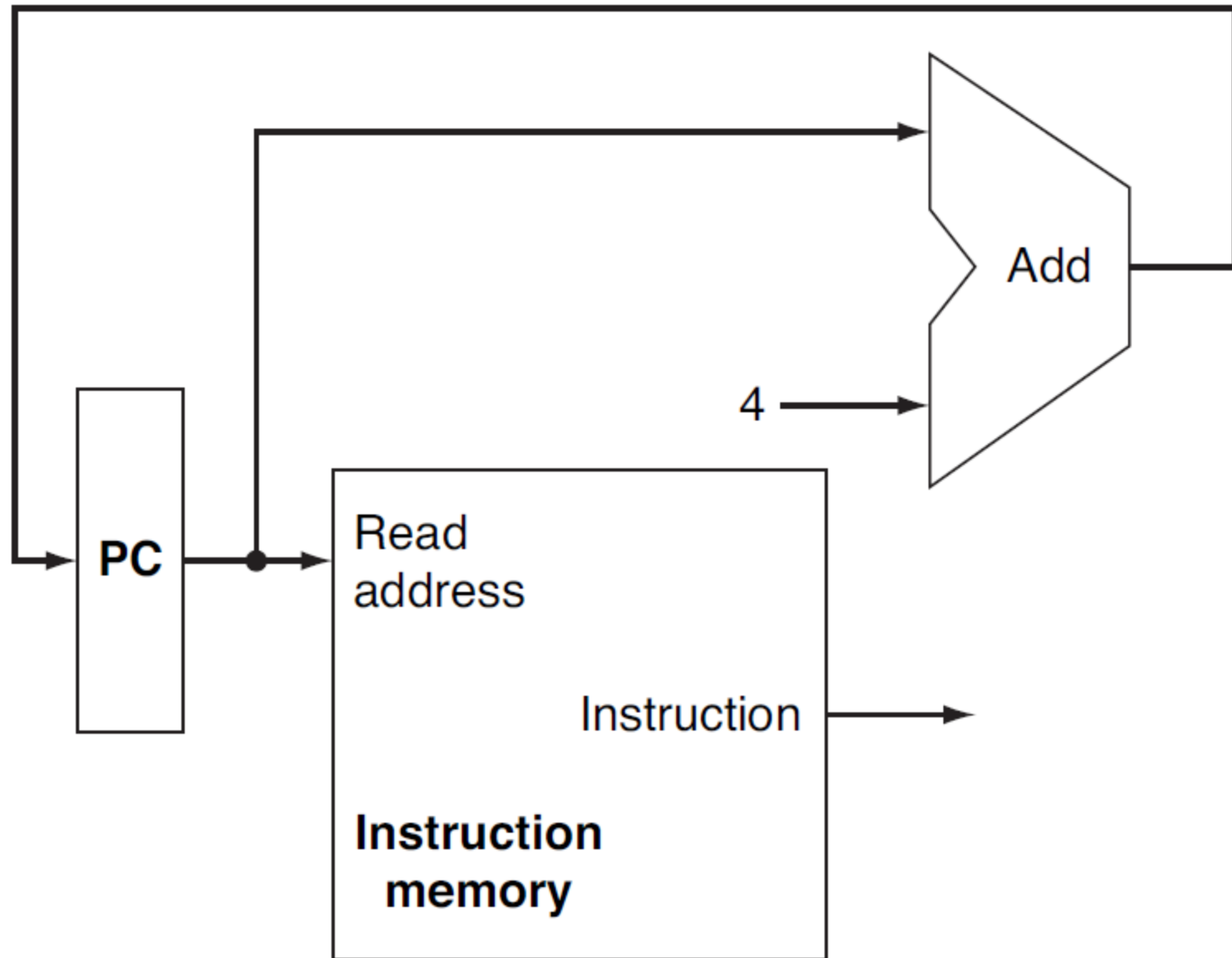

# ALU Instructions – Operations

**ADD R1, R2, R3**

# ALU Instructions – Operations

- Read R2 and R3 from Register file
  - Send 2 and 3 to RF
  - RF reads contents of R2 and R3

**ADD R1, R2, R3**

# ALU Instructions – Operations

- Read R2 and R3 from Register file
  - Send 2 and 3 to RF
  - RF reads contents of R2 and R3
- Add contents of R2 and R3 in the ALU

ADD R1, R2, R3

# ALU Instructions – Operations


- Read R2 and R3 from Register file
  - Send 2 and 3 to RF
  - RF reads contents of R2 and R3
- Add contents of R2 and R3 in the ALU
- Feed the sum output to the RF; Ask it to write into R1

**ADD R1, R2, R3**

# ALU Operations – Elements


**ADD R1, R2, R3**

# ALU Operations – Elements

 

ADD R1, R2, R3


# ALU Operations – Elements

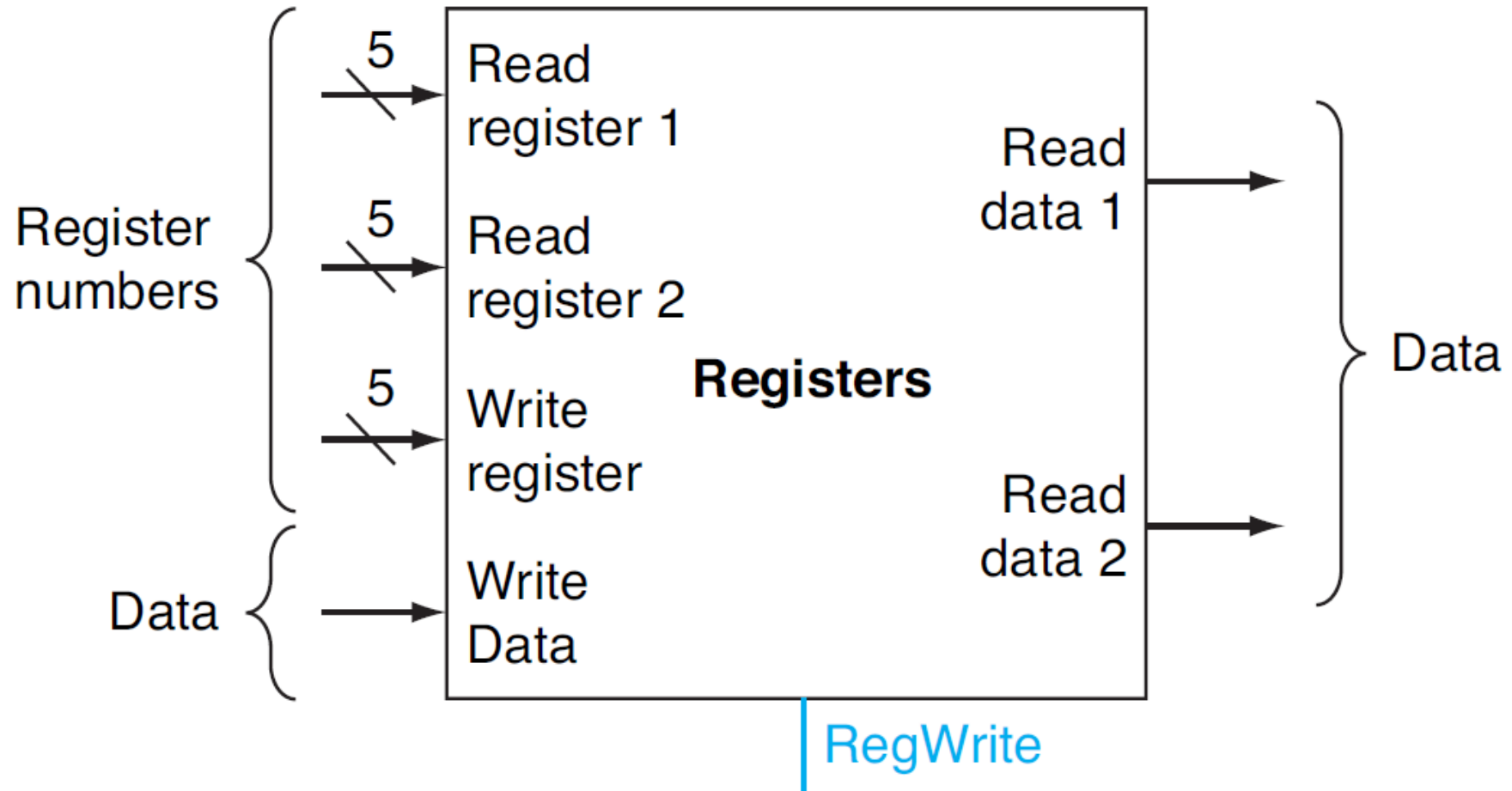

**ADD R1, R2, R3**



# ALU Operations – Elements

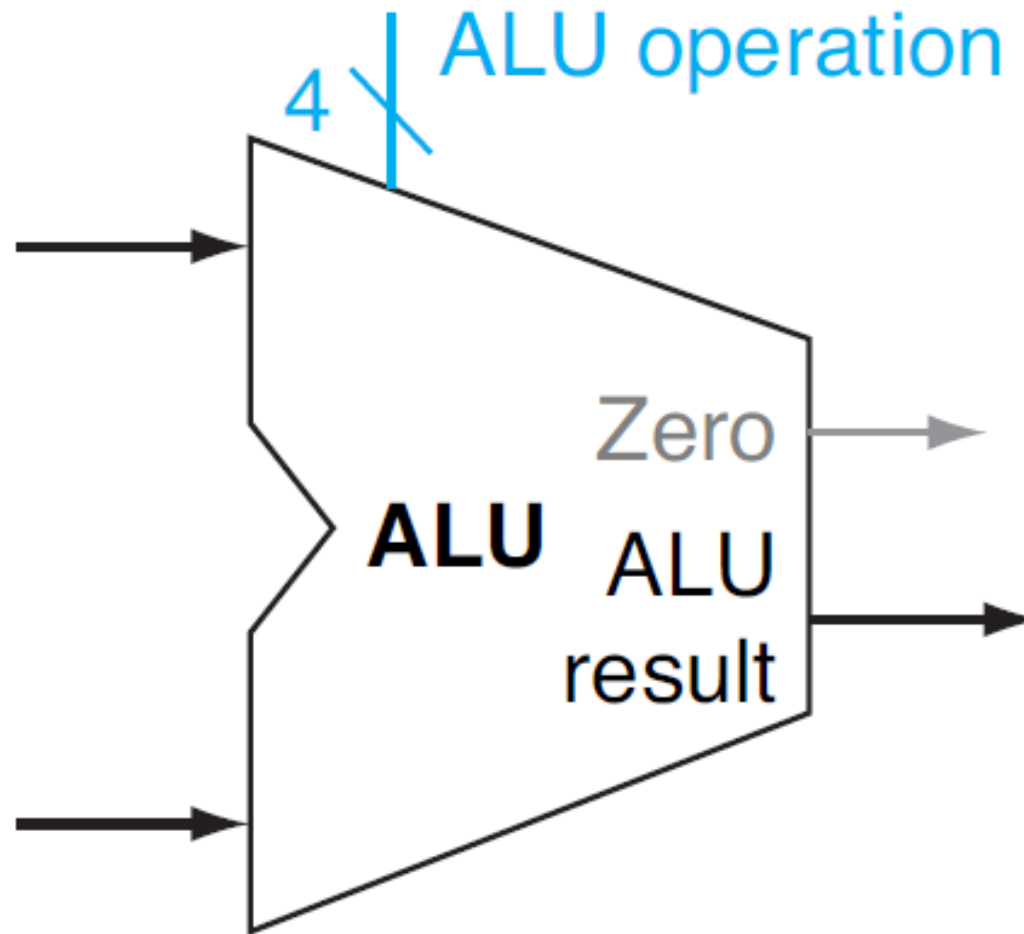

ADD R1, R2, R3

# ALU Operations – Datapath


ADD R1, R2, R3

# ALU Operations – Datapath

- How will the design change for ADDI?

ADDI R1, R2, -13

# ALU Operations – Datapath

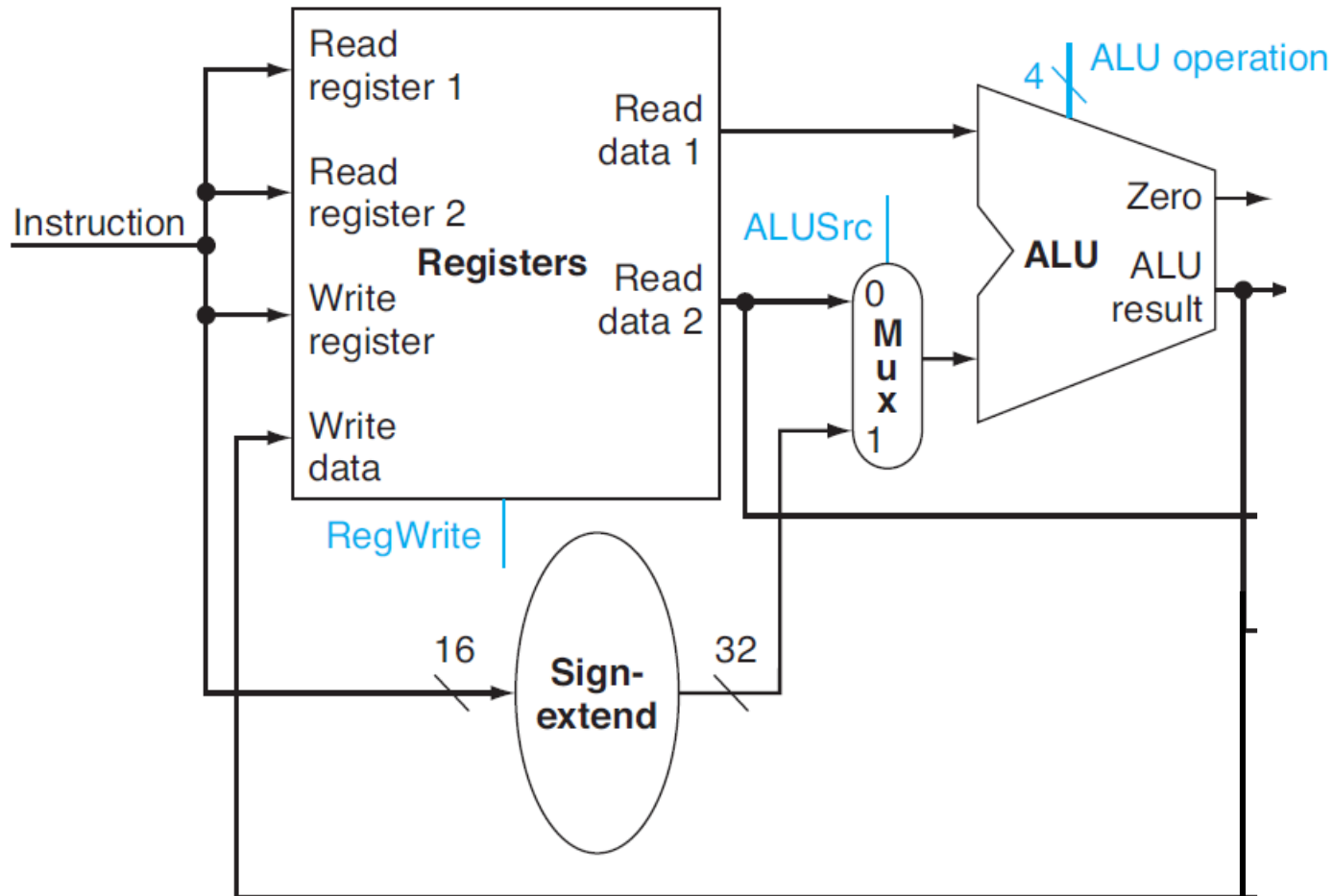

**ADDI R1, R2, -13**

# Loads and Stores – Actions

LW R1, -8(R2)

# Loads and Stores – Actions

- Calculate full address
  - Sum of -8 (offset) and contents of R2 (base)
  - Size of offset? Size of contents of R2?

LW R1, -8(R2)

# Loads and Stores – Actions

- Calculate full address
  - Sum of -8 (offset) and contents of R2 (base)
  - Size of offset? Size of contents of R2?
- Send the address to Data memory

LW R1, -8(R2)

# Loads and Stores – Actions

- Calculate full address
  - Sum of -8 (offset) and contents of R2 (base)
  - Size of offset? Size of contents of R2?
- Send the address to Data memory
- DM reads out the contents of  $\text{Mem}[\text{R2}+(-8)]$

LW R1, -8(R2)




# Loads and Stores – Actions

- Calculate full address
  - Sum of -8 (offset) and contents of R2 (base)
  - Size of offset? Size of contents of R2?
- Send the address to Data memory
- DM reads out the contents of  $\text{Mem}[\text{R2}+(-8)]$
- Feed the value from memory to the RF; Ask it to write the value into R1


LW R1, -8(R2)

# Loads and Stores – Elements

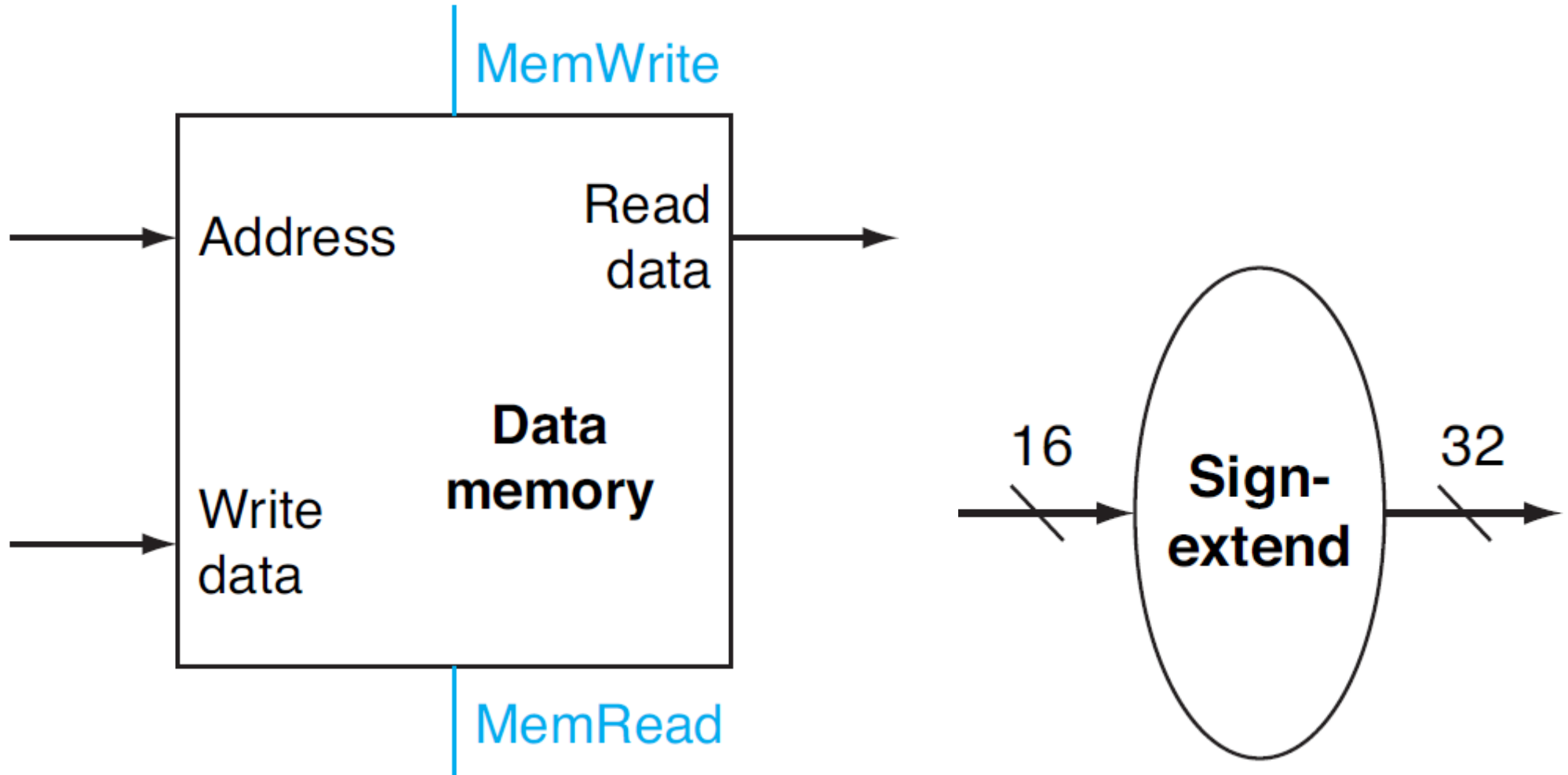


LW R1, -8(R2)

# Memory and R-type Instructions

 


# Memory Instruction – Load

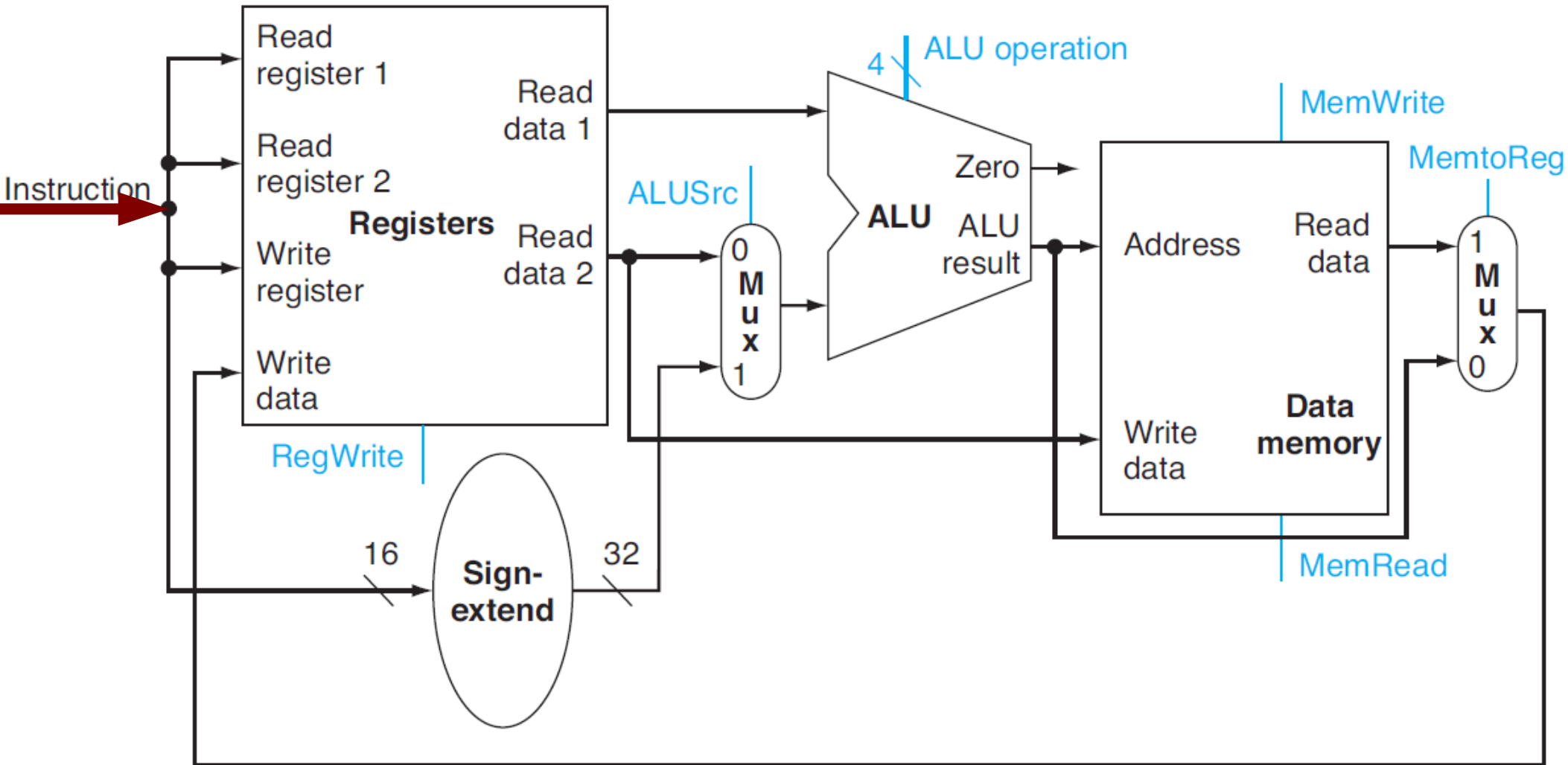


LW R1, -8(R2)

# Memory Instruction – Load

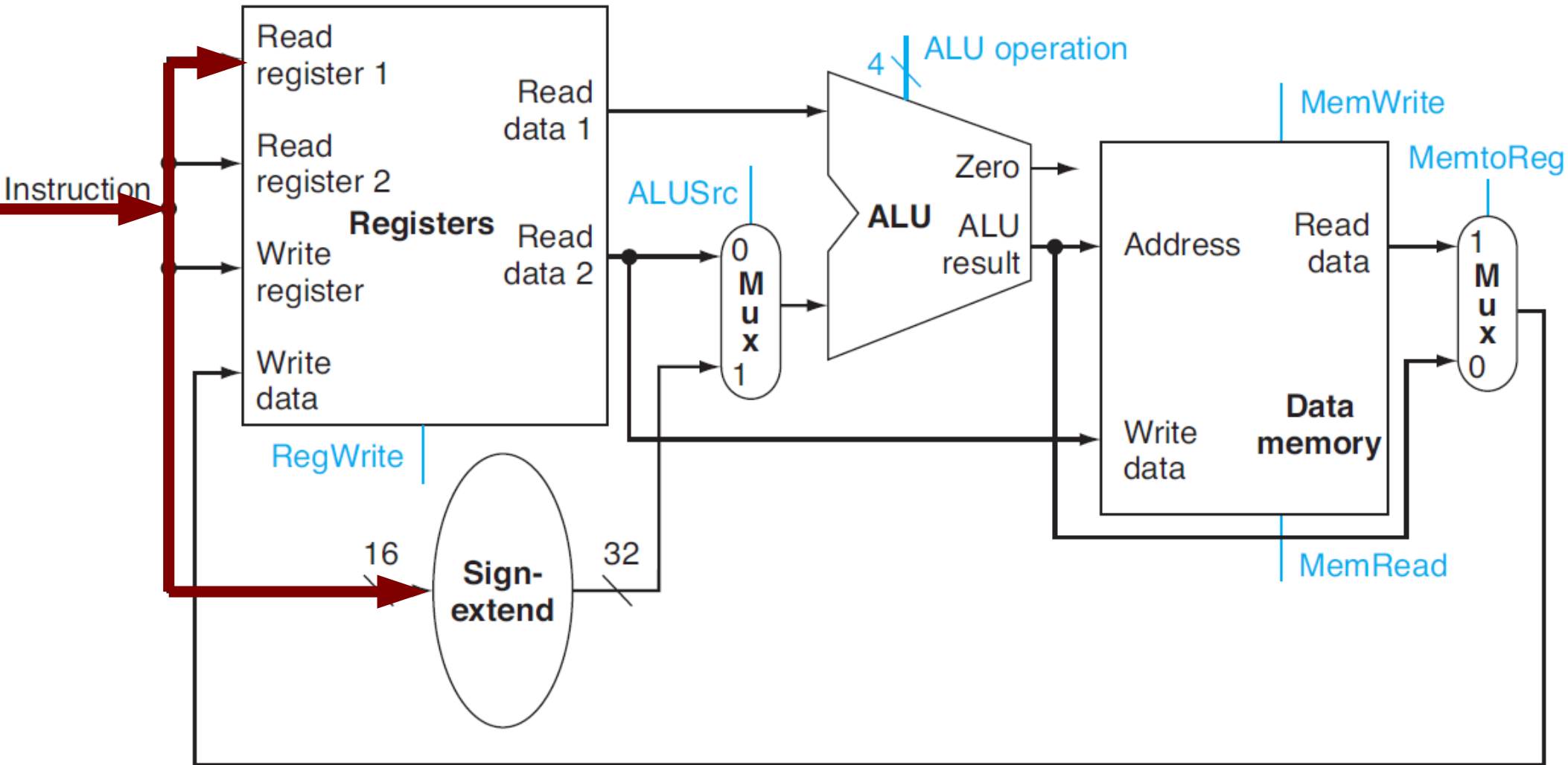


LW R1, -8(R2)

# Memory Instruction – Load

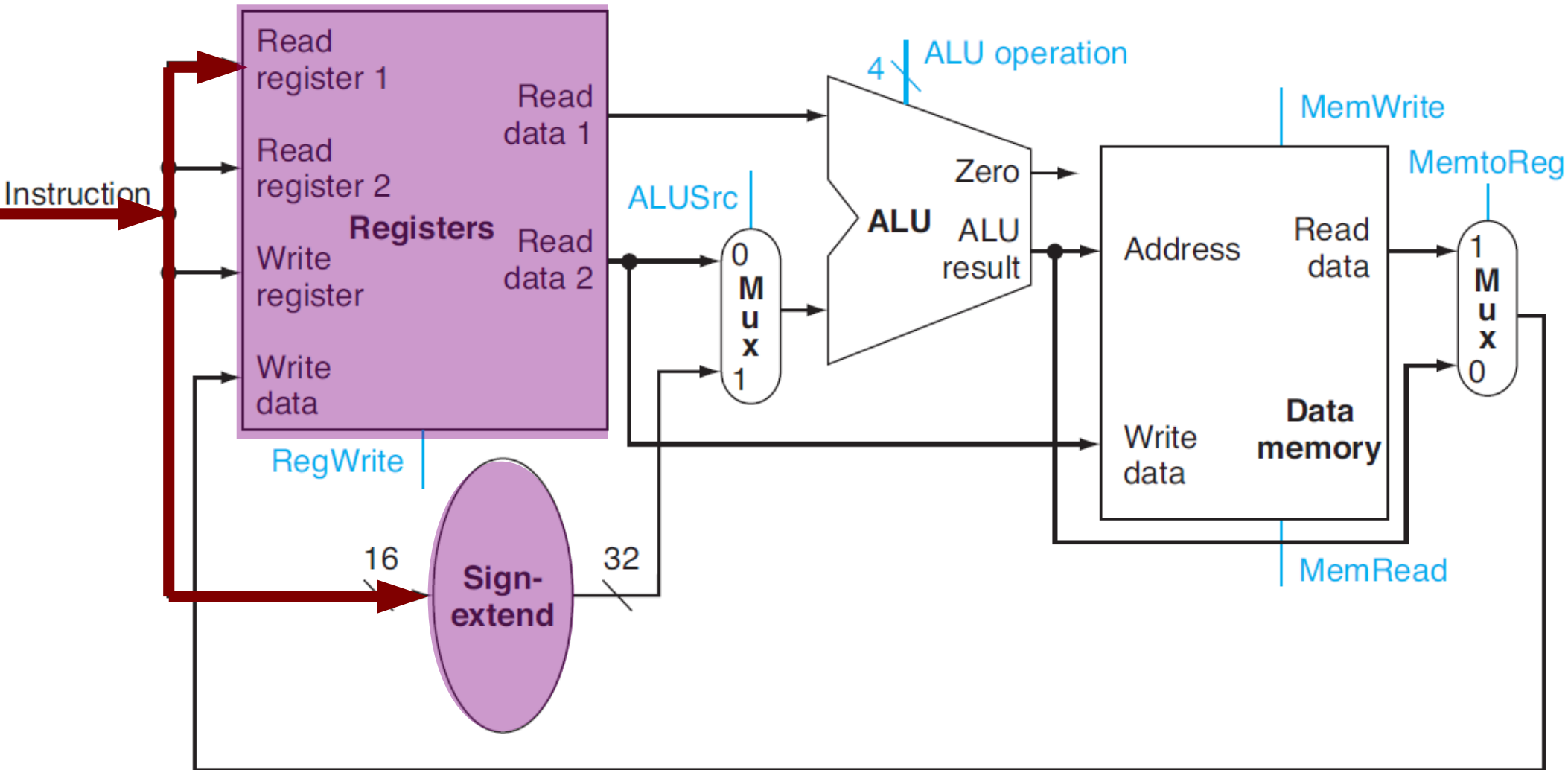


LW R1, -8(R2)

# Memory Instruction – Load

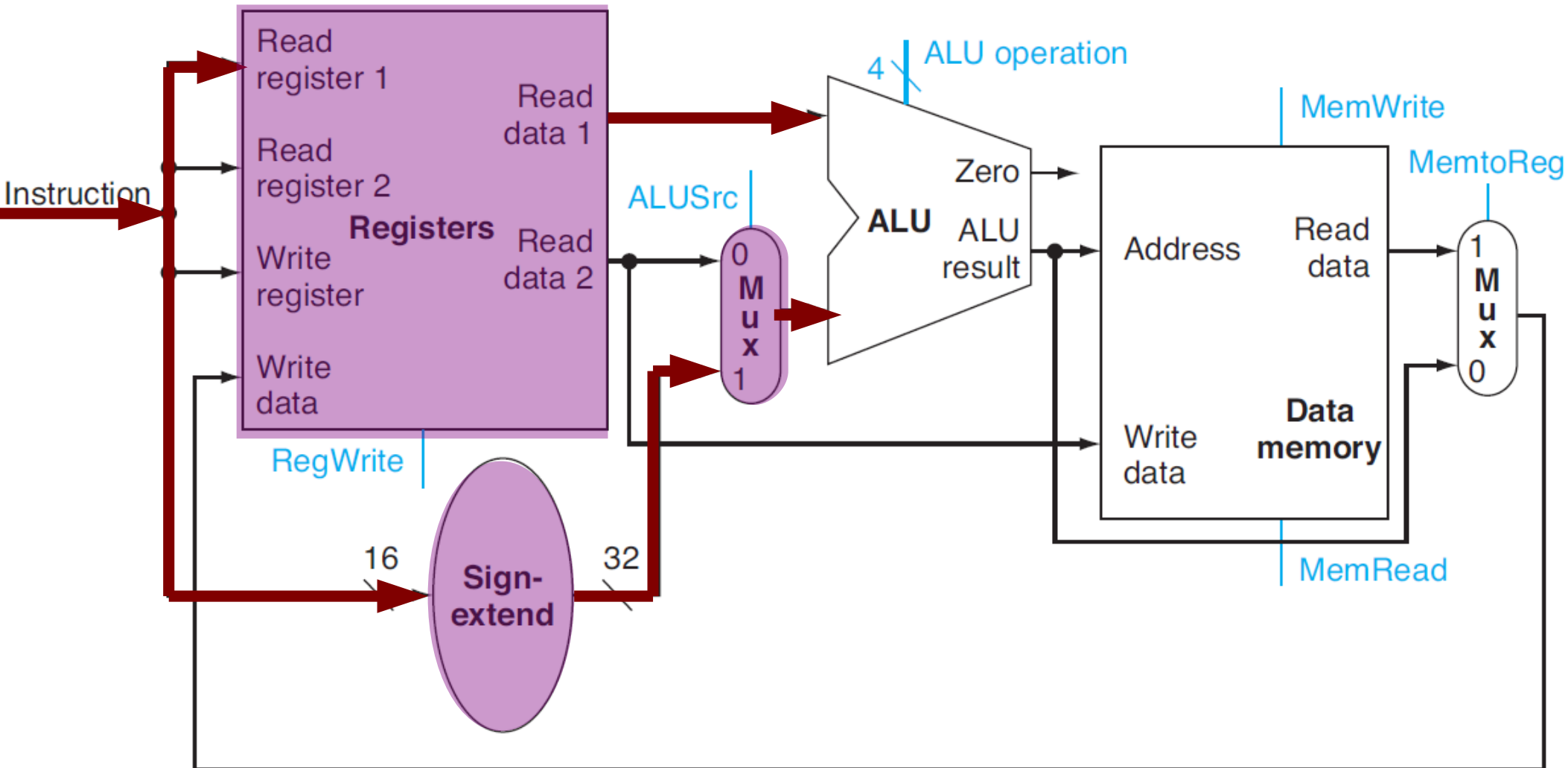

LW R1, -8(R2)


# Memory Instruction – Load

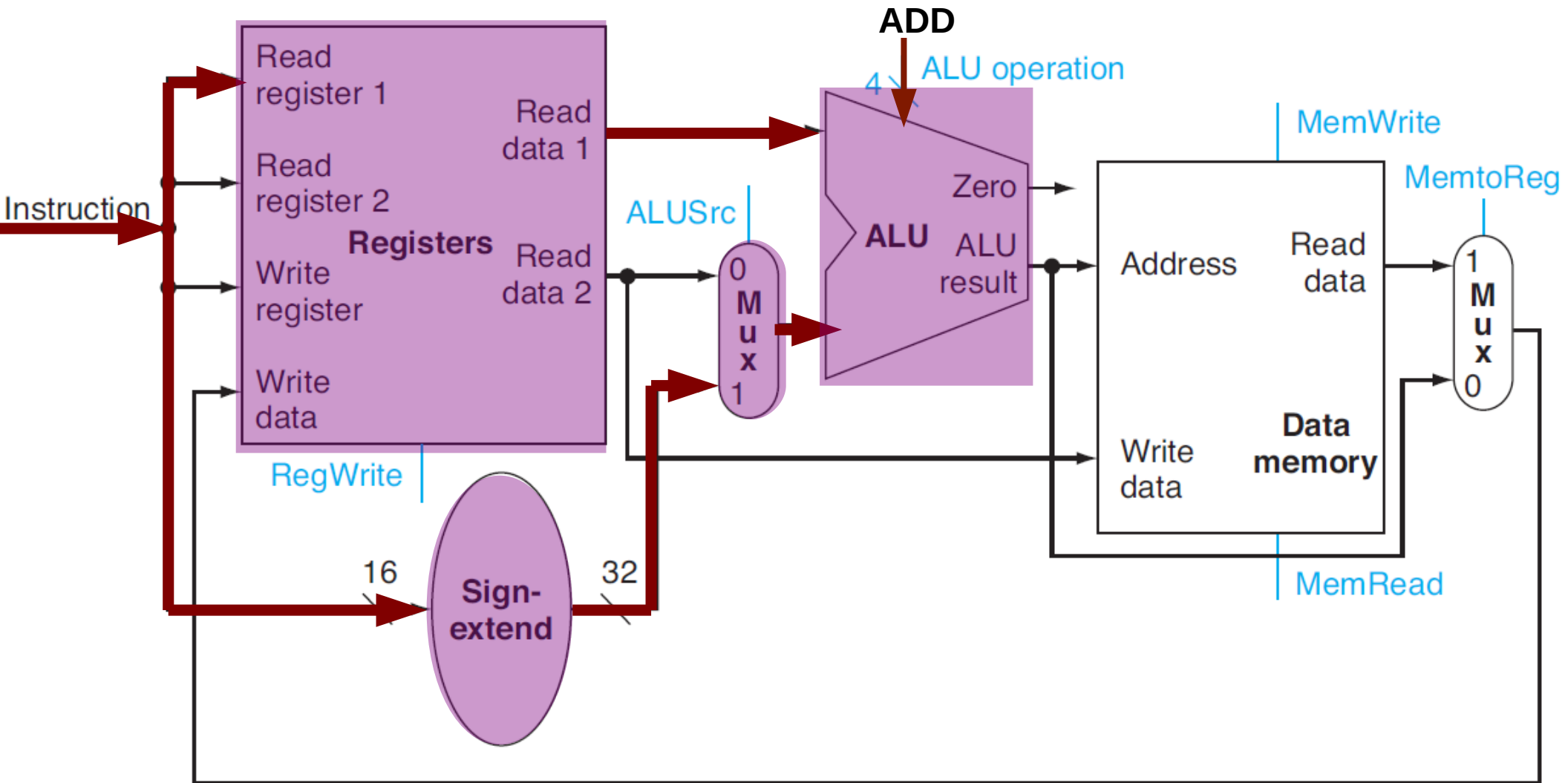

LW R1, -8(R2)




# Memory Instruction – Load

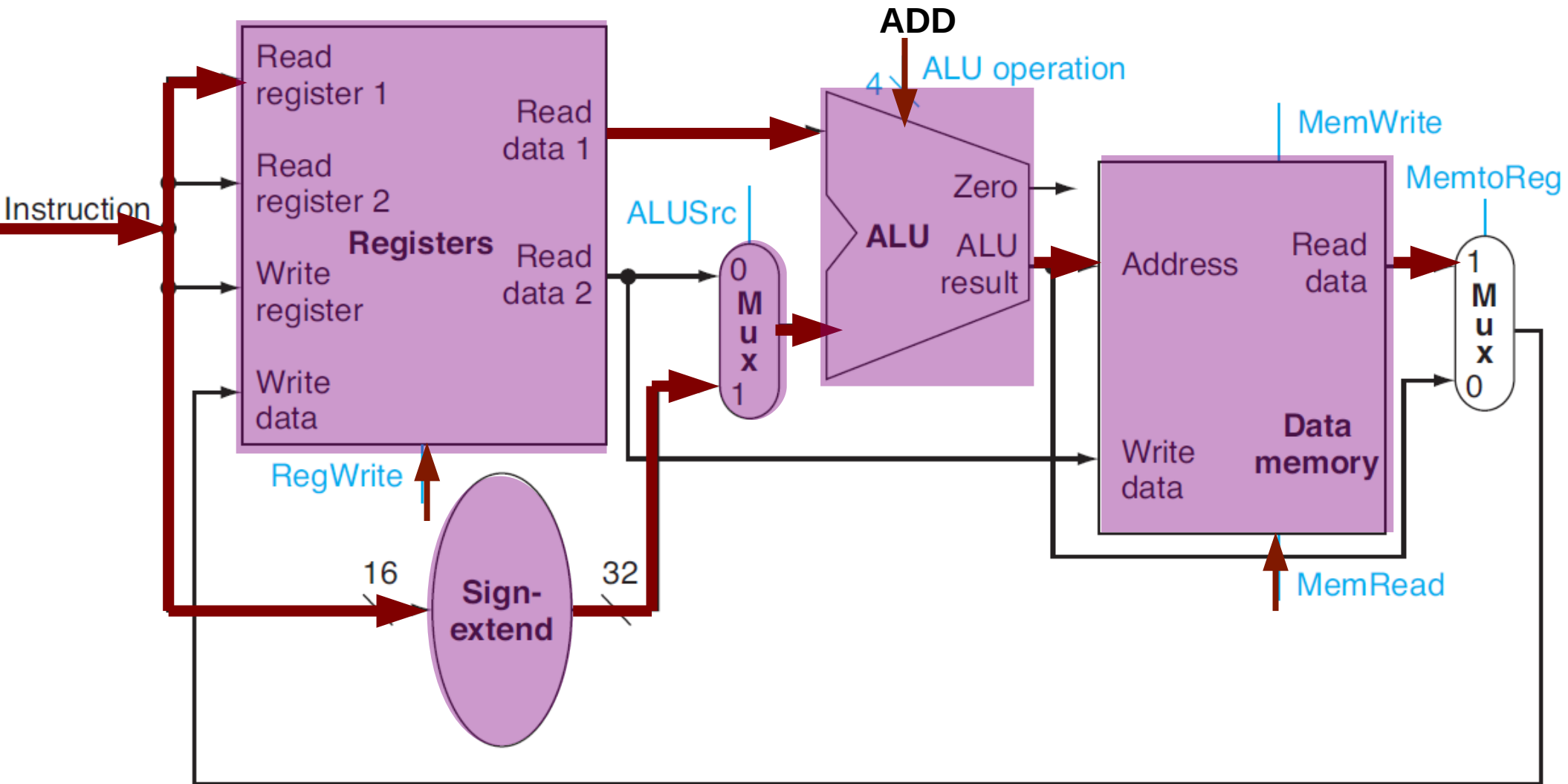


LW R1, -8(R2)

# Memory Instruction – Load

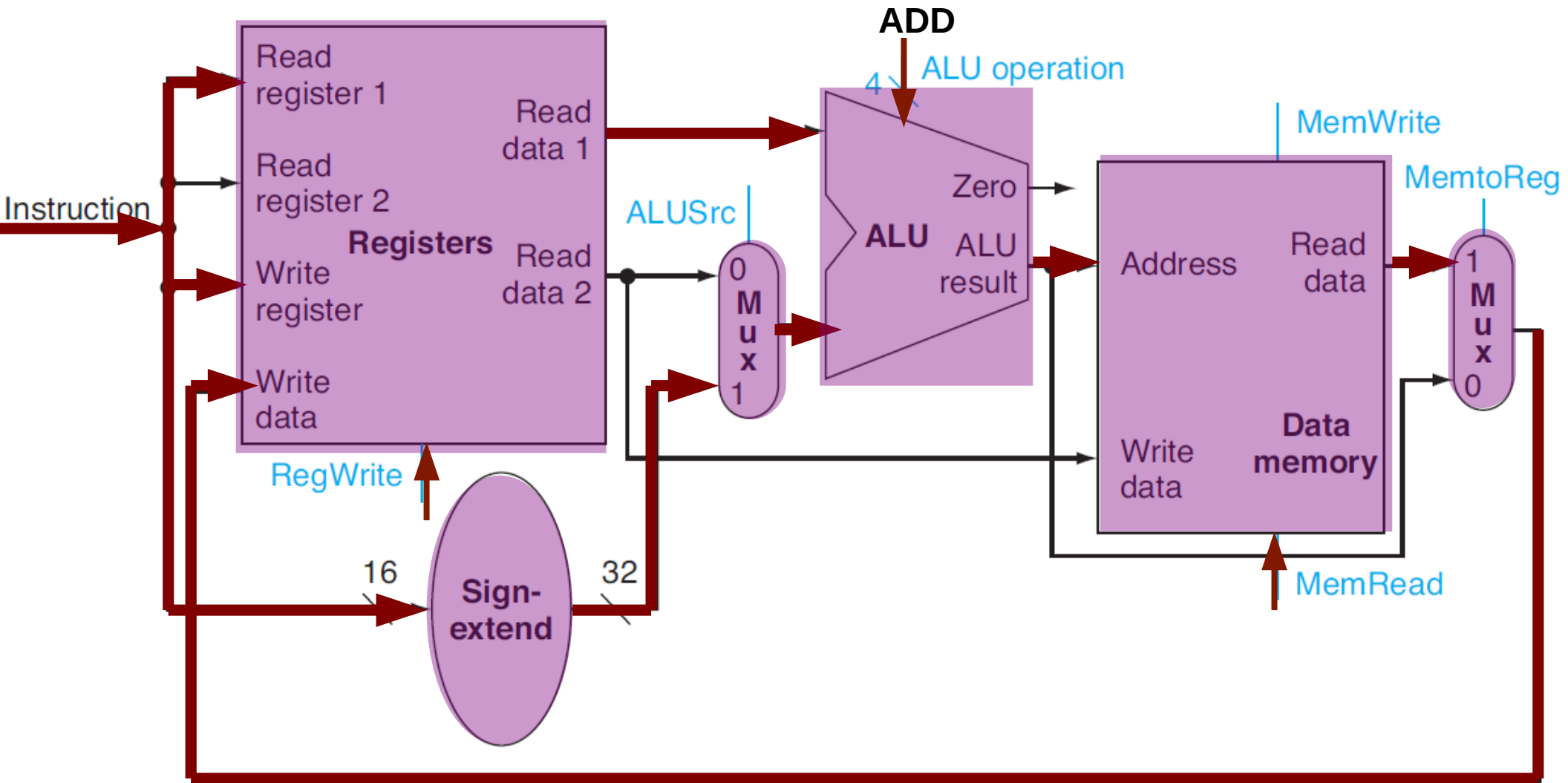


LW R1, -8(R2)

# Memory Instruction – Load

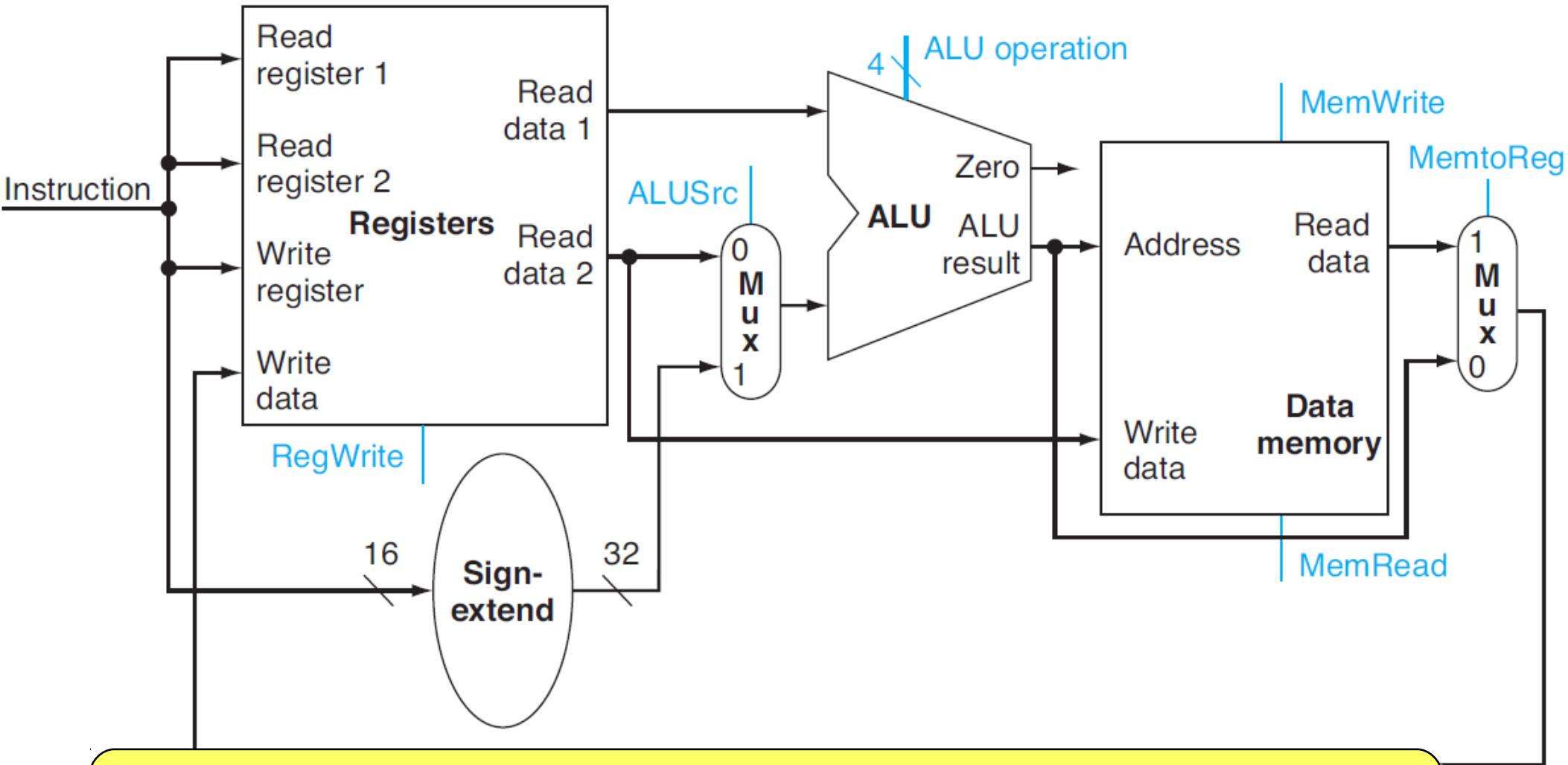


**Control Signals: RegWrite=1; ALUSrc=1; ALUoperation=ADD;  
MemRead=1; MemWrite=0; MemToReg=1;**

# Memory Instruction – Store

 


SW R1, -8(R2)

# Memory Instruction – Store

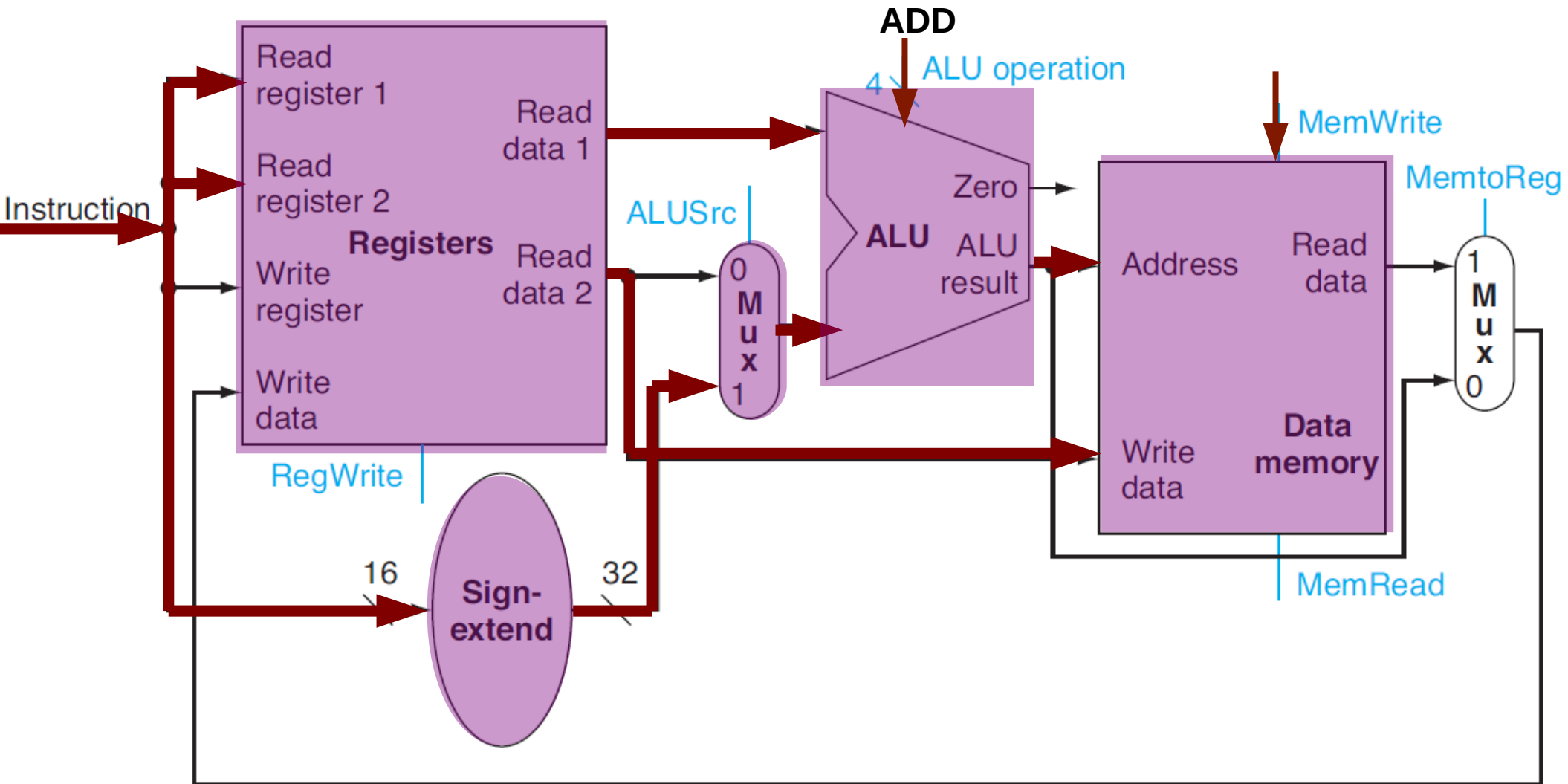


SW R1, -8(R2)

# Memory Instruction – Store

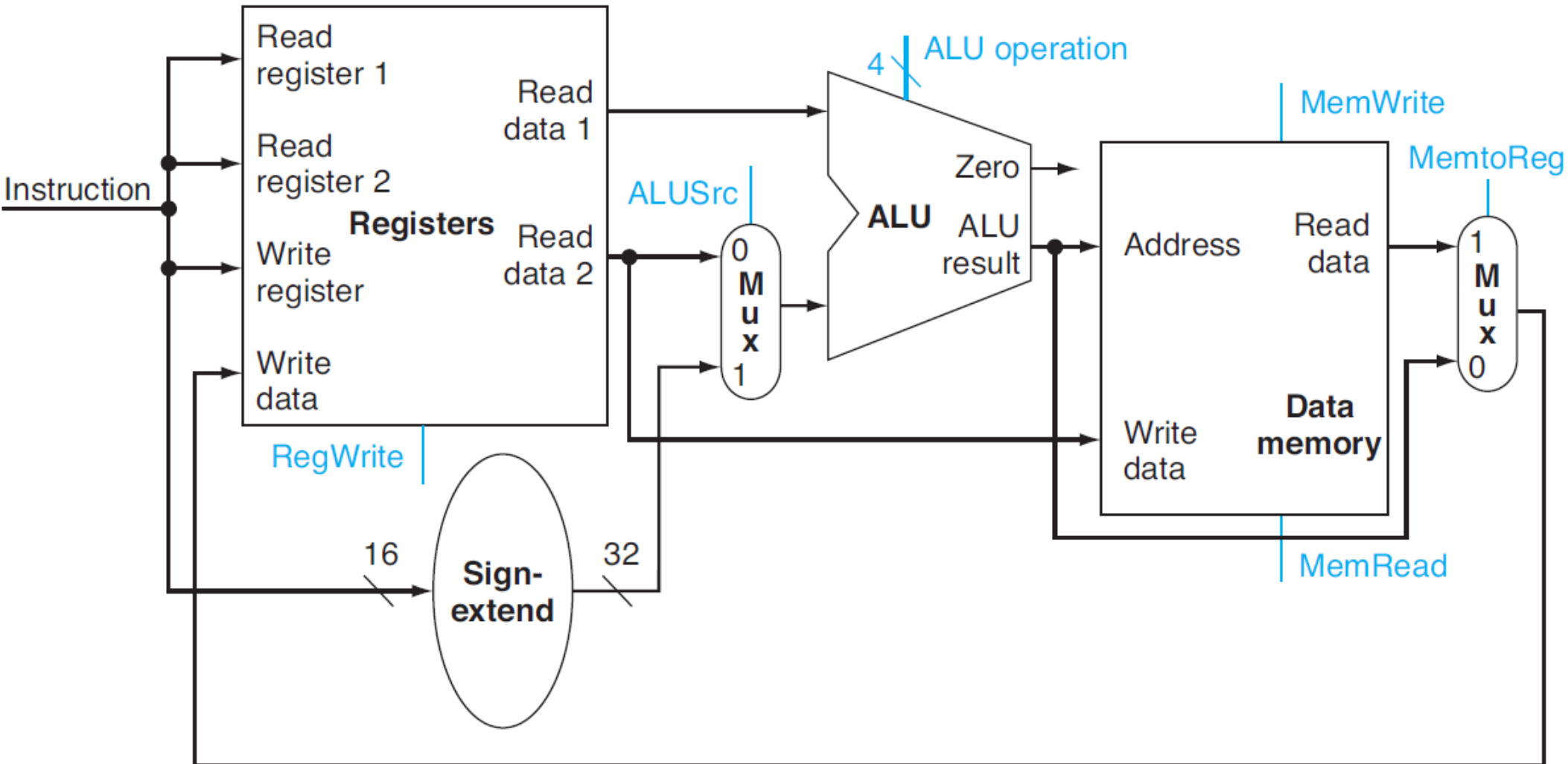


**Control Signals:**

# Memory Instruction – Store

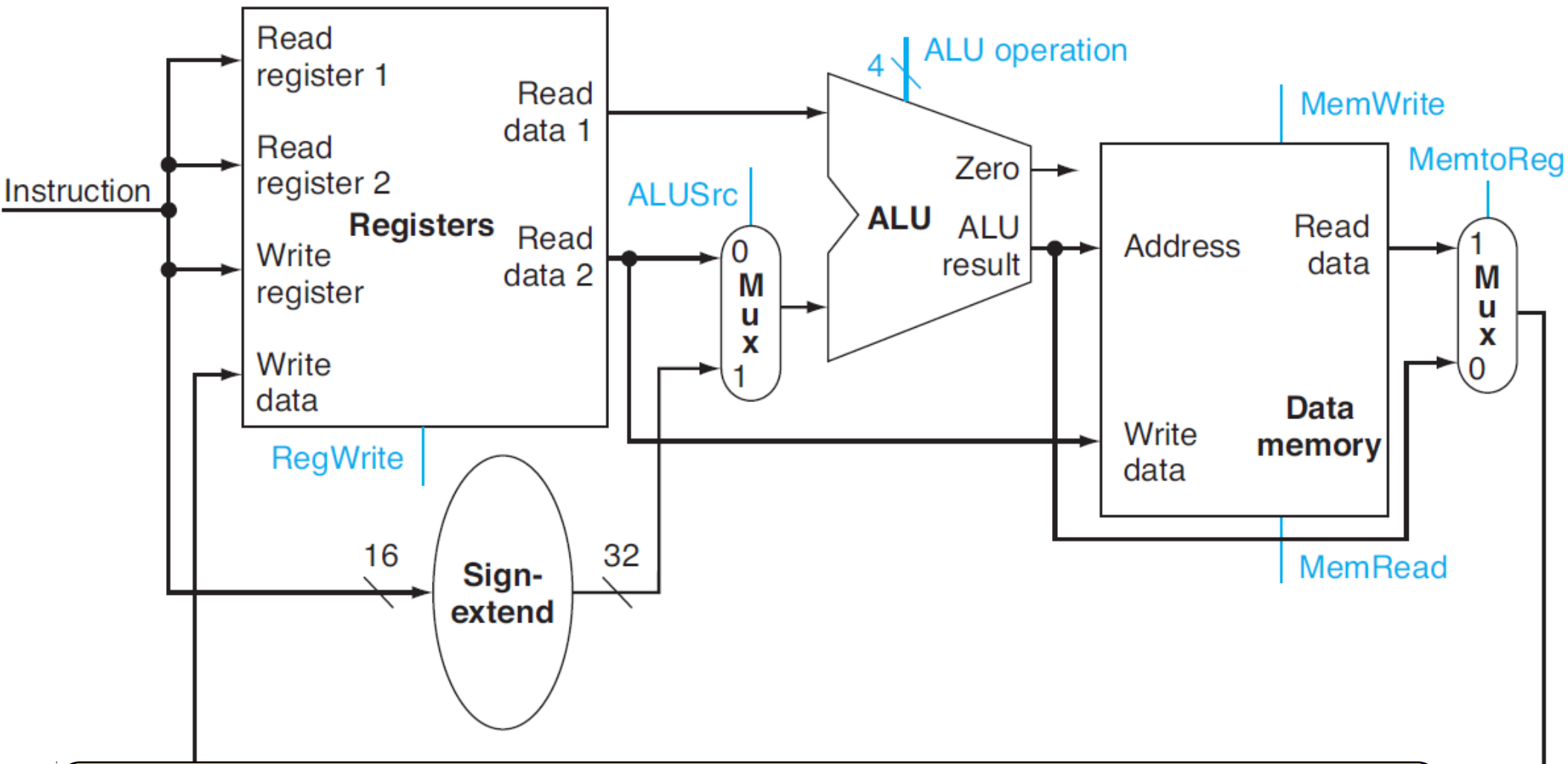

**Control Signals: RegWrite=0; ALUSrc=1; ALUoperation=ADD;  
MemRead=0; MemWrite=1; MemToReg=X;**


# R Type Instruction – ADD

 

ADD R1, R2, R3




# R Type Instruction – ADD

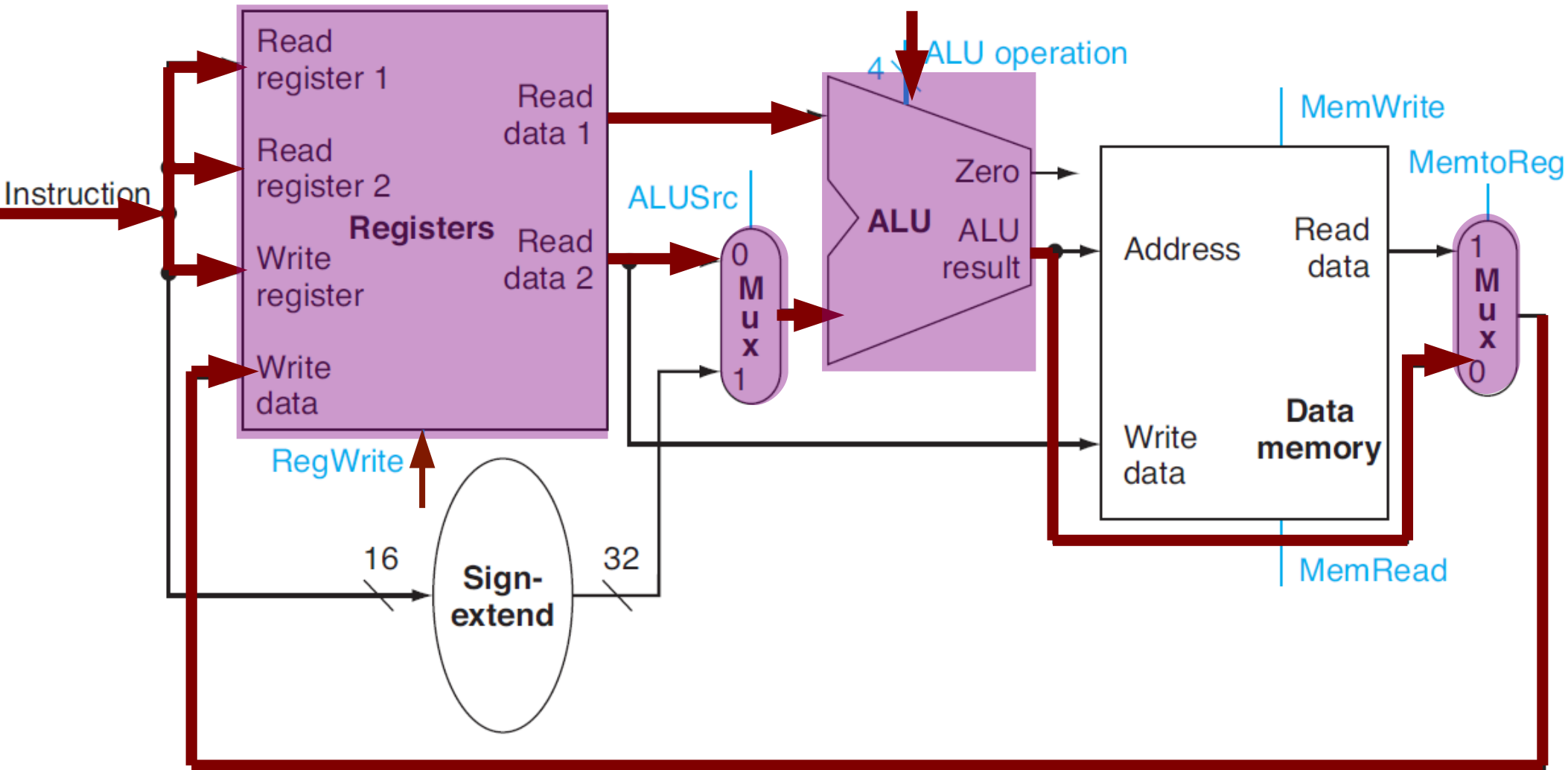


ADD R1, R2, R3

# R Type Instruction – ADD

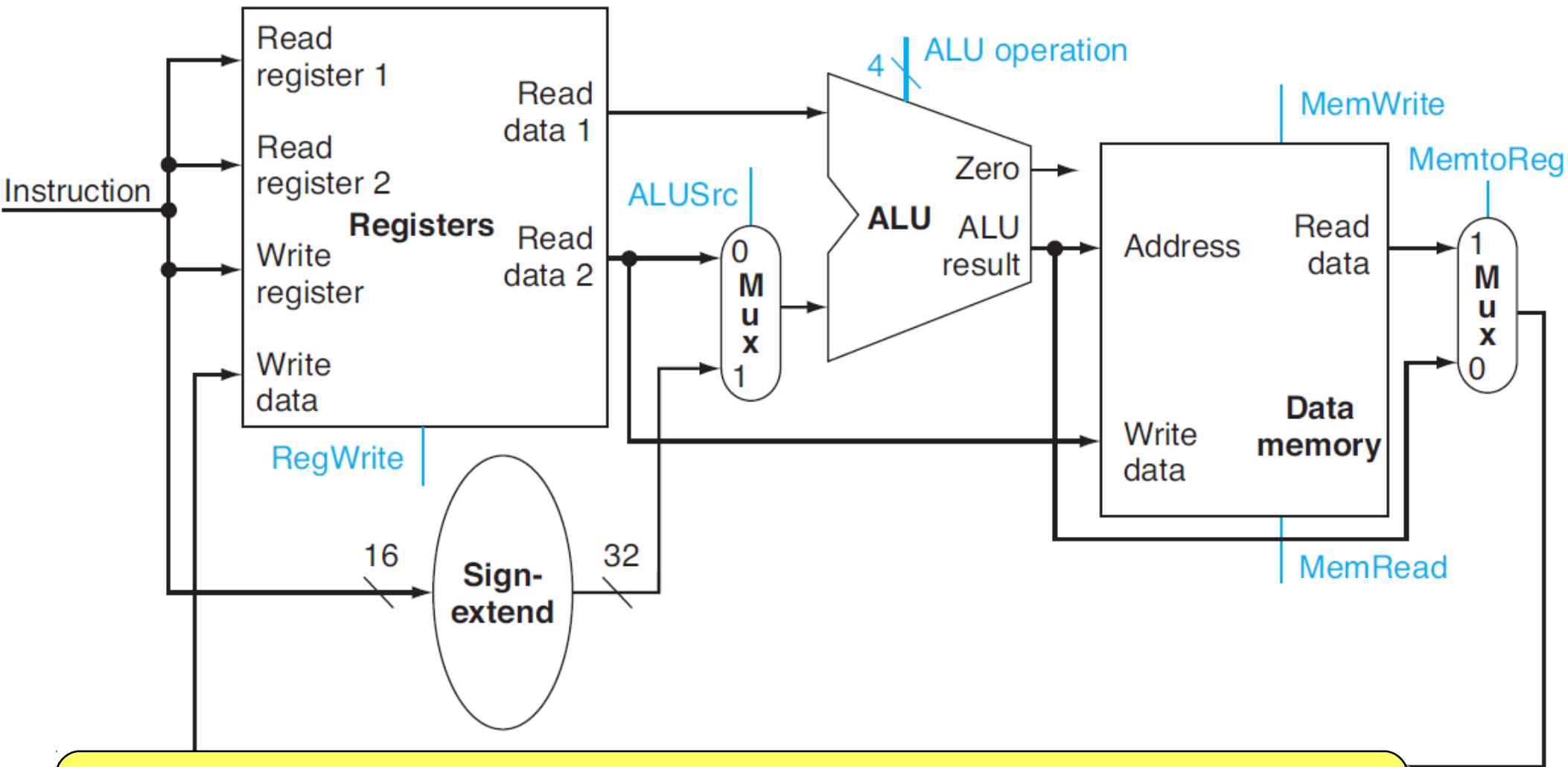


**Control Signals:**

# R Type Instruction – ADD

 


**Control Signals: RegWrite=1; ALUSrc=0; ALUoperation=ADD;  
MemRead=X; MemWrite=X; MemToReg=0;**

# I Type Instruction – ADDI

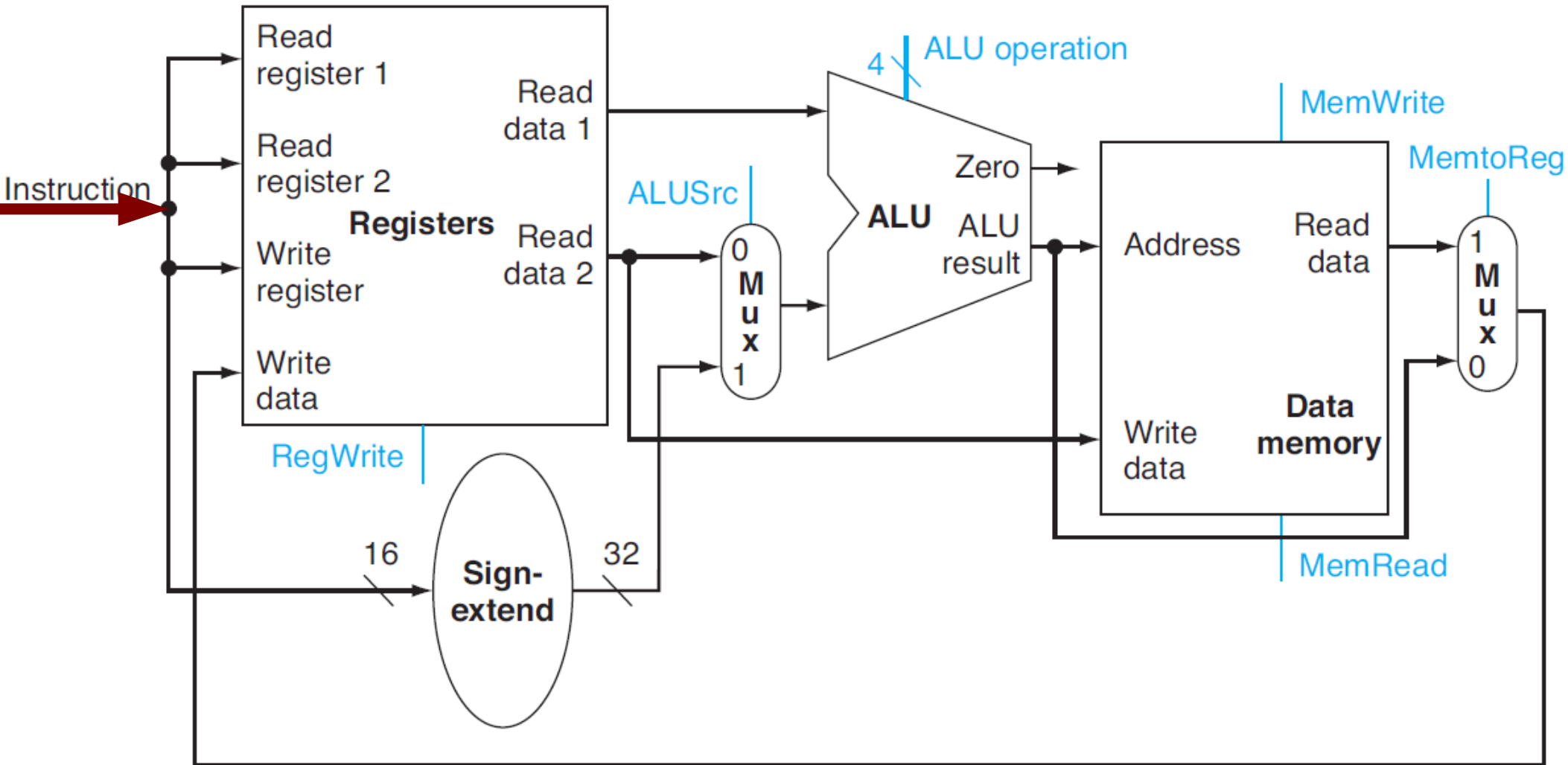


ADDI R1, R2, 13

# I Type Instruction – ADDI

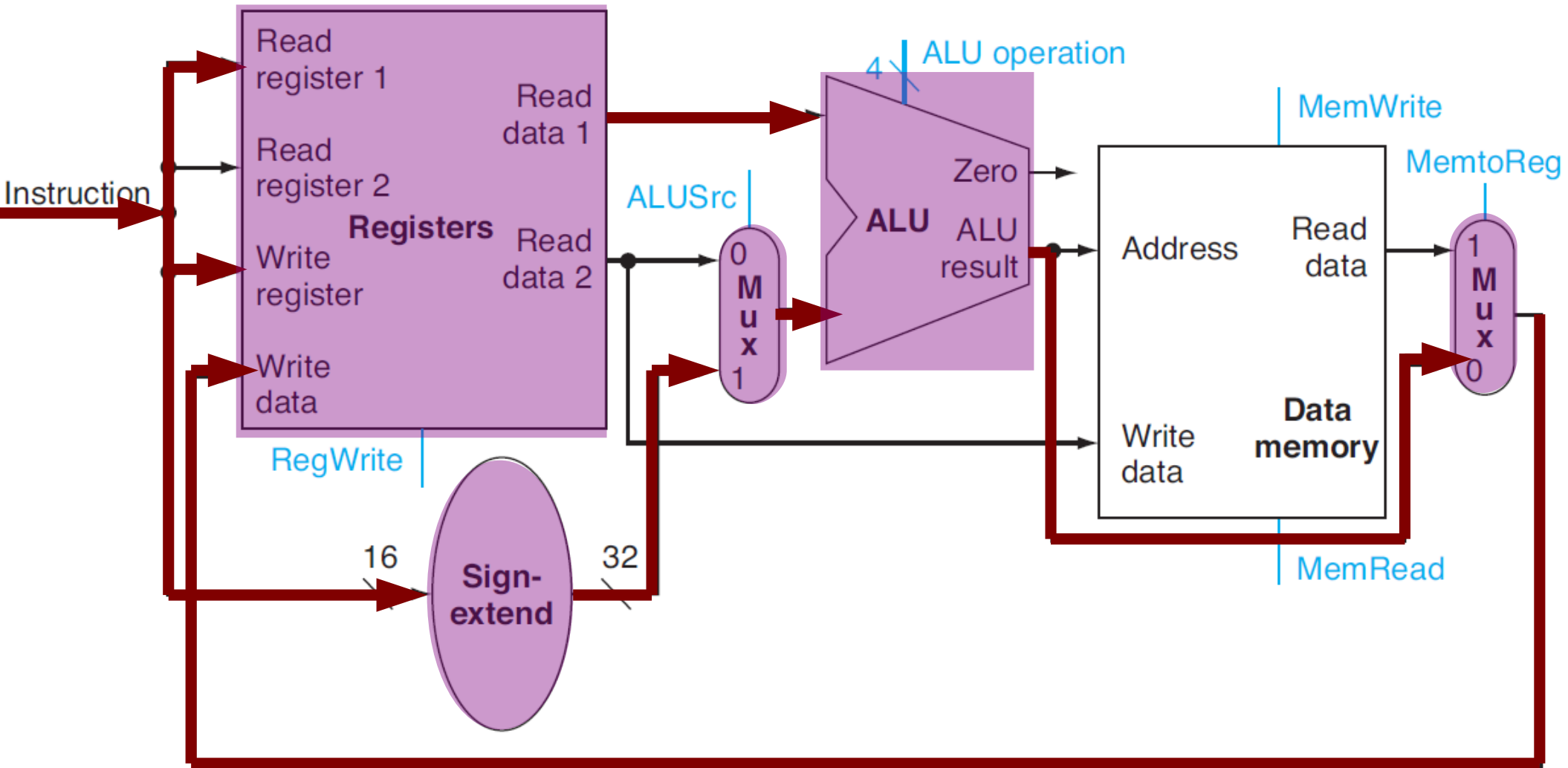


ADDI R1, R2, 13

# I Type Instruction – ADDI

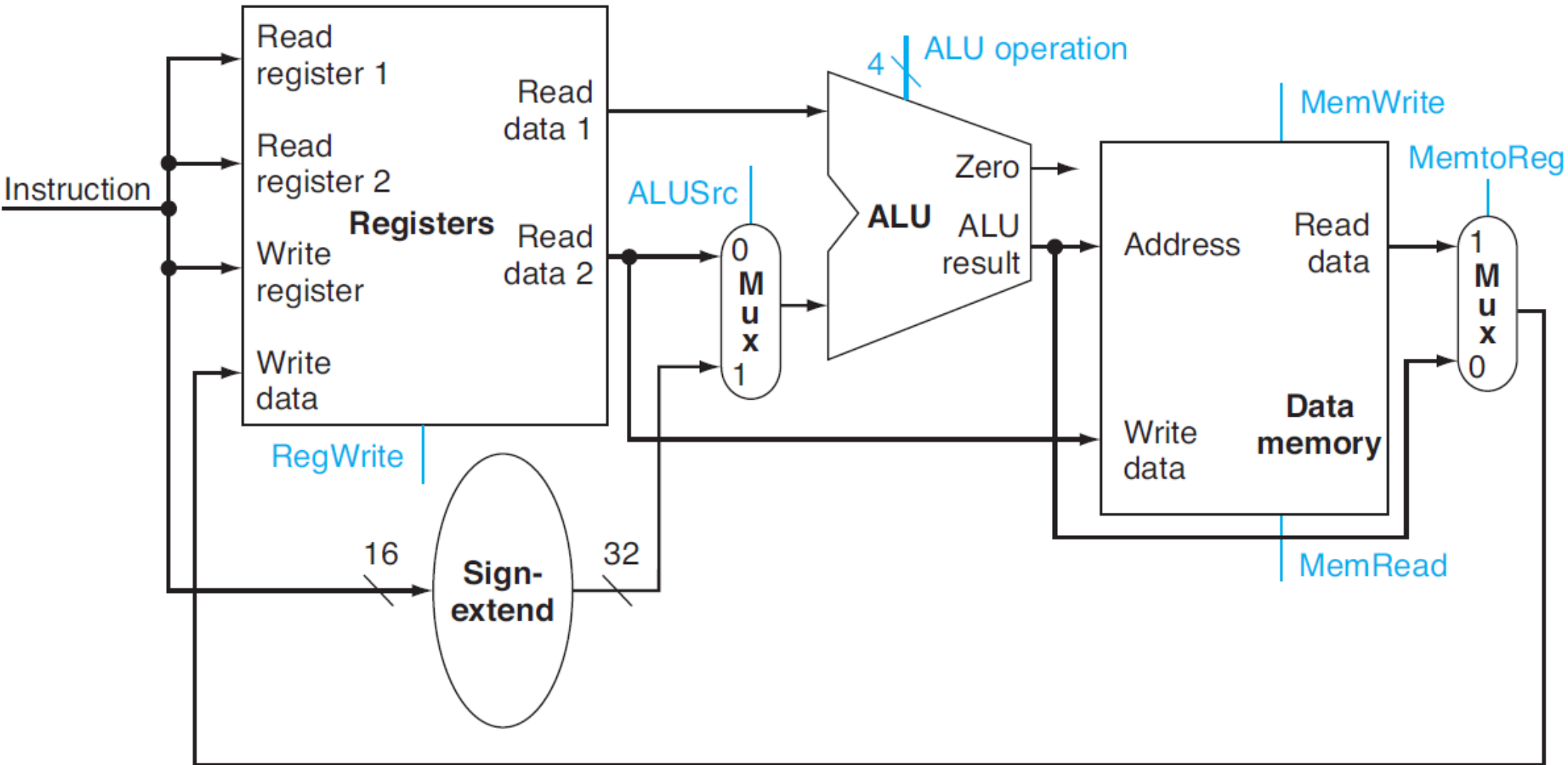

**Control Signals:**

# I Type Instruction – ADDI

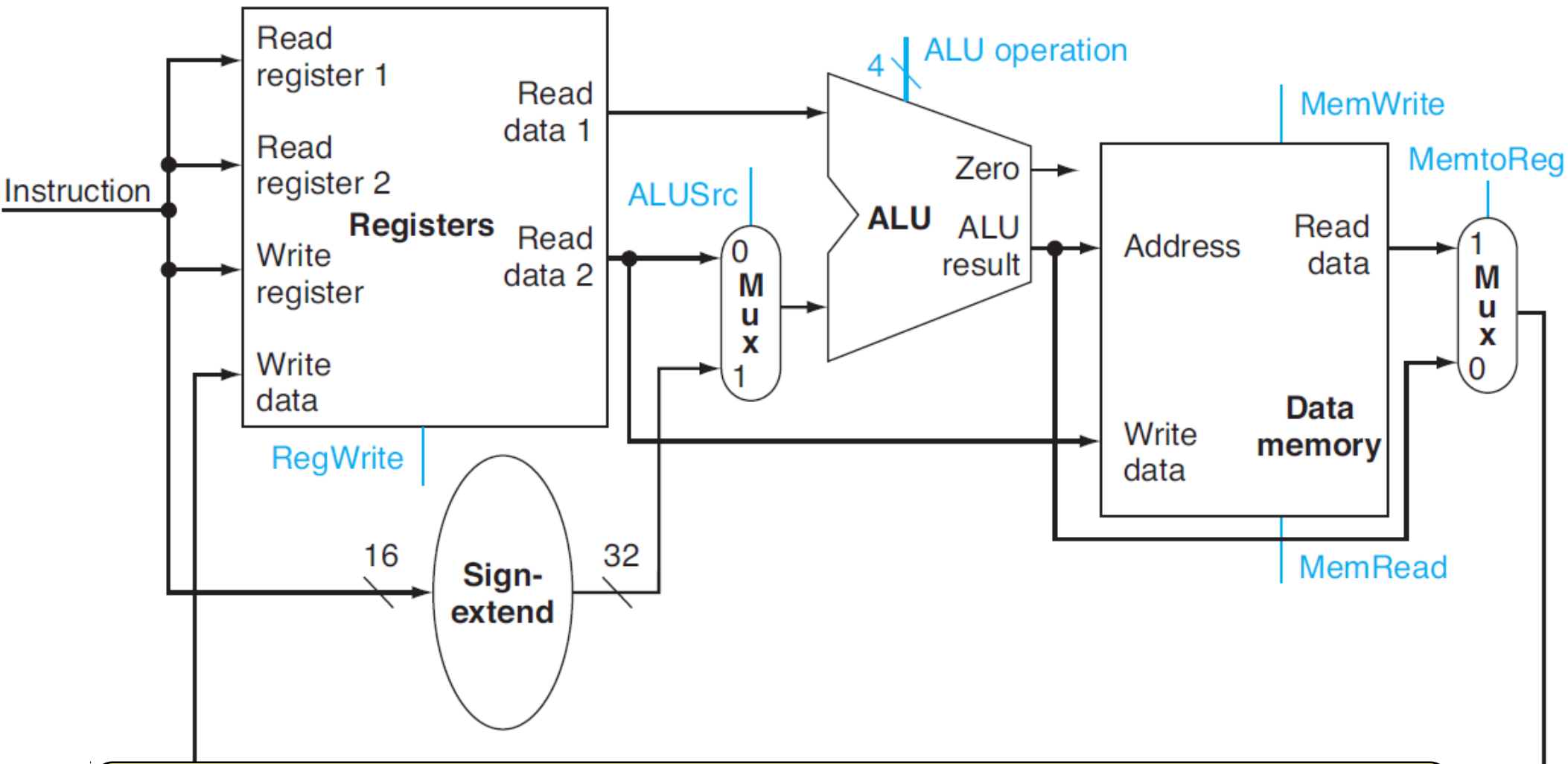

# BEQ – Actions

BEQ R1, R2, -16



# BEQ – Actions

- Read R1 and R2 from Register file
  - Send 1 and 2 to RF
  - RF reads contents of R1 and R2

BEQ R1, R2, -16

# BEQ – Actions

- Read R1 and R2 from Register file
  - Send 1 and 2 to RF
  - RF reads contents of R1 and R2
- Send to ALU; Ask it to Subtract

BEQ R1, R2, -16

# BEQ – Actions

- Read R1 and R2 from Register file
  - Send 1 and 2 to RF
  - RF reads contents of R1 and R2
- Send to ALU; Ask it to Subtract
- Read out Zero flag from ALU

# BEQ – Actions


- Read R1 and R2 from Register file
  - Send 1 and 2 to RF
  - RF reads contents of R1 and R2
- Send to ALU; Ask it to Subtract
- Read out Zero flag from ALU
- If Z flag == 0; then  $PC = (PC + 4) - 16$

BEQ R1, R2, -16

# BEQ – Actions

- Read R1 and R2 from Register file
  - Send 1 and 2 to RF
  - RF reads contents of R1 and R2
- Send to ALU; Ask it to Subtract
- Read out Zero flag from ALU
- If Z flag == 0; then  $PC = (PC + 4) - 16$
- Else if Z flag == 1; then  $PC = PC + 4$


# Branches – Elements

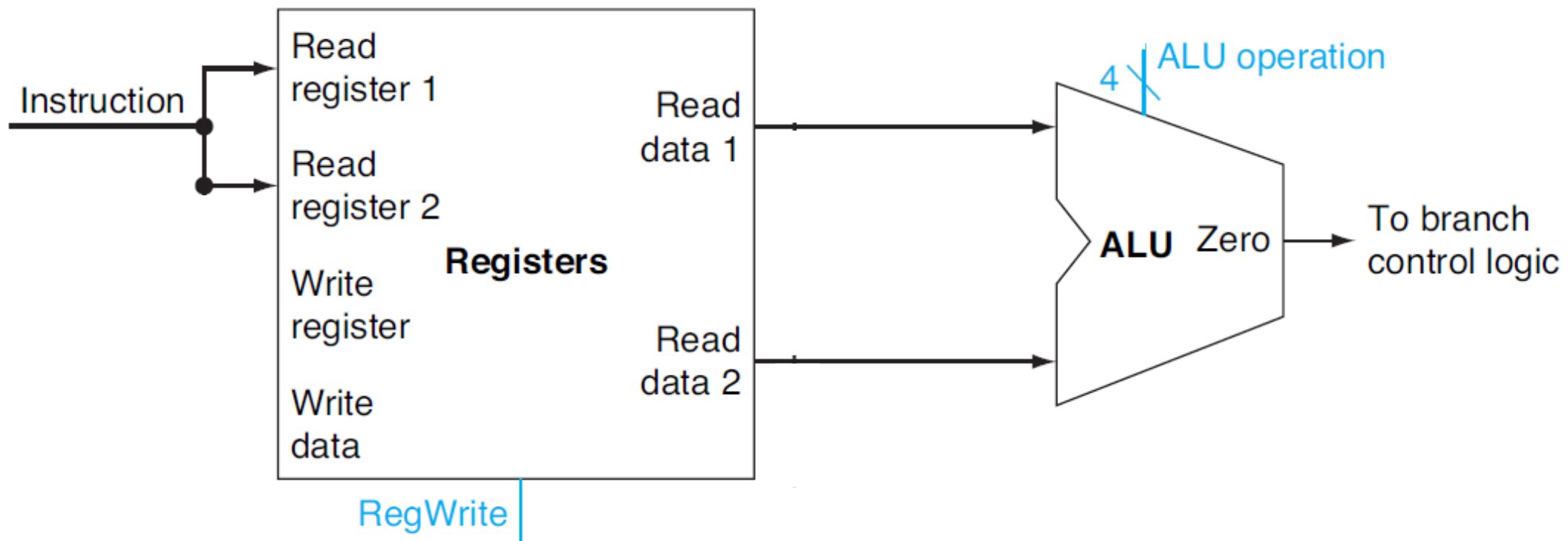


BEQ R1, R2, LABEL

BEQ R1, R2, -16

# Branches – Elements

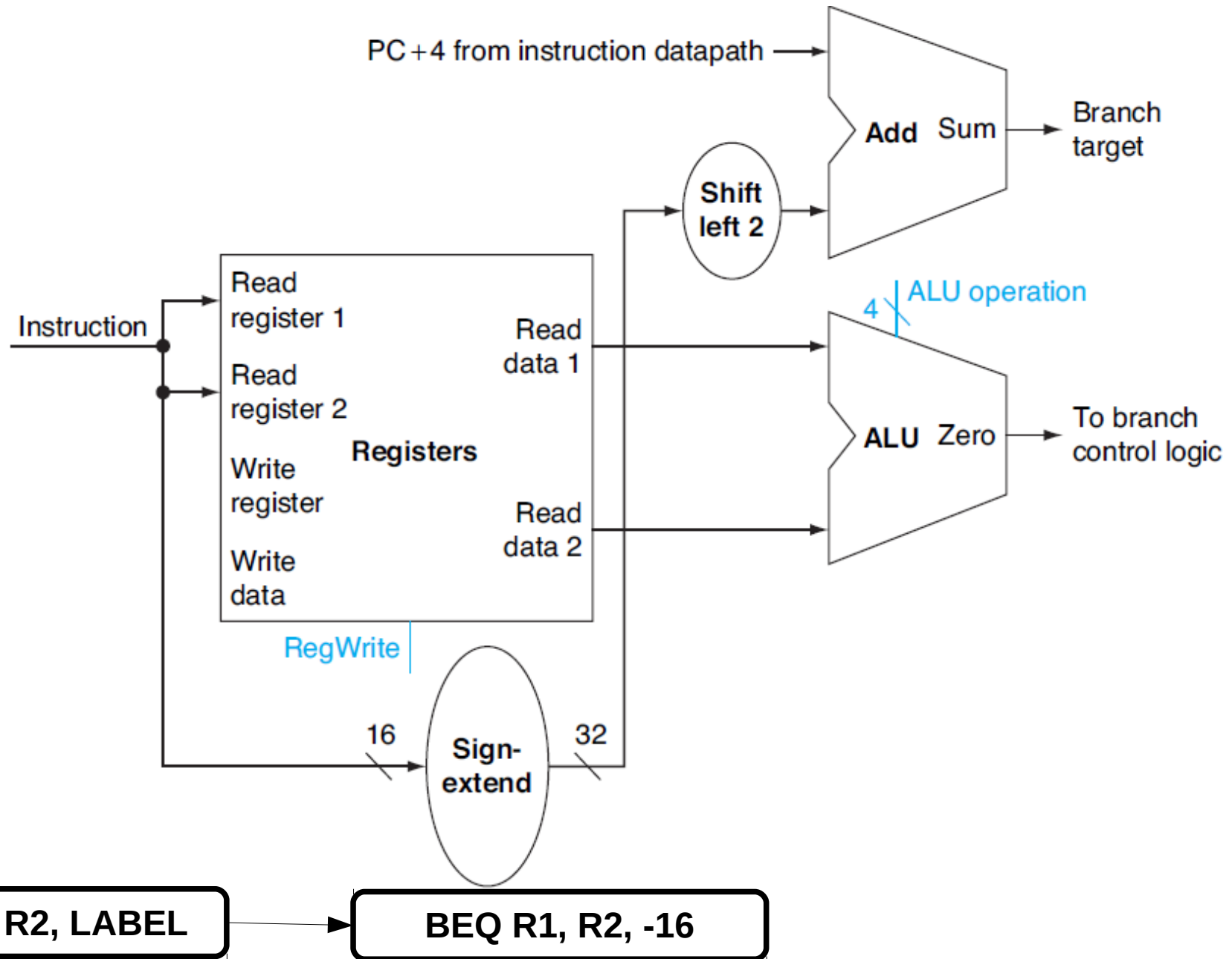


# The MIPS Datapath

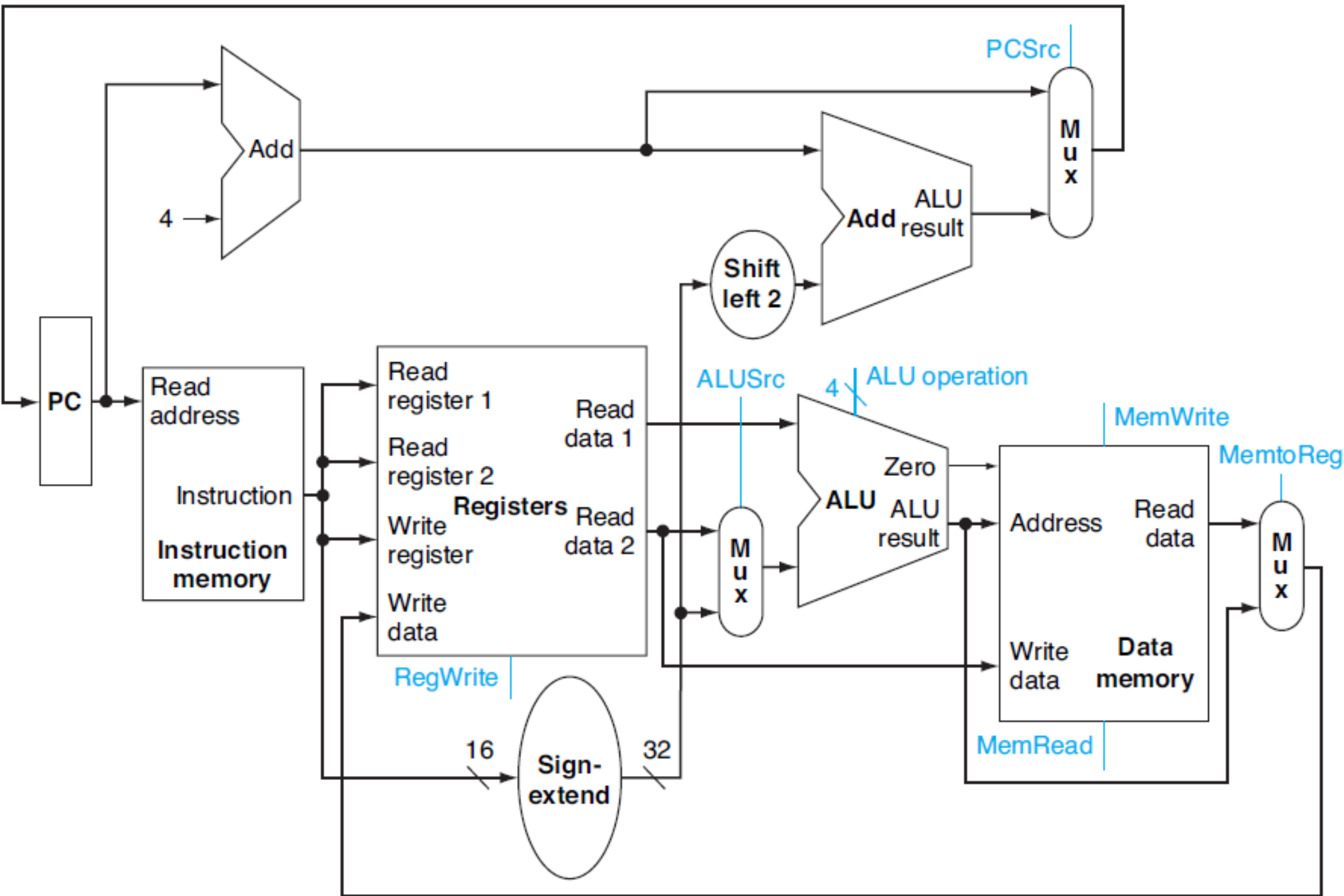





# The MIPS Datapath – BEQ

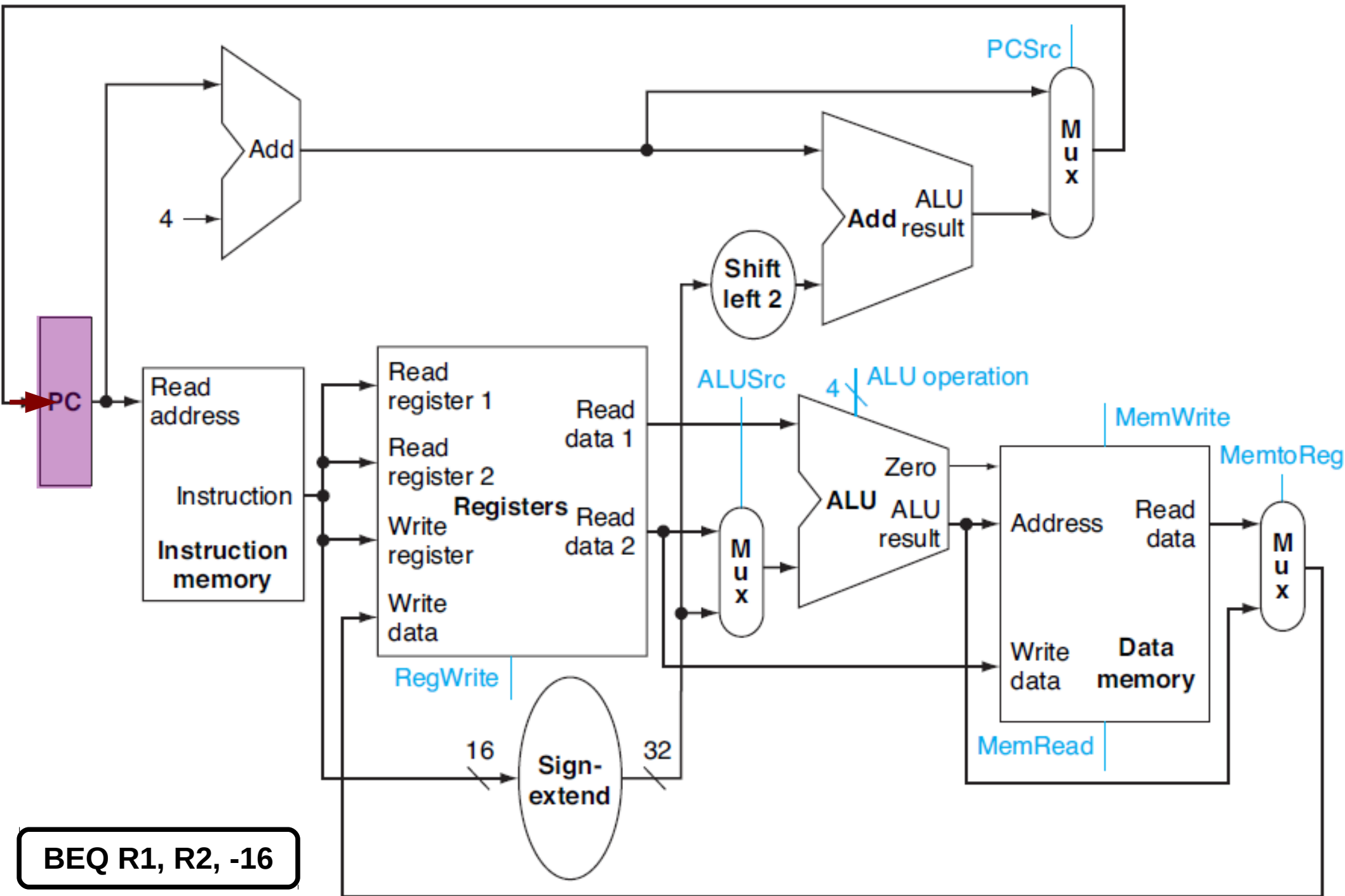


# The MIPS Datapath – BEQ

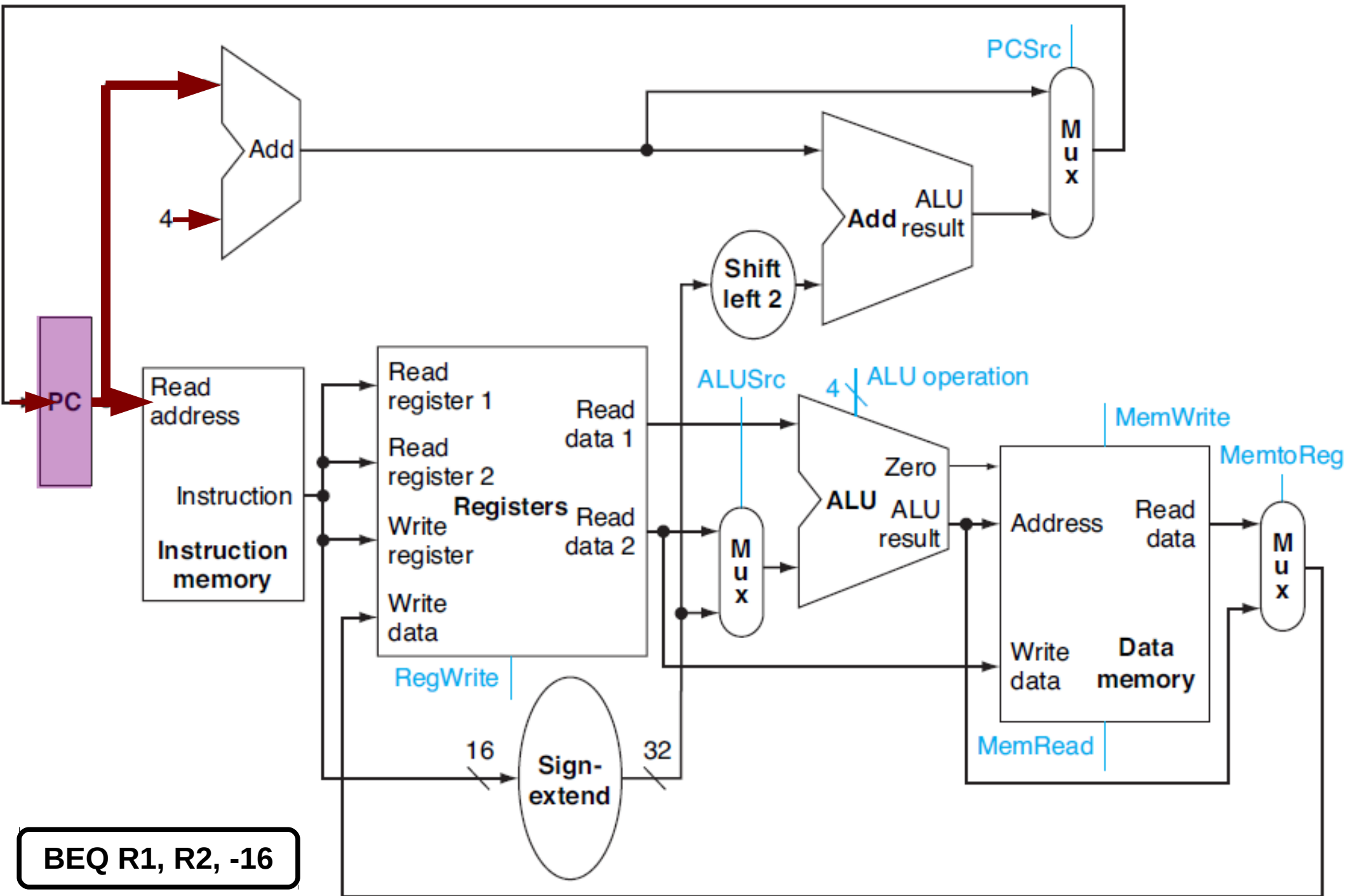


# The MIPS Datapath – BEQ

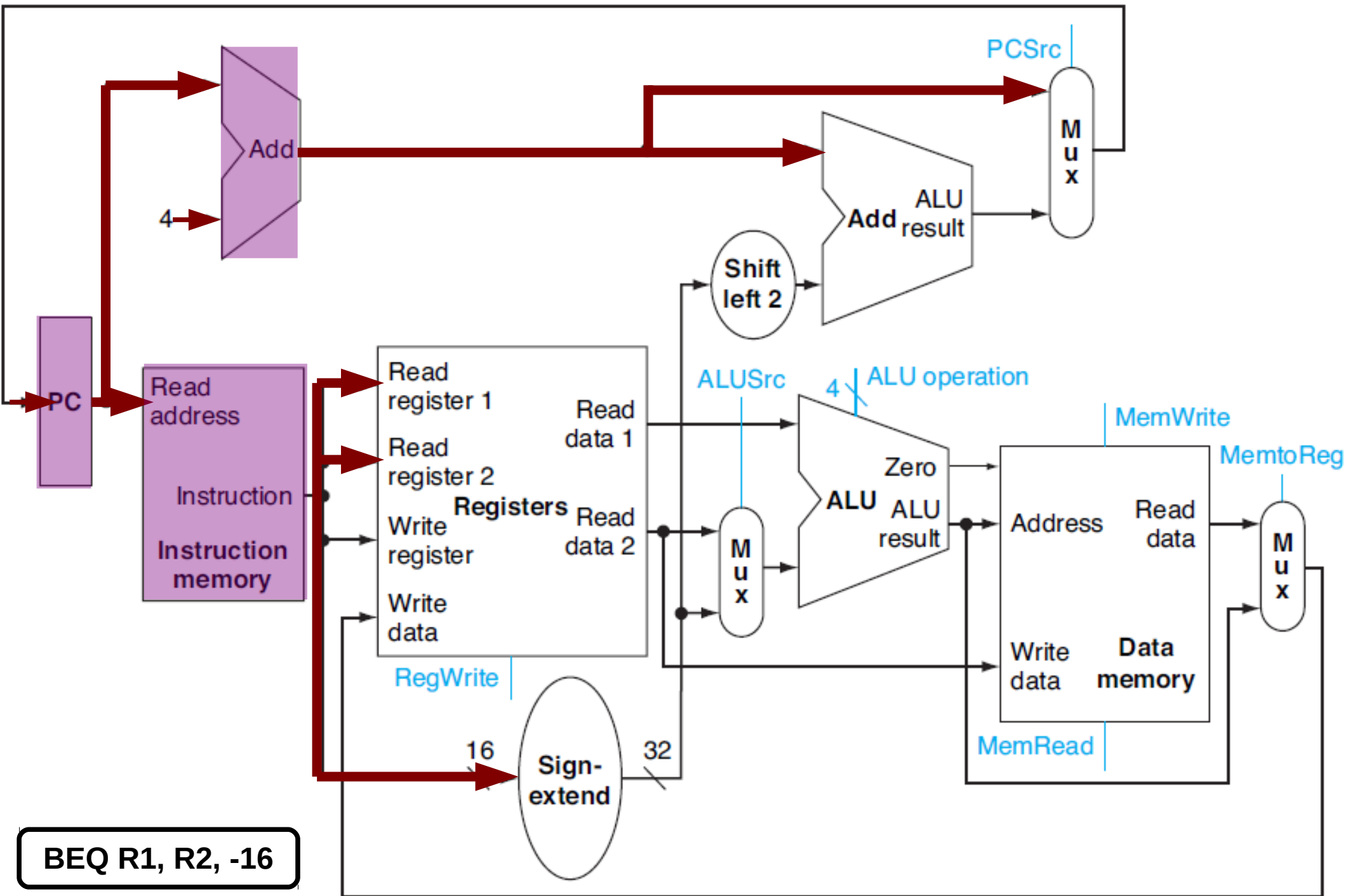


# The MIPS Datapath – BEQ

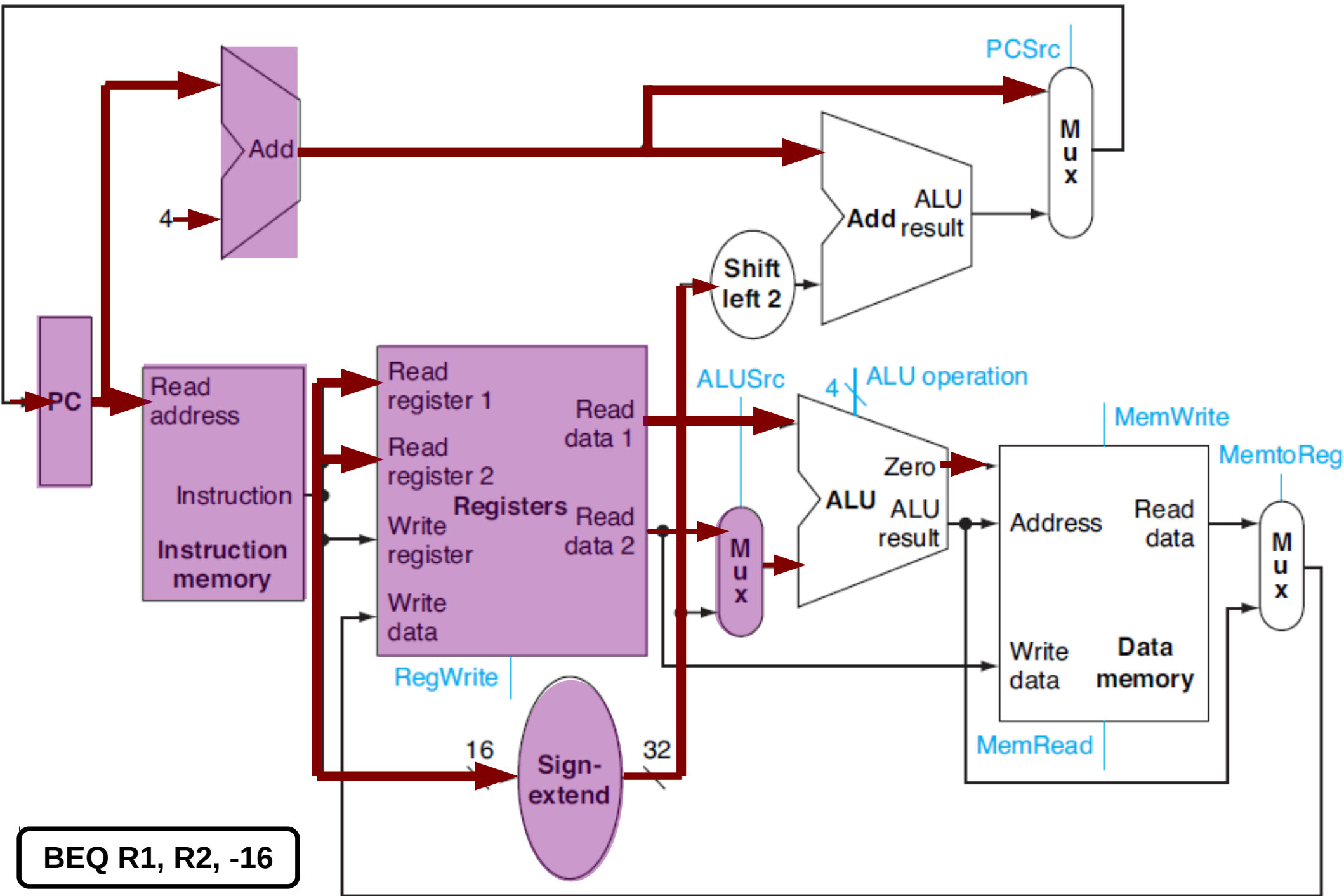


# The MIPS Datapath – BEQ

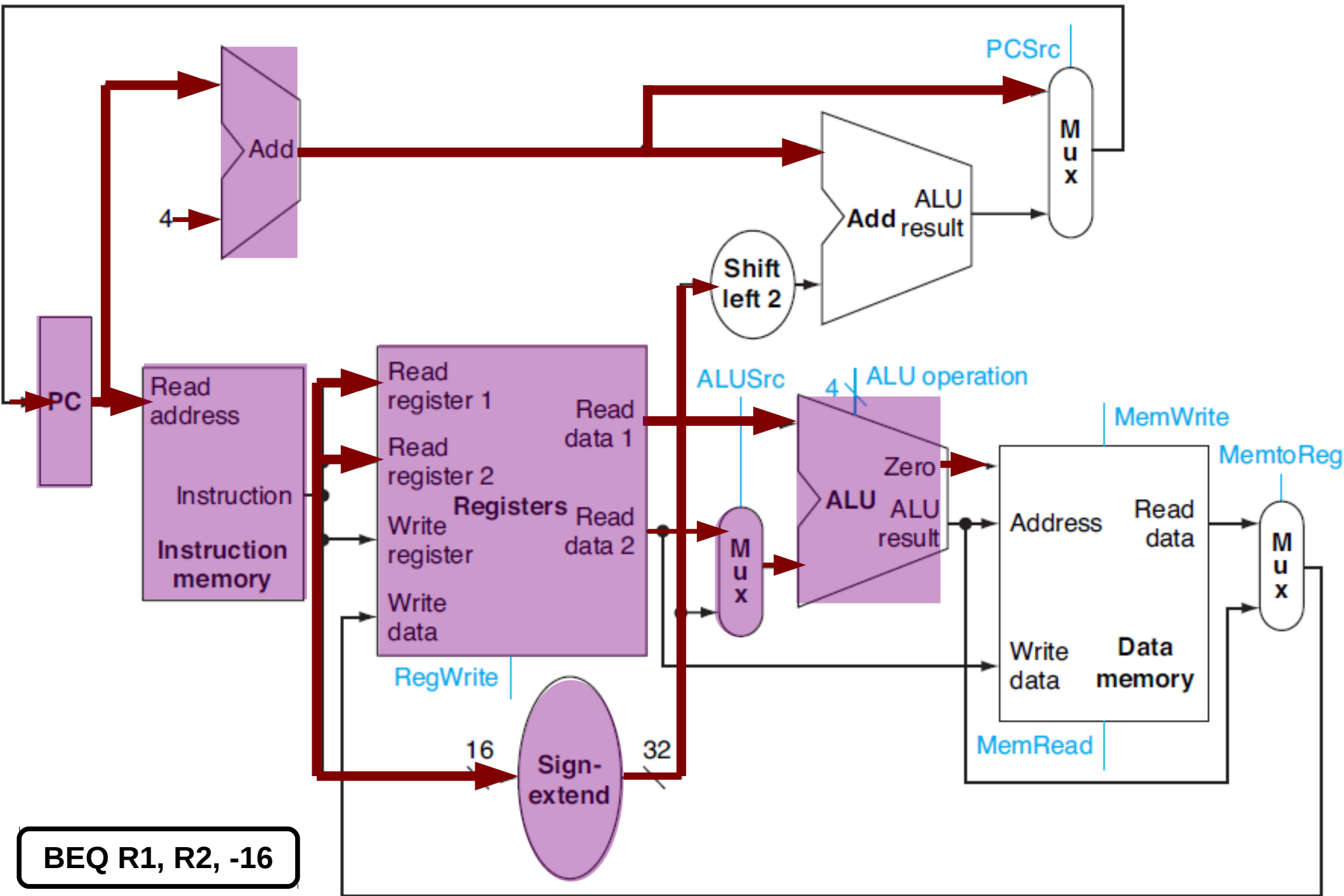


# The MIPS Datapath – BEQ

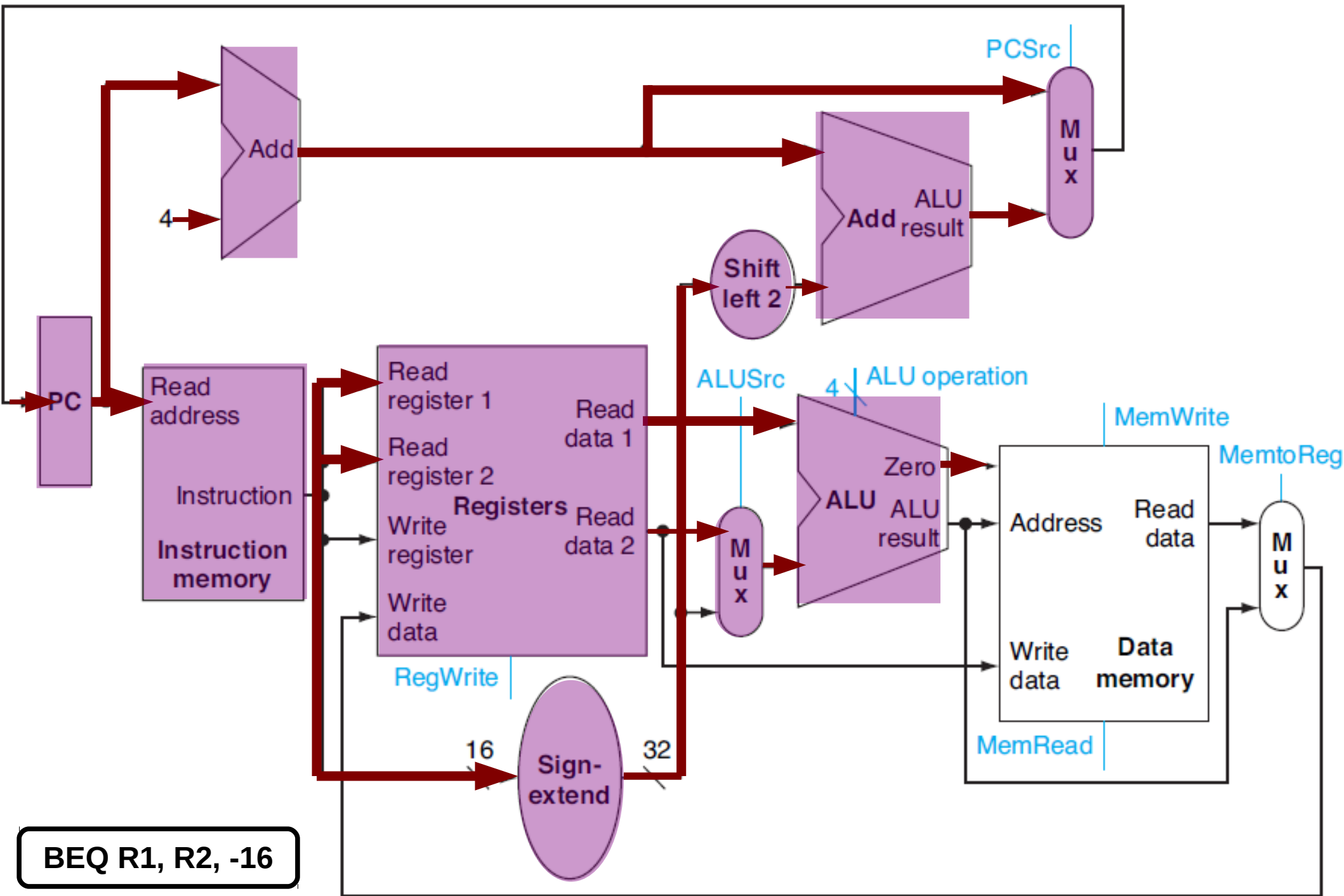

# The MIPS Datapath – BEQ

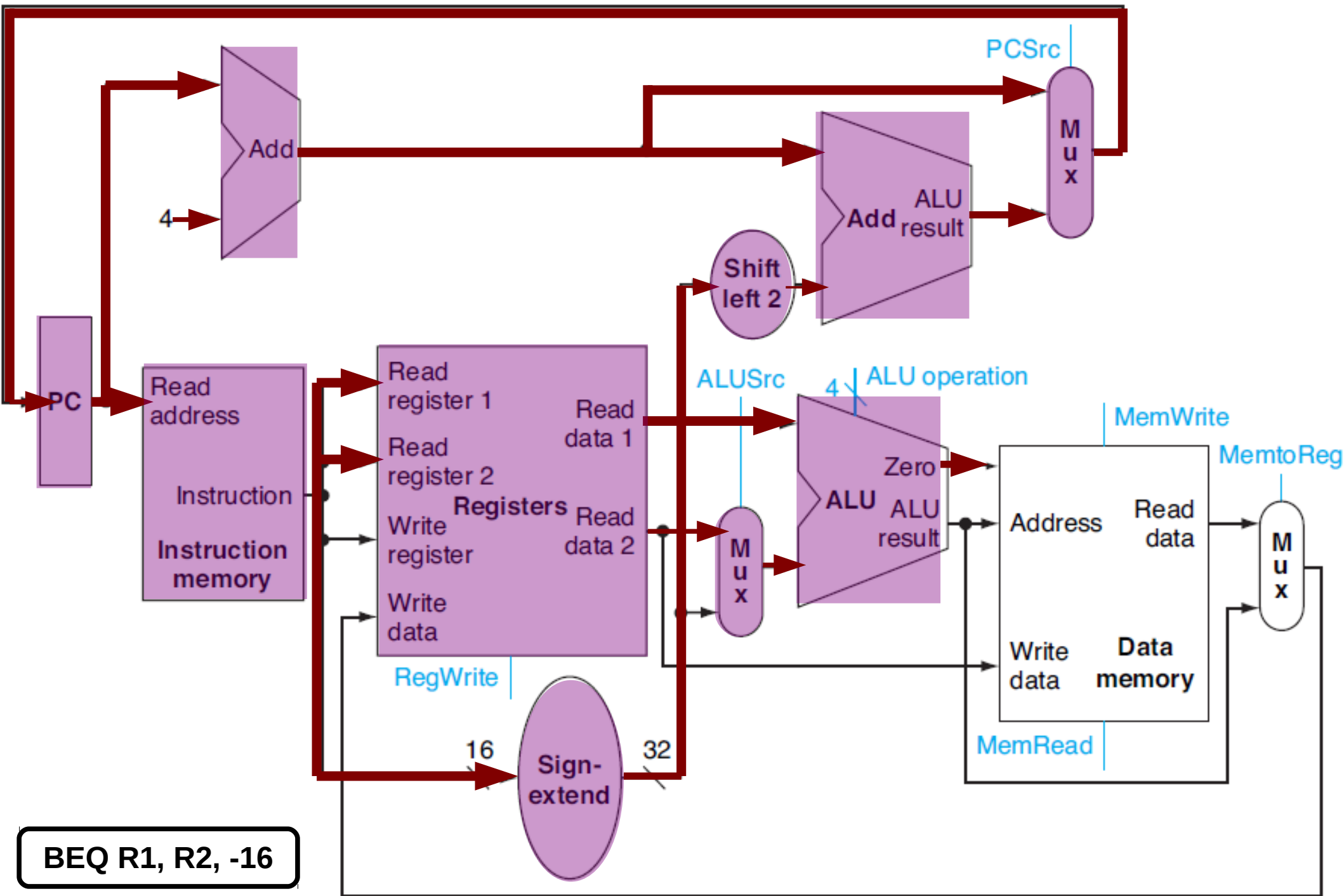


# The MIPS Datapath – BEQ

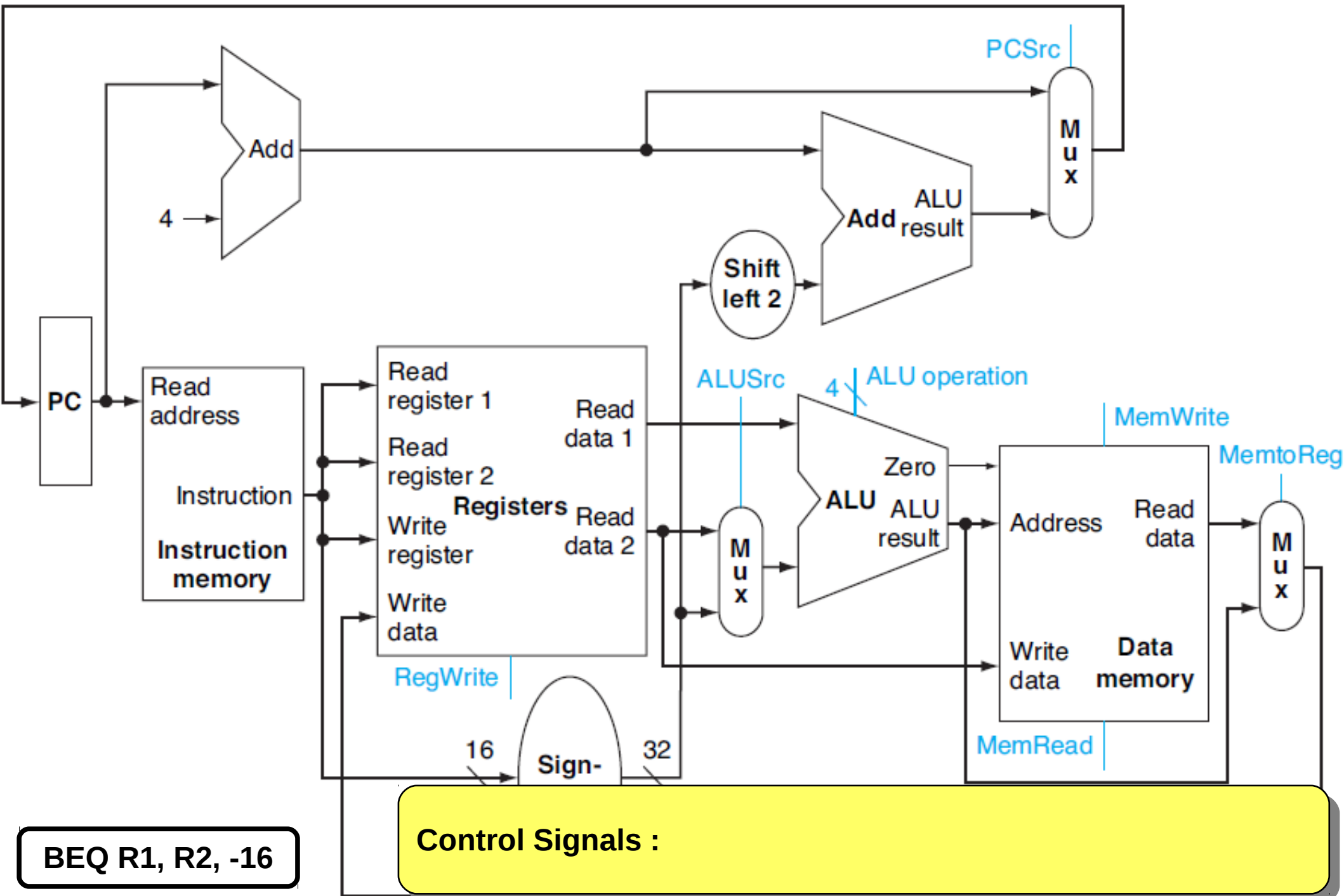




# The MIPS Datapath – BEQ

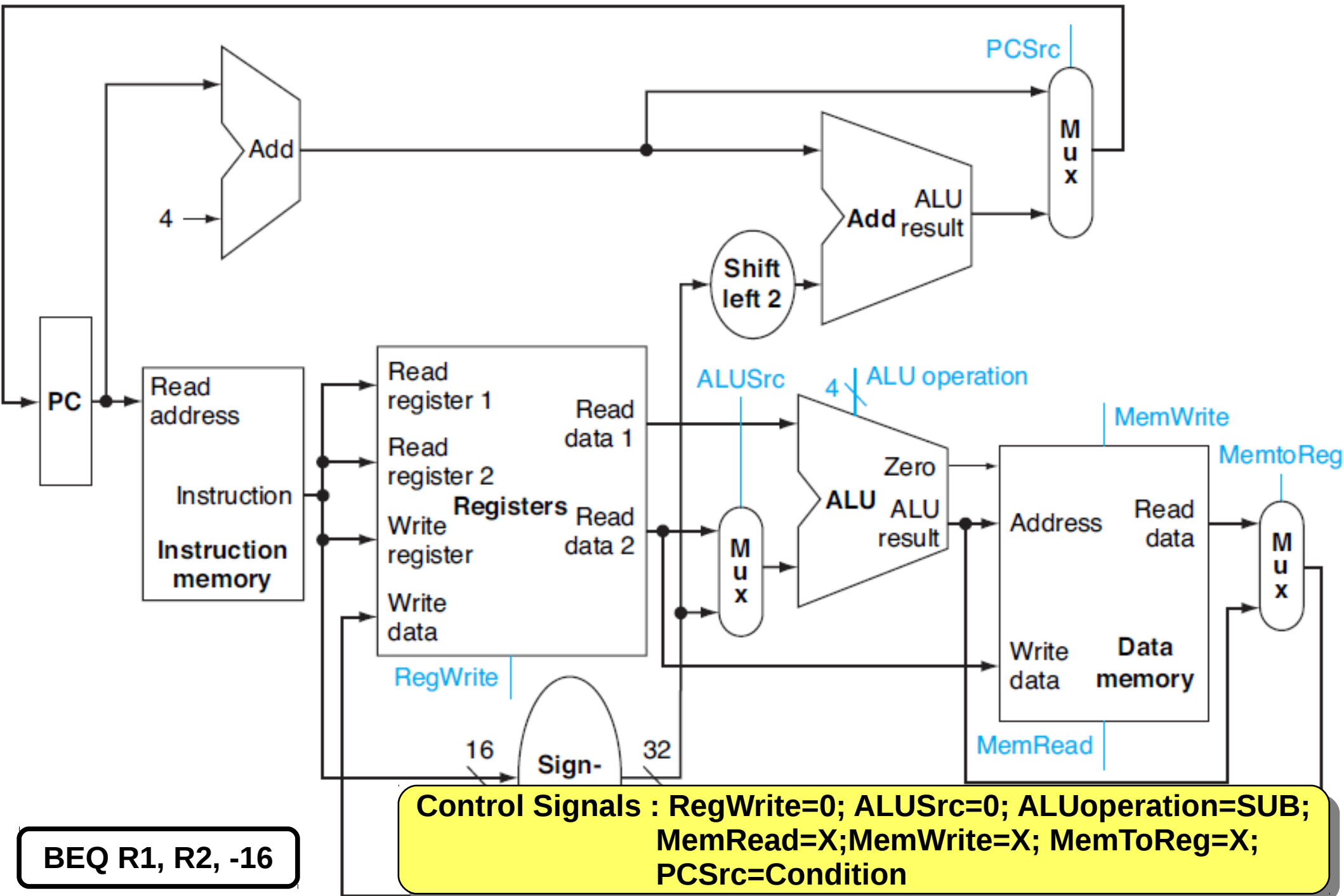

# MIPS Datapath and Control Lines

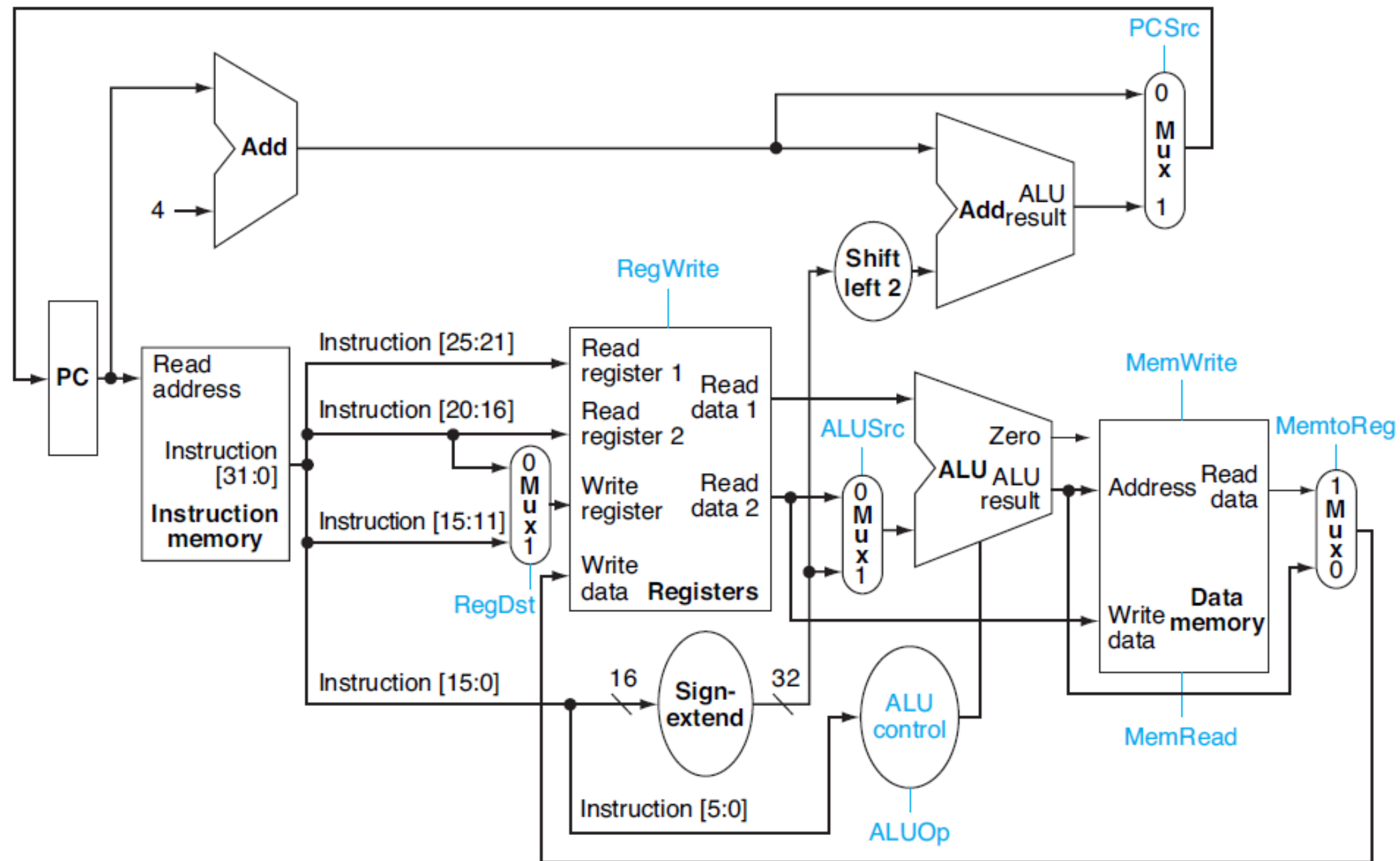

# Module Outline


- MIPS datapath implementation
  - Register File, Instruction memory, Data memory
- Instruction interpretation and execution.
- Combinational control
- Assignment: Datapath design and Control Unit design using SystemC.

# Backup

# ALU Instructions

- ALU instructions (R type), Memory Transfer (effective address calculation), Branches (BEQ)


- R-type

 

**OP rd, rs, rt**

**op:** Opcode (class of instruction). Eg. ALU  
**funct:** Which subunit of the ALU to activate?

- I-type

 

**OP rt, rs, IMM**


# ALU Instructions

- ALU instructions (R type), Memory Transfer (effective address calculation), Branches (BEQ)
- Identified by Opcode fields and Funct fields

# ALU Instructions

- ALU instructions (R type), Memory Transfer (effective address calculation), Branches (BEQ)


- R-type

 

**OP rd, rs, rt**

**op:** Opcode (class of instruction). Eg. ALU  
**funct:** Which subunit of the ALU to activate?

- I-type

 

**OP rt, rs, IMM**