

# M3 – ALU Design

# Module Outline

- Integer Arithmetic
  - Adder, Subtractor, Multiplier, Divider
- Arithmetic and Logical Unit Design
  - ALU Design in SystemC

# Multiplication

- Start with long-multiplication approach

$$\begin{array}{r} 1000 \\ \times 1001 \\ \hline 1000 \\ 0000 \\ 0000 \\ 1000 \\ \hline 1001000 \end{array}$$


# Multiplication

- Start with long-multiplication approach

$$\boxed{1000} \times \boxed{1001}$$

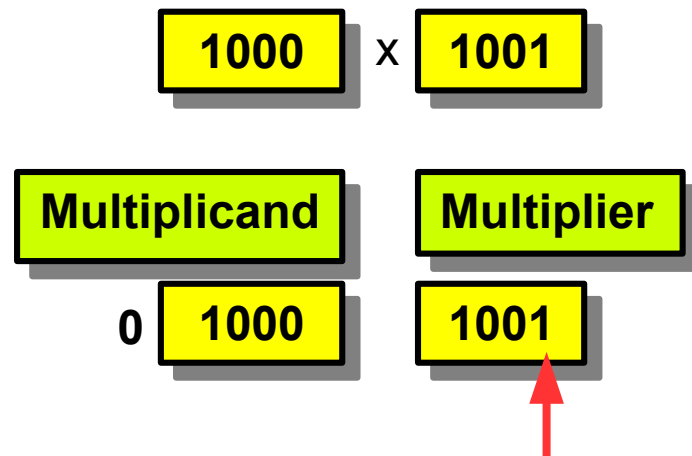
# Multiplication

- Start with long-multiplication approach



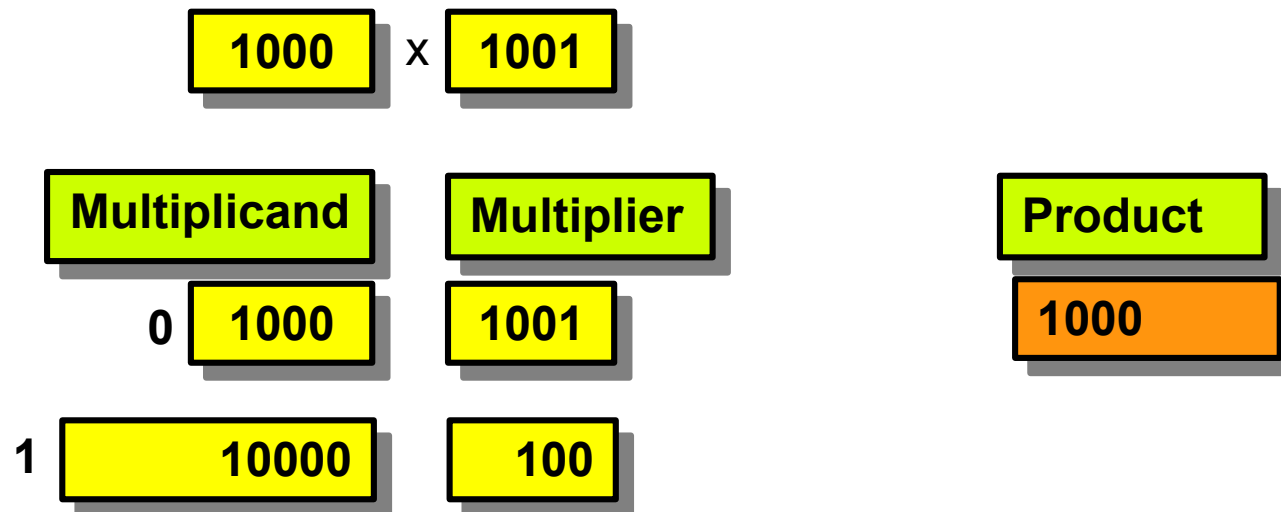
# Multiplication

- Start with long-multiplication approach


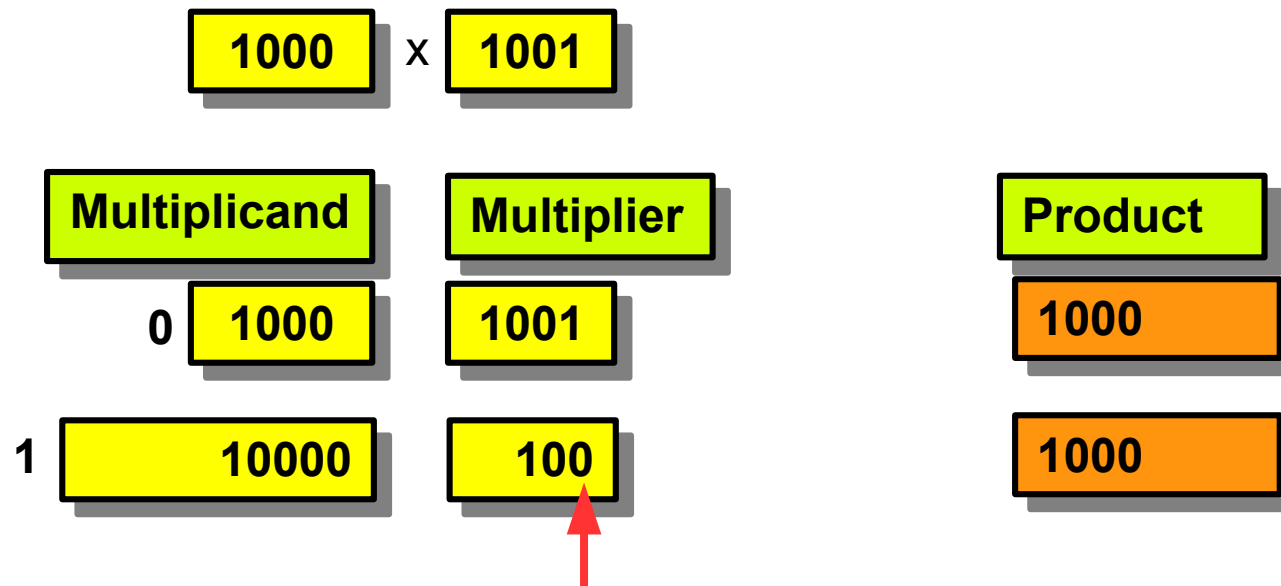
# Multiplication

- Start with long-multiplication approach



# Multiplication


- Start with long-multiplication approach

	1000	x	1001	
	<b>Multiplicand</b>		<b>Multiplier</b>	<b>Product</b>
0	1000		1001	1000
1	10000		100	1000
2	100000		10	1000



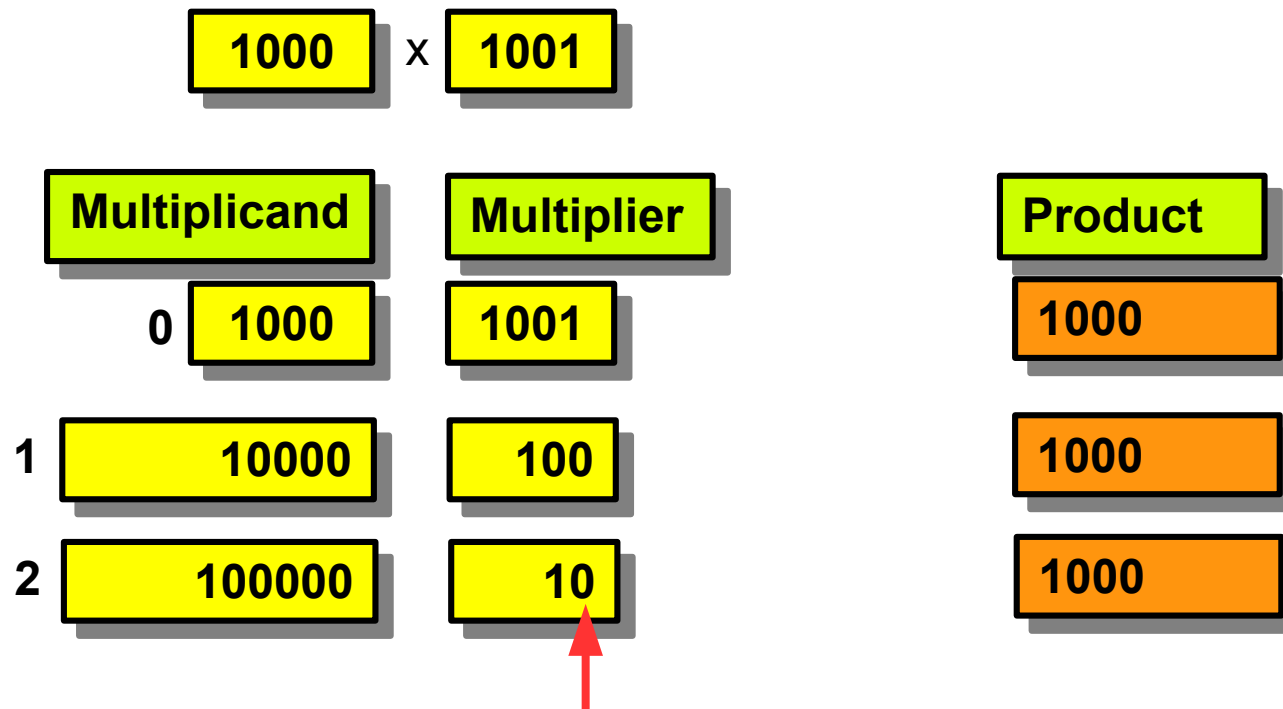
# Multiplication

- Start with long-multiplication approach


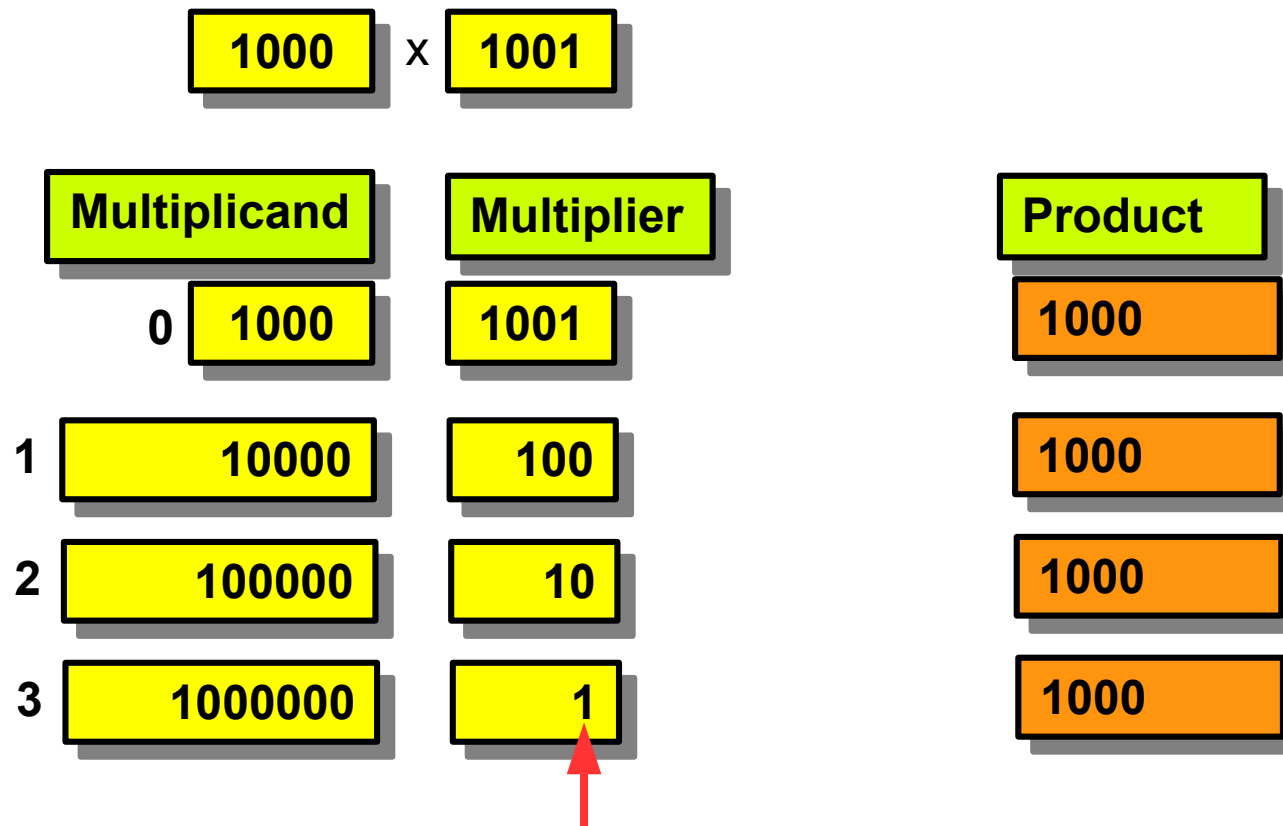
# Multiplication

- Start with long-multiplication approach



# Multiplication

- Start with long-multiplication approach

1000		x	1001		
Multiplicand		Multiplier		Product	
0	1000	1001		1000	
1	10000	100		1000	
2	100000	10		1000	
3	1000000	1		1001000	

# Multiplication

- Start with long-multiplication approach


	1000	x	1001	
	<b>Multiplicand</b>		<b>Multiplier</b>	<b>Product</b>
0	1000		1001	1000
1	10000		100	1000
2	100000		10	1000
3	1000000		1	1001000
4	10000000			1001000

# Multiplication Hardware




Start


# Multiplication Hardware

 

# Multiplication Hardware

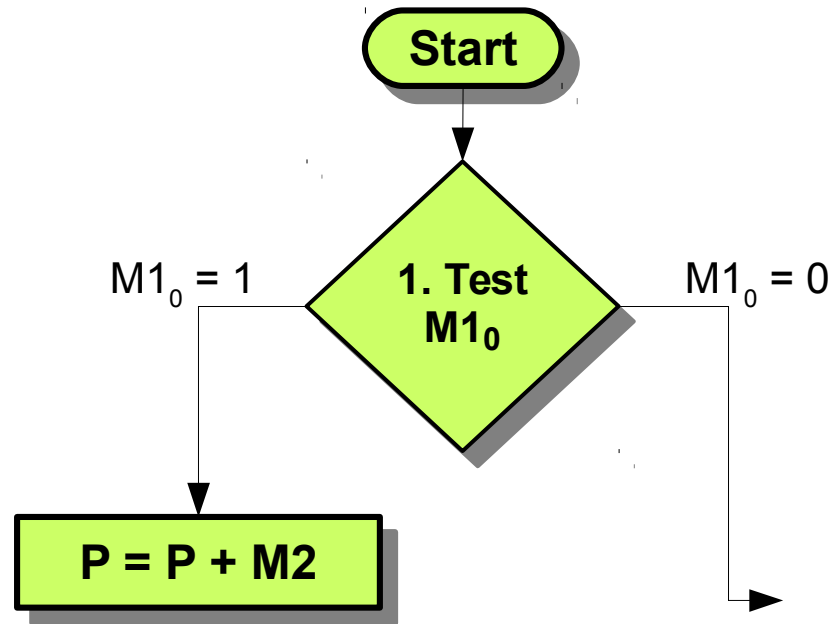


# Multiplication Hardware

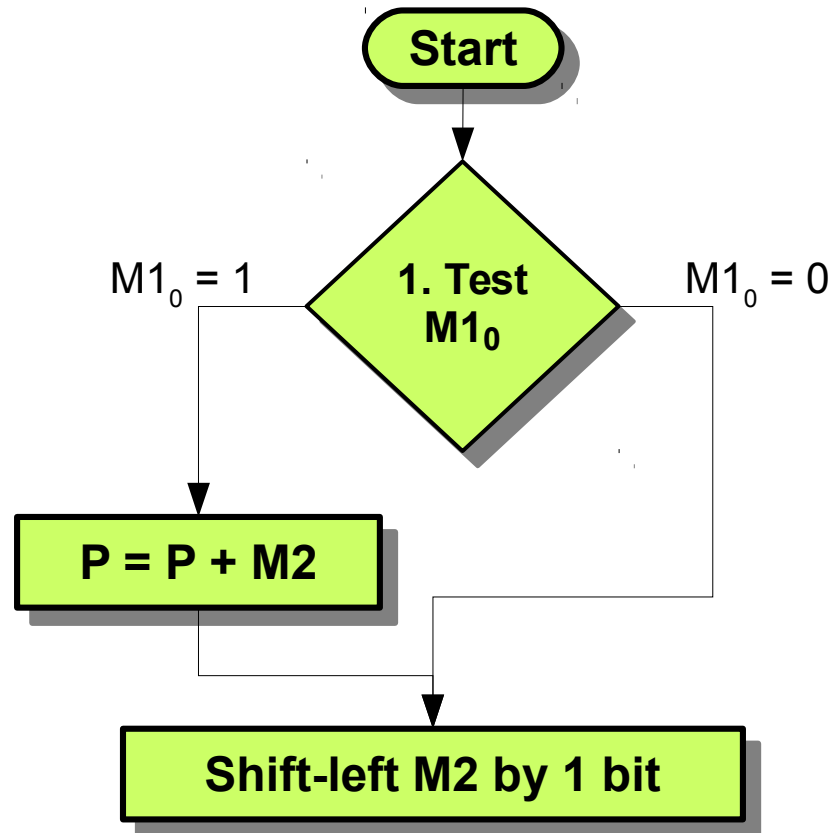





# Multiplication Hardware

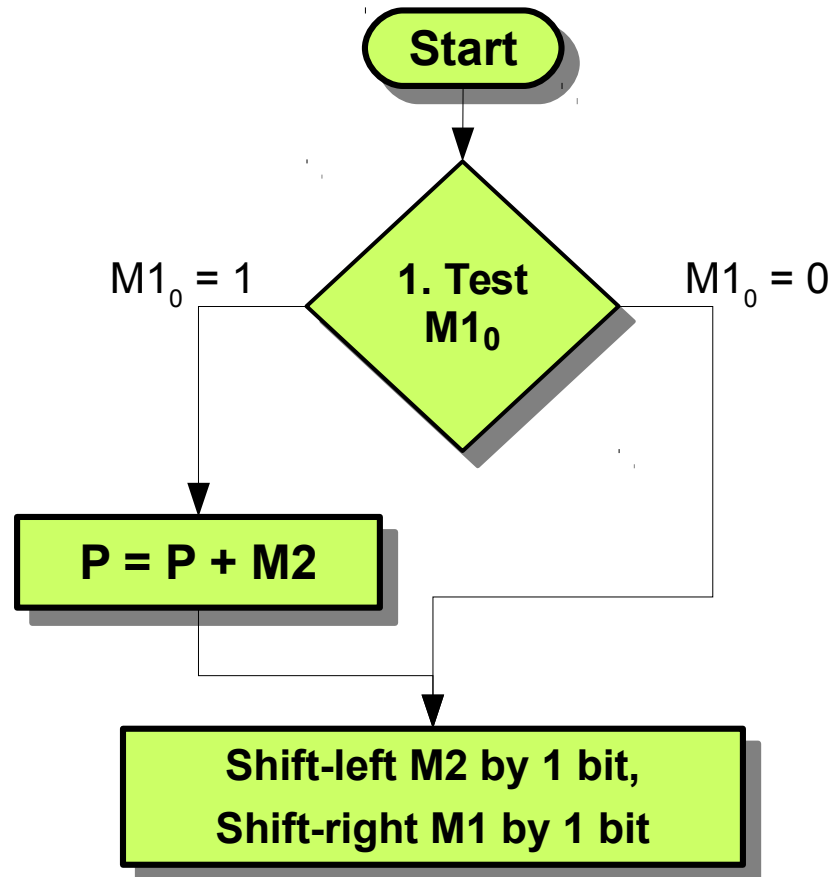


# Multiplication Hardware

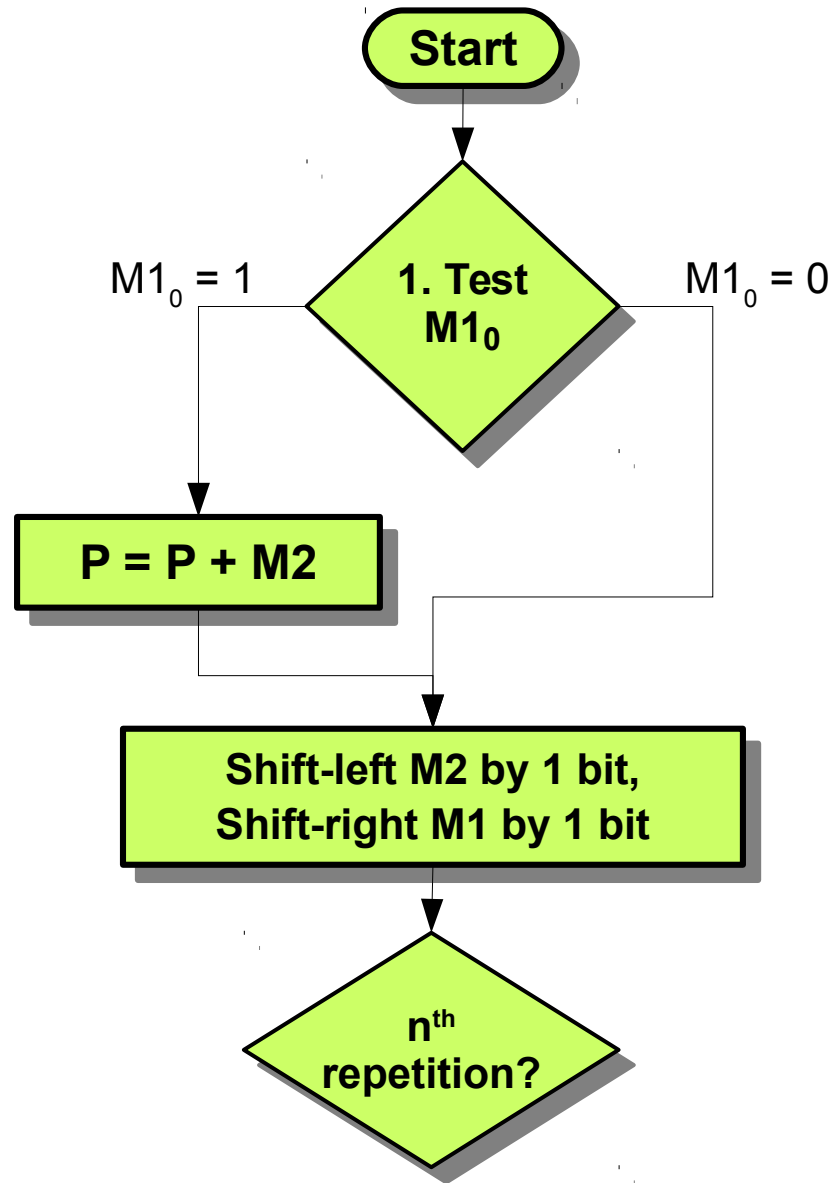


# Multiplication Hardware

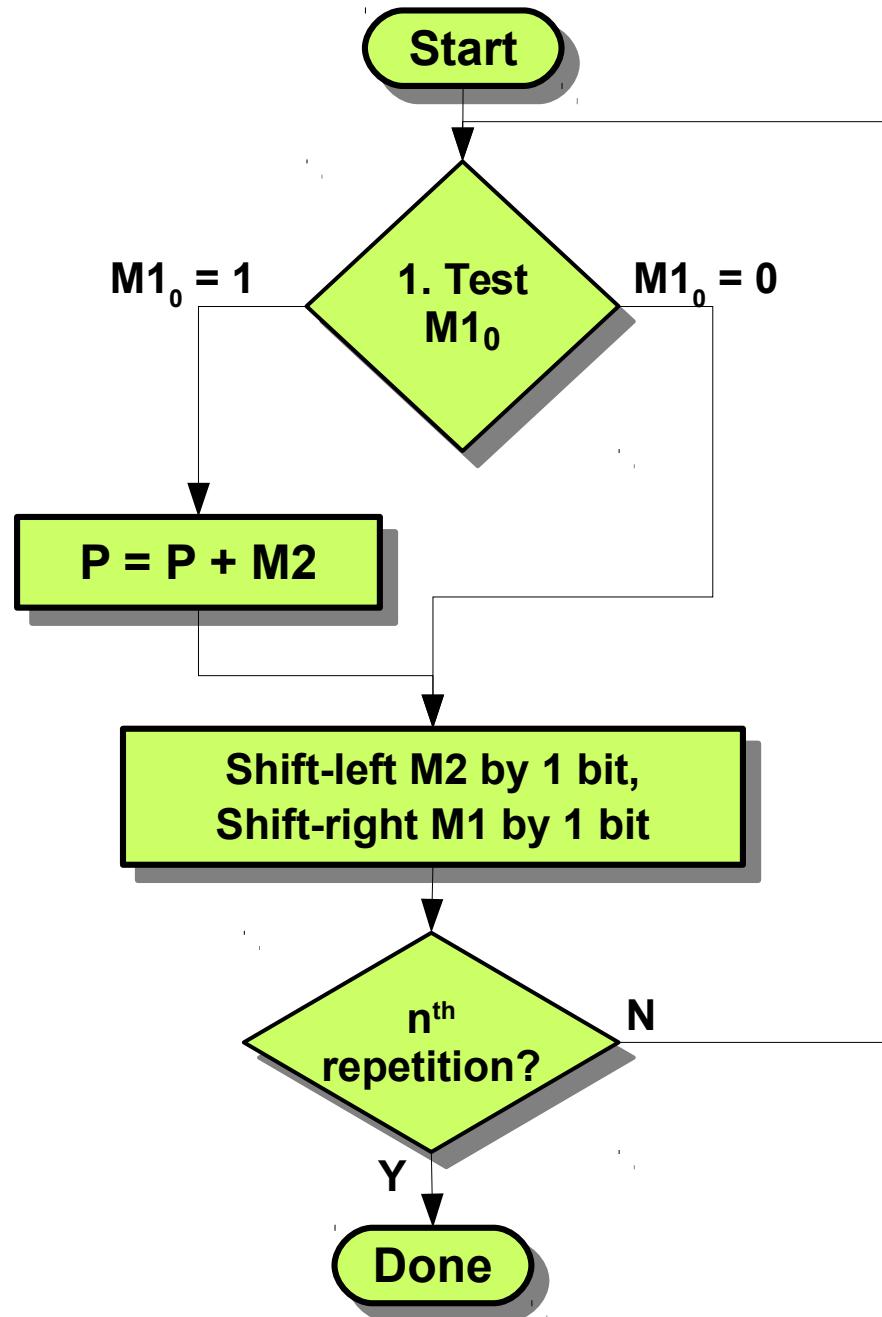


# Multiplication Hardware

 


# Multiplication Hardware

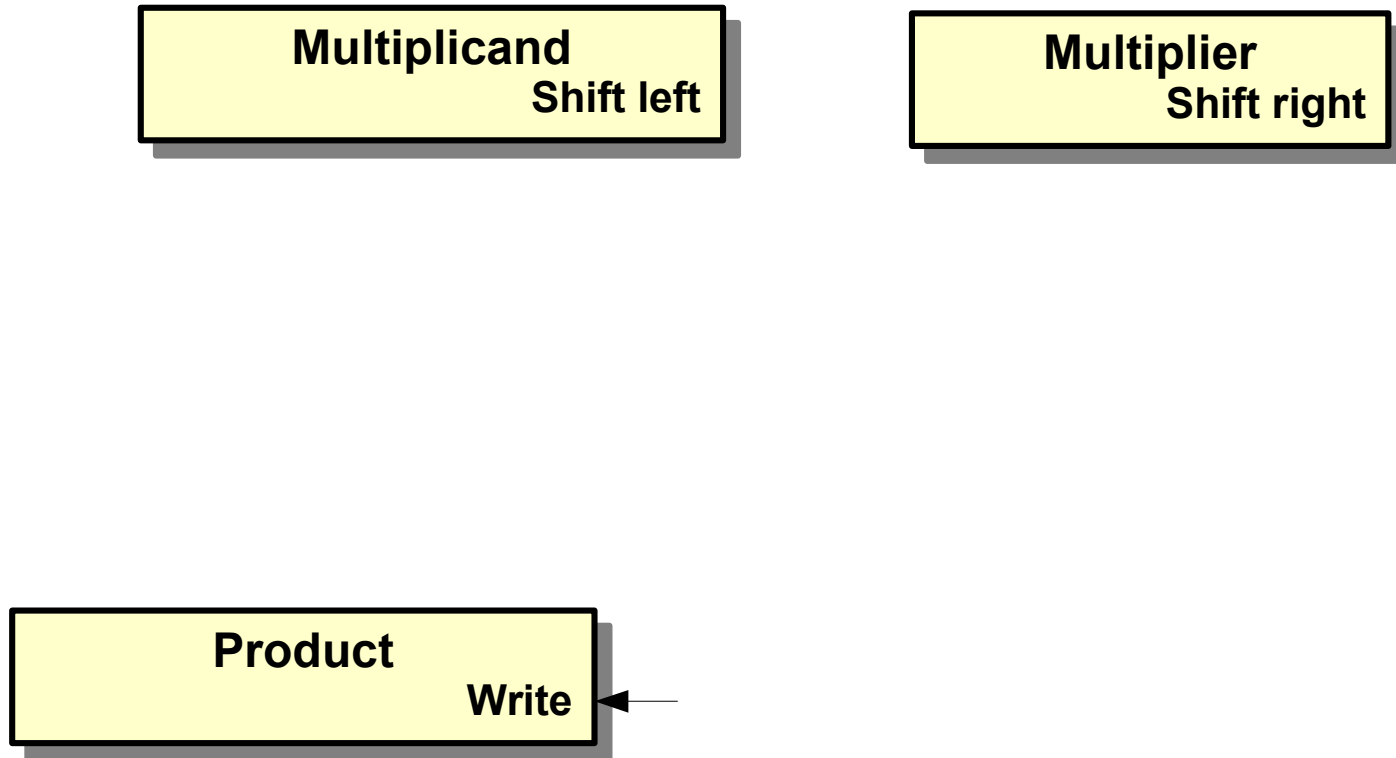


# Multiplication Hardware

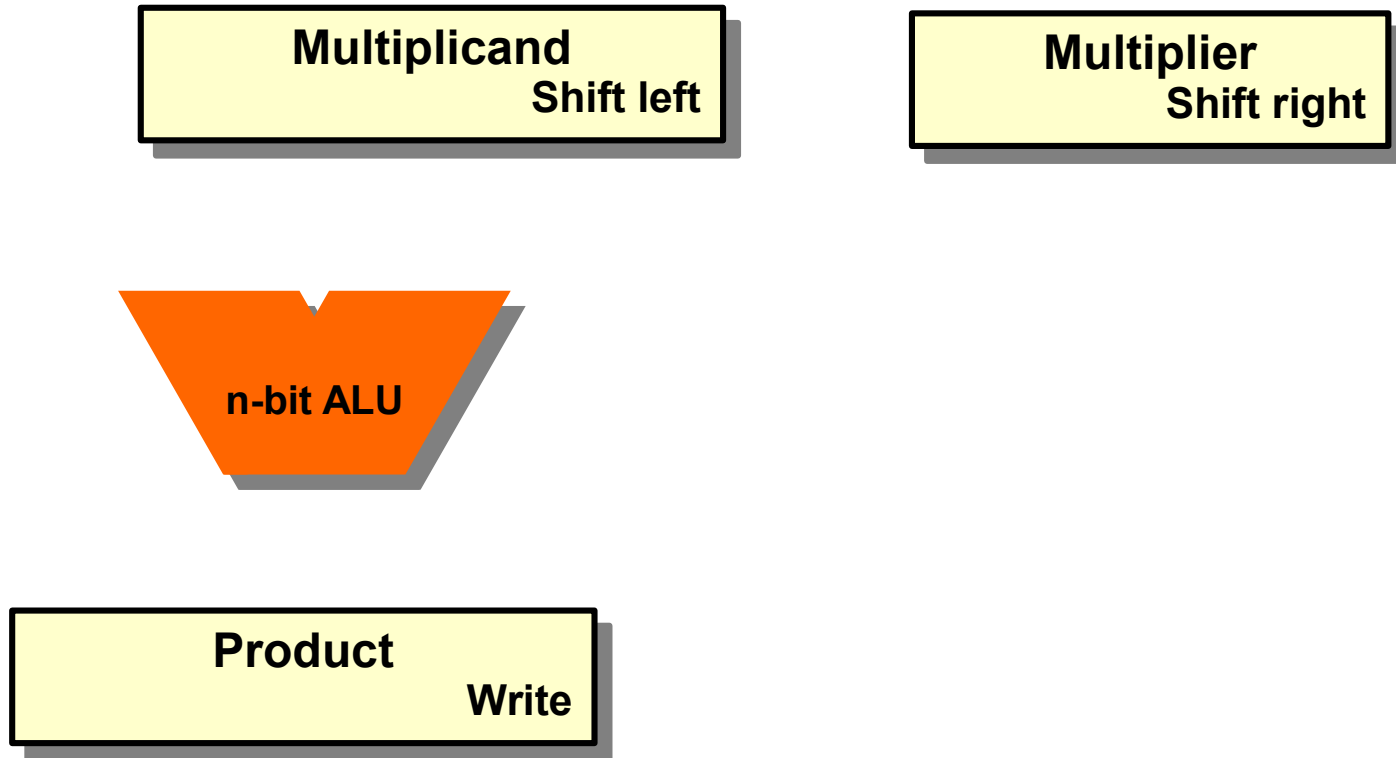

# Multiplication Hardware

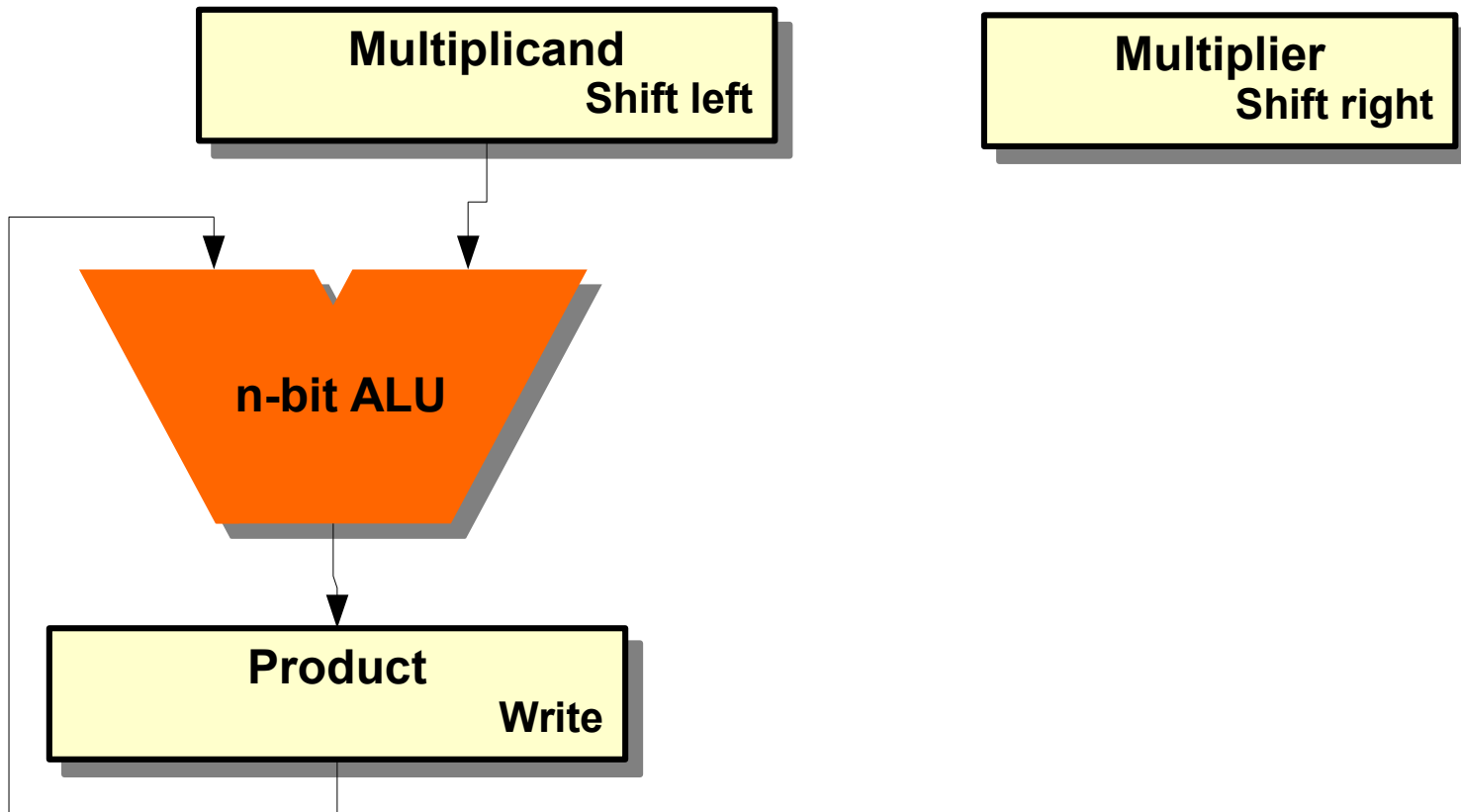


# Multiplication Hardware

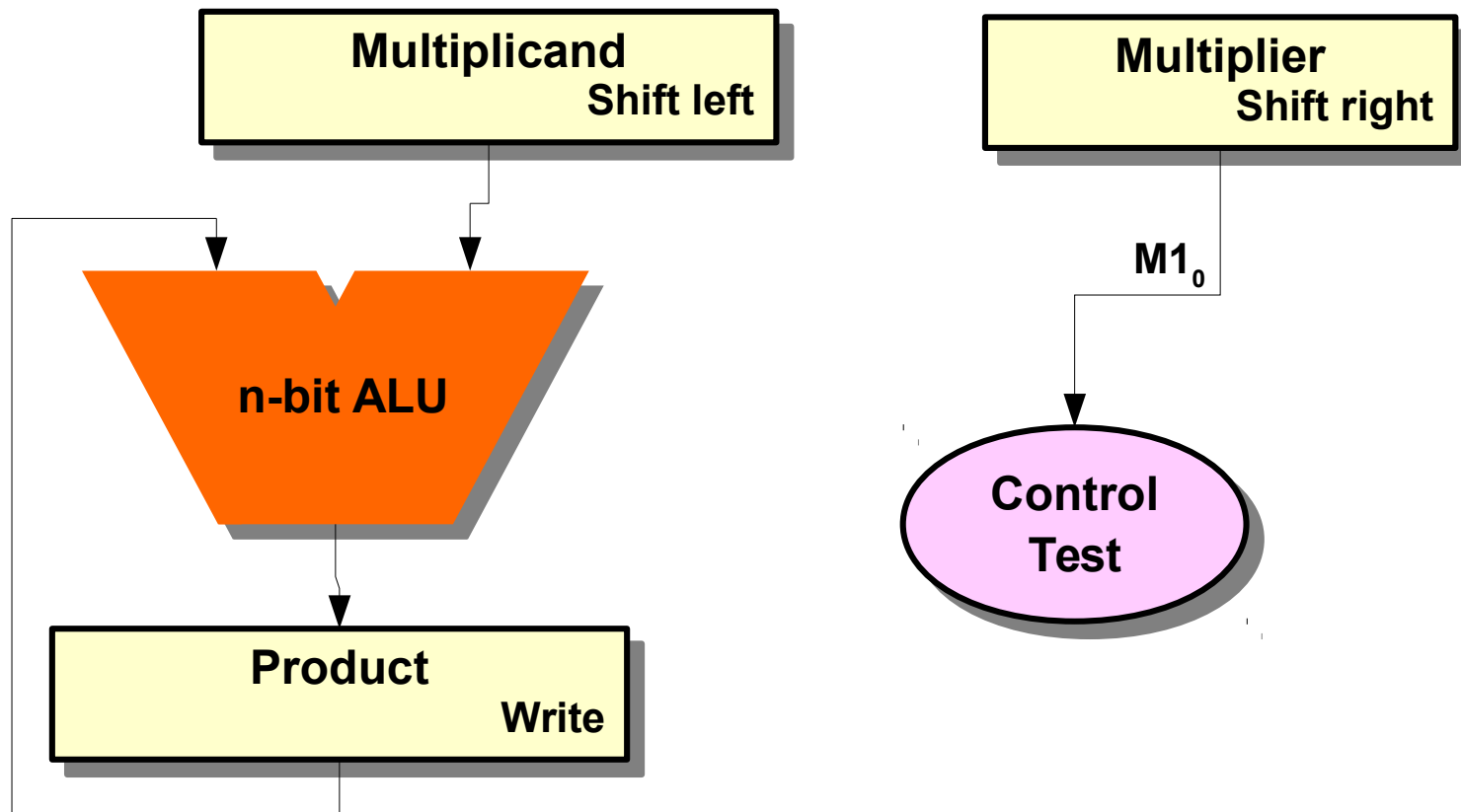



# Multiplication Hardware

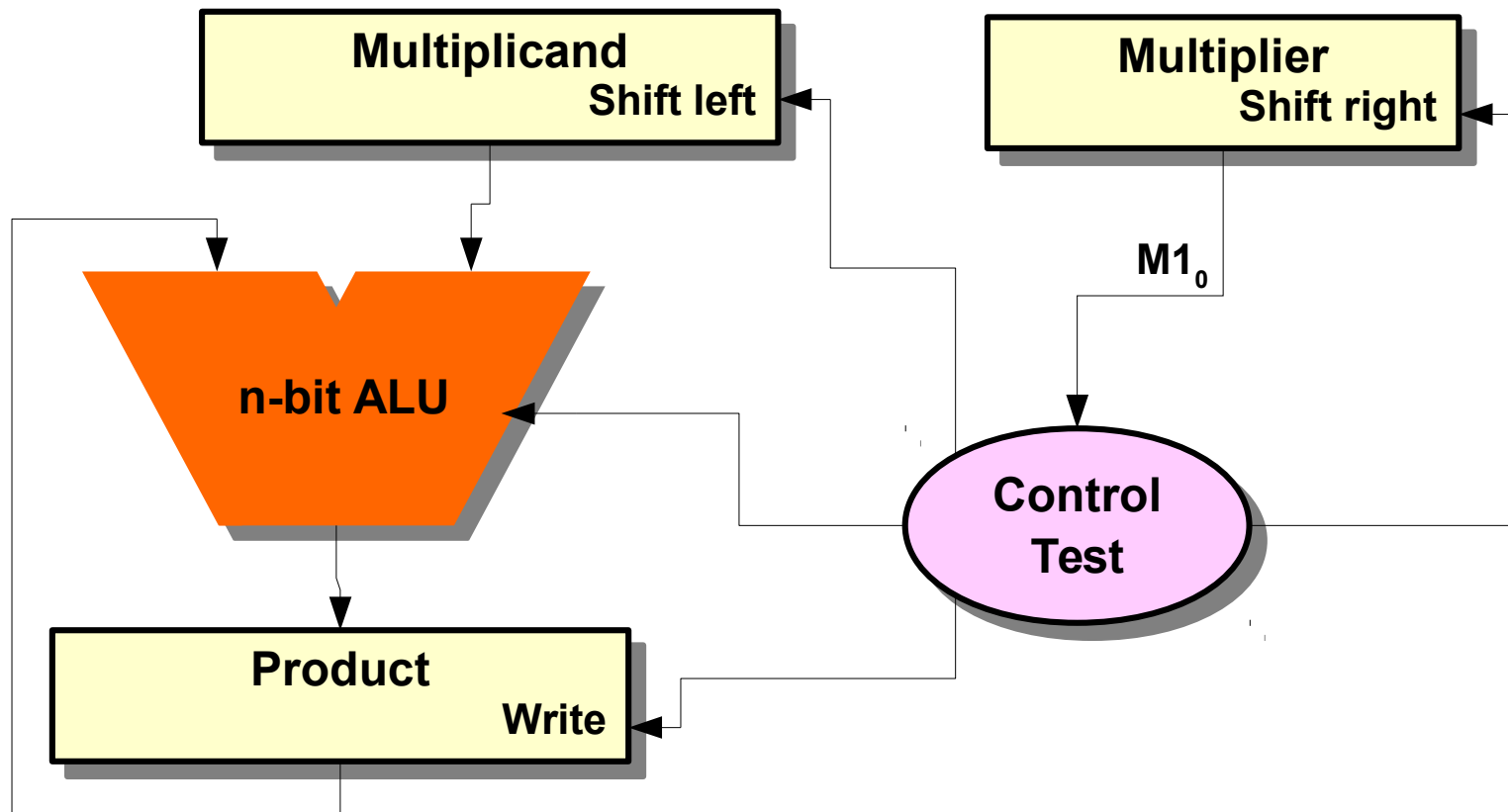

# MIPS Multiplication

- Two 32-bit registers for product
  - HI: most-significant 32 bits
  - LO: least-significant 32-bits

# MIPS Multiplication

- Two 32-bit registers for product
  - HI: most-significant 32 bits
  - LO: least-significant 32-bits
- Instructions
  - `mult rs, rt` / `multu rs, rt`
    - 64-bit product in HI/LO


# MIPS Multiplication

- Two 32-bit registers for product
  - HI: most-significant 32 bits
  - LO: least-significant 32-bits
- Instructions
  - `mult rs, rt` / `multu rs, rt`
    - 64-bit product in HI/LO
  - `mfhi rd` / `mflo rd`
    - Move from HI/LO to rd
    - Can test HI value to see if product overflows 32 bits

# MIPS Multiplication

- Two 32-bit registers for product
  - HI: most-significant 32 bits
  - LO: least-significant 32-bits
- Instructions
  - `mult rs, rt` / `multu rs, rt`
    - 64-bit product in HI/LO
  - `mfhi rd` / `mflo rd`
    - Move from HI/LO to rd
    - Can test HI value to see if product overflows 32 bits
  - `mul rd, rs, rt`
    - Least-significant 32 bits of product → rd

# Division

 


*n*-bit operands yield *n*-bit  
quotient and remainder

# Division


- Check for 0 divisor
- Long division approach
  - If divisor  $\leq$  dividend bits
    - 1 bit in quotient, subtract
  - Otherwise
    - 0 bit in quotient, bring down next dividend bit
- Restoring division
  - Do the subtract, and if remainder goes  $< 0$ , add divisor back
- Signed division
  - Divide using absolute values
  - Adjust sign of quotient and remainder as required

# Division Hardware

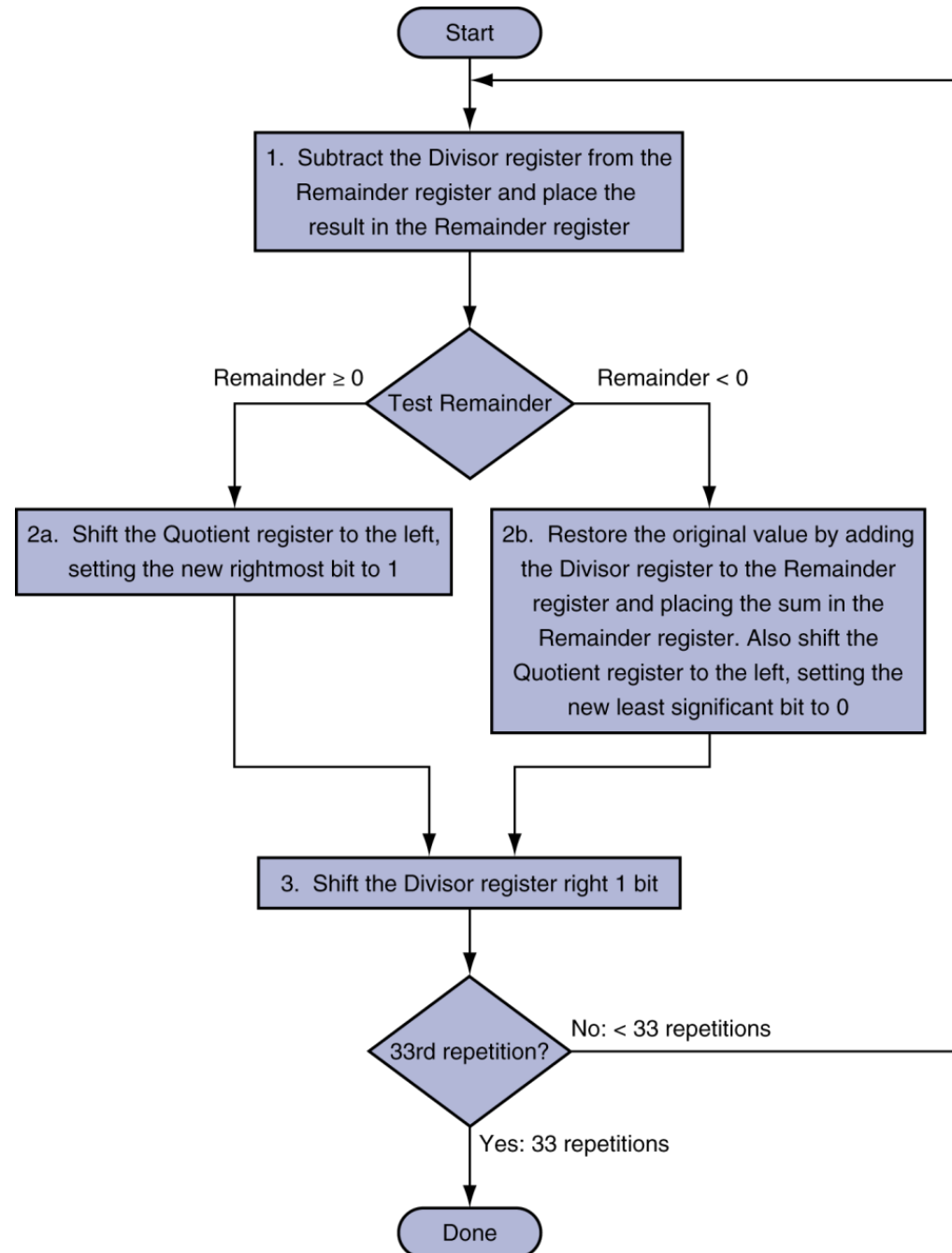



# Division Hardware

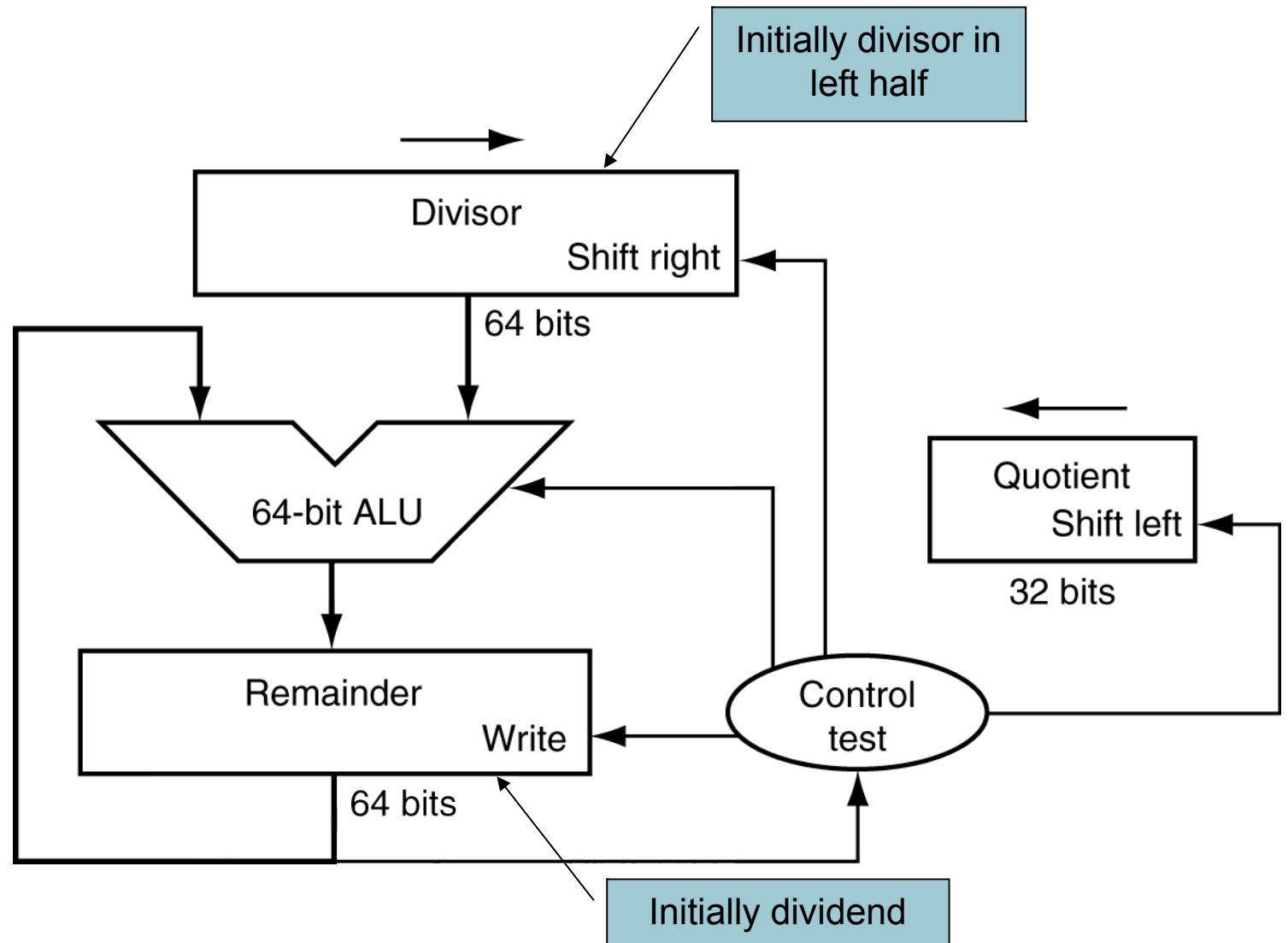

# MIPS Division

- Use HI/LO registers for result
  - HI: 32-bit remainder
  - LO: 32-bit quotient
- Instructions
  - `div rs, rt` / `divu rs, rt`
  - No overflow or divide-by-0 checking
    - Software must perform checks if required
  - Use `mfhi`, `mflo` to access result

# Module Outline

- Integer Arithmetic
  - Adder, Subtractor, Multiplier, Divider
- Arithmetic and Logical Unit Design
  - ALU Design in SystemC

# Extra


# Multiplication

- Start with long-multiplication approach

$$\begin{array}{r} 1000 \\ \times 1001 \\ \hline 0 \quad 1000 \end{array}$$

 
# Multiplication

- Start with long-multiplication approach



 
# Multiplication

- Start with long-multiplication approach


 
# Multiplication


- Start with long-multiplication approach





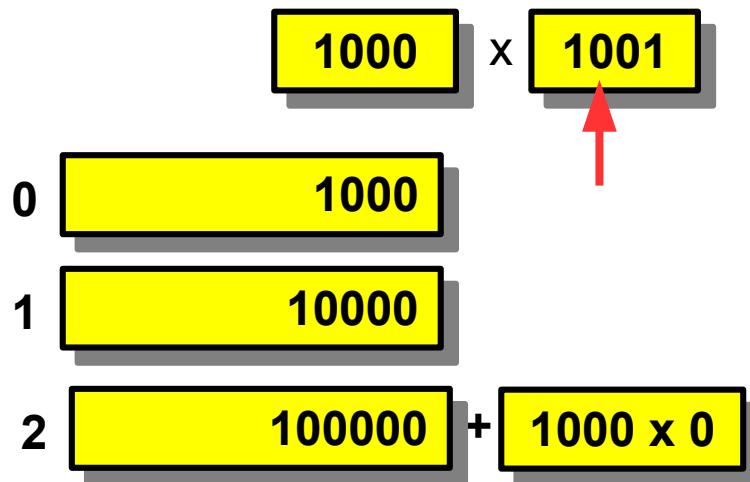
# Multiplication

- Start with long-multiplication approach



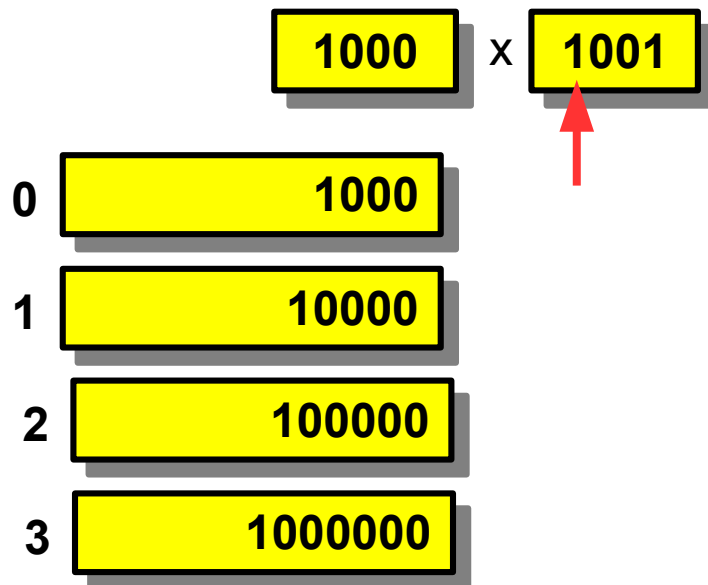
# Multiplication

- Start with long-multiplication approach



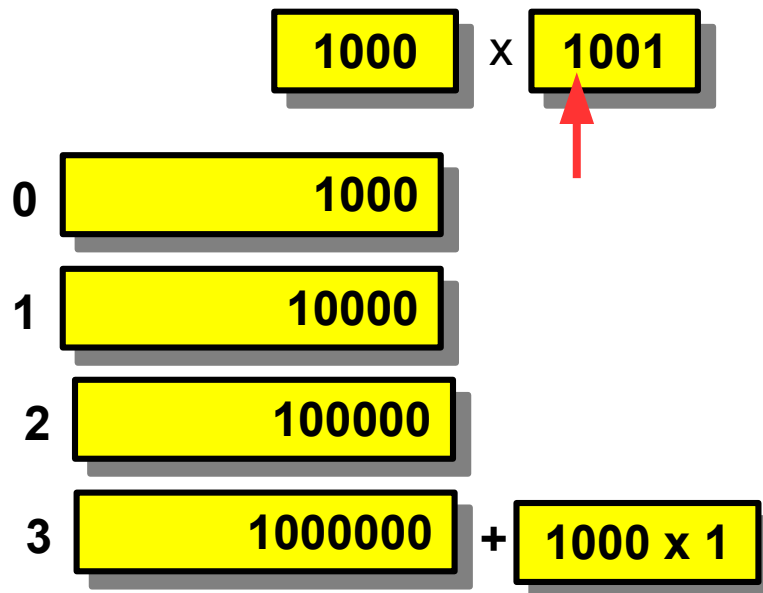
# Multiplication

- Start with long-multiplication approach



 
# Multiplication

- Start with long-multiplication approach



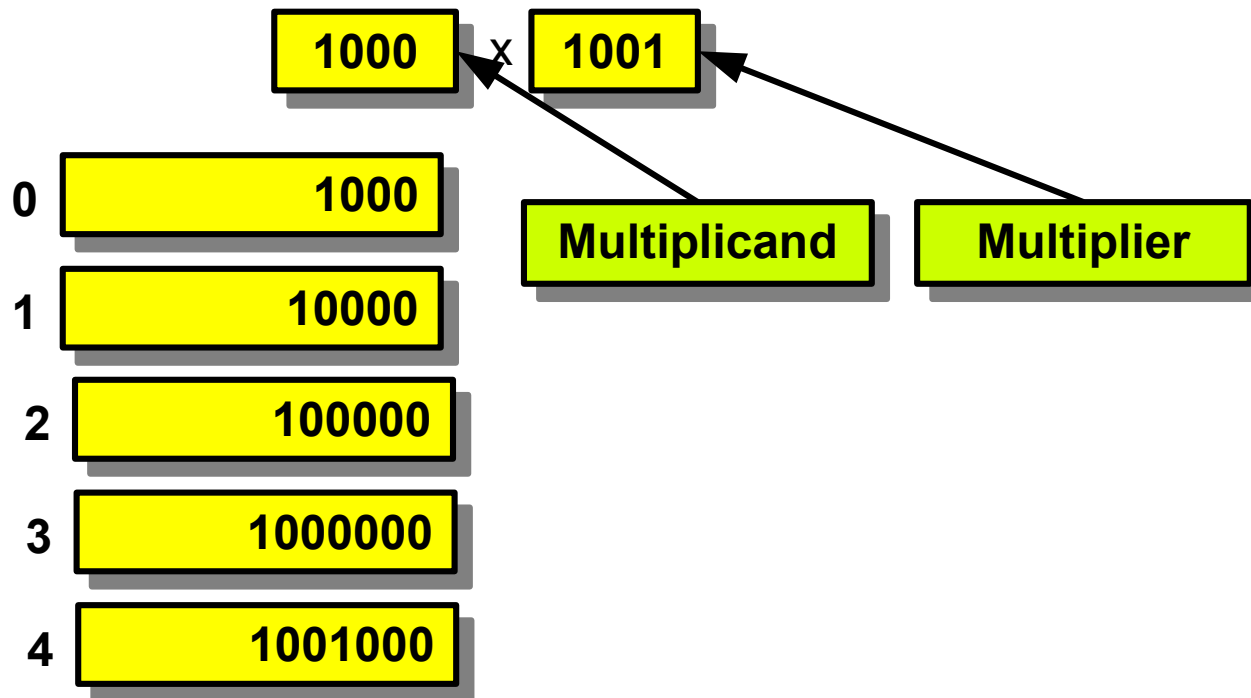
# Multiplication

- Start with long-multiplication approach



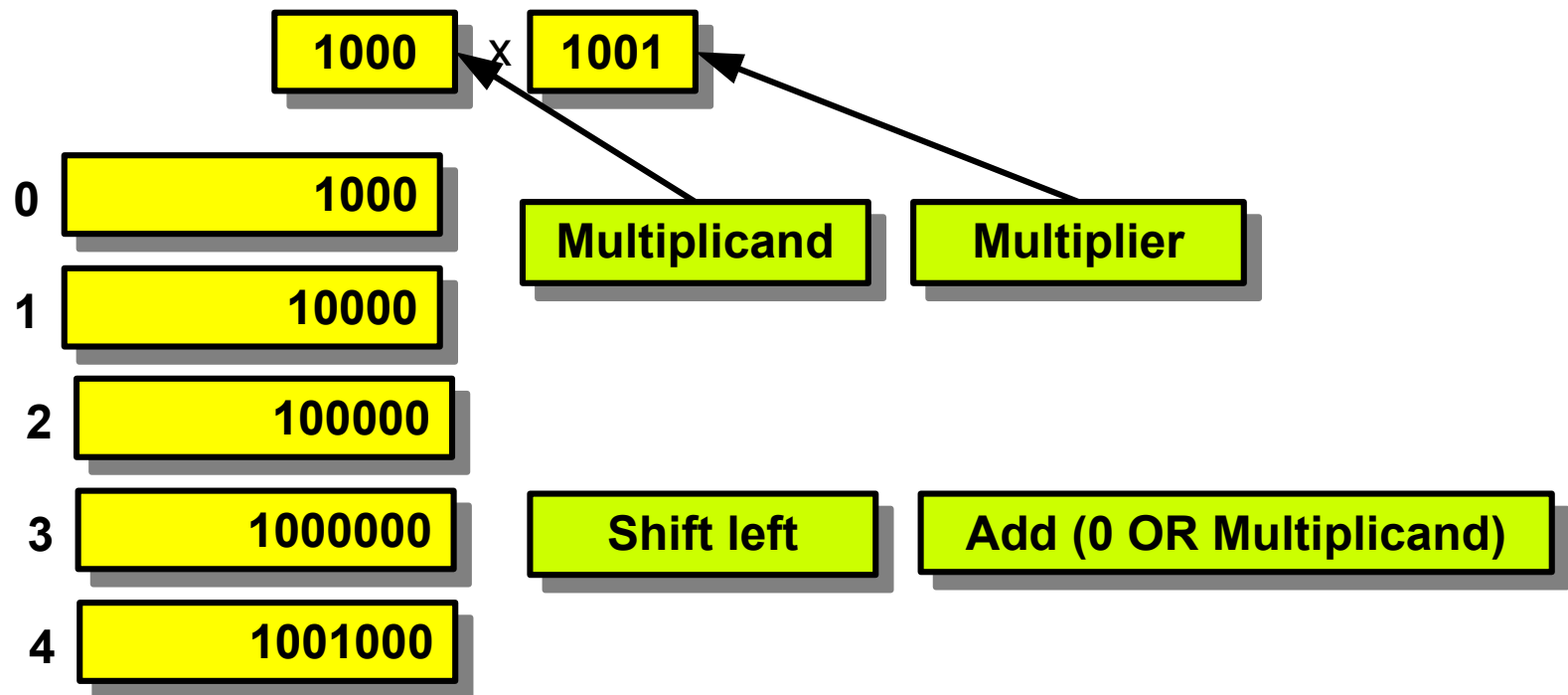
# Multiplication

- Start with long-multiplication approach



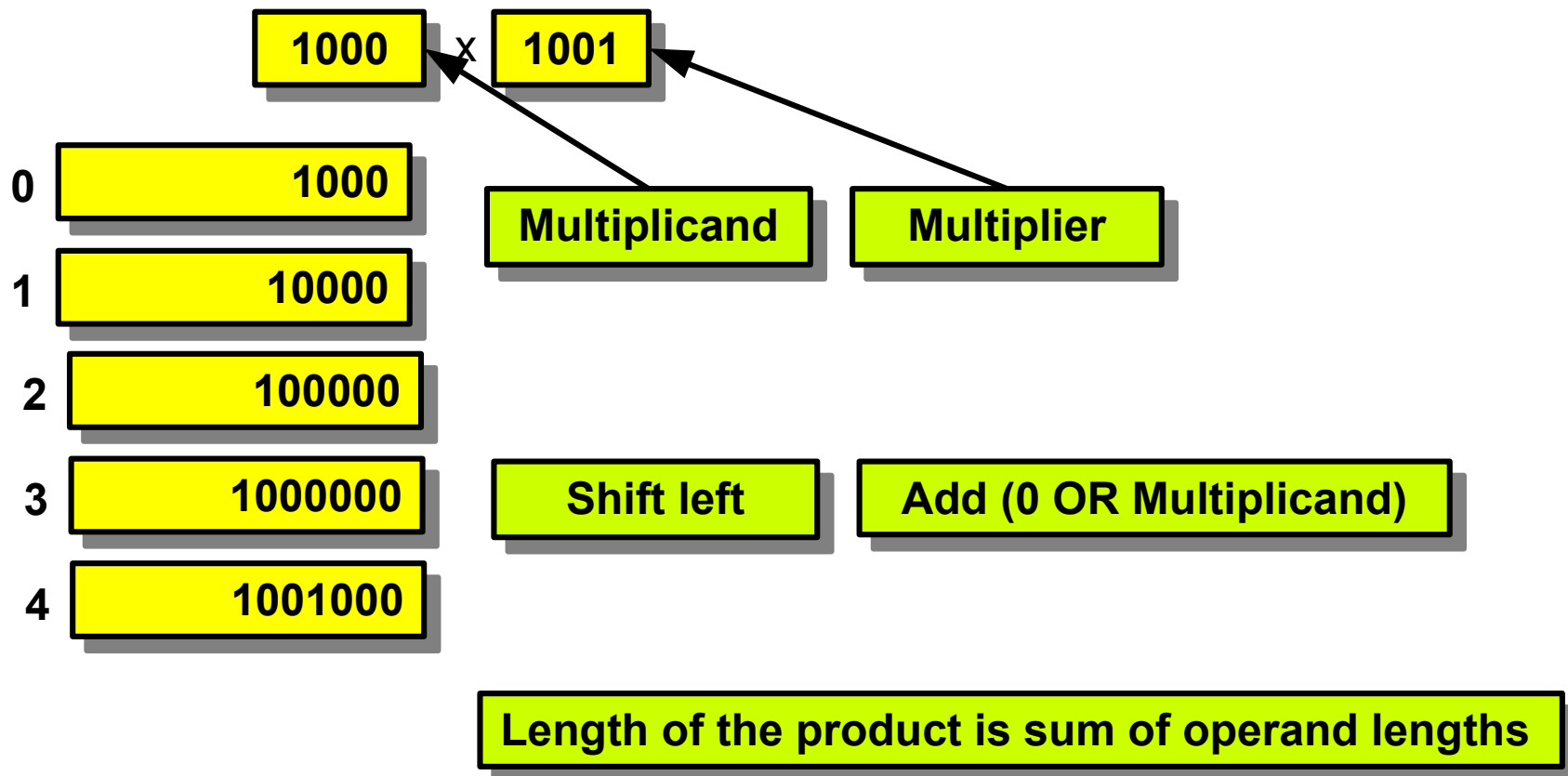
# Multiplication

- Start with long-multiplication approach



# Optimized Multiplication Hardware


- Perform steps in parallel: add/shift

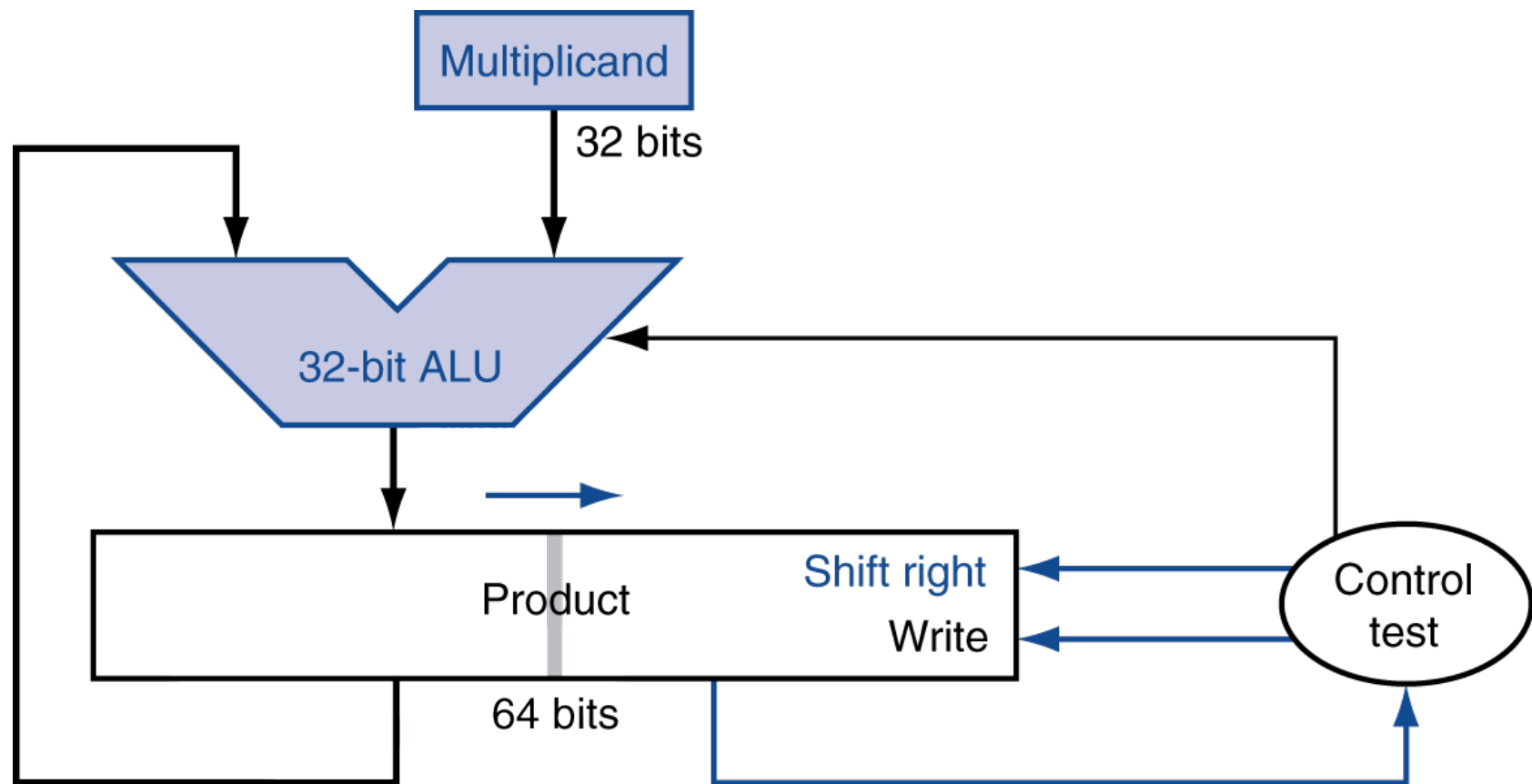




# Fast Multiplication

- Using multiple adders

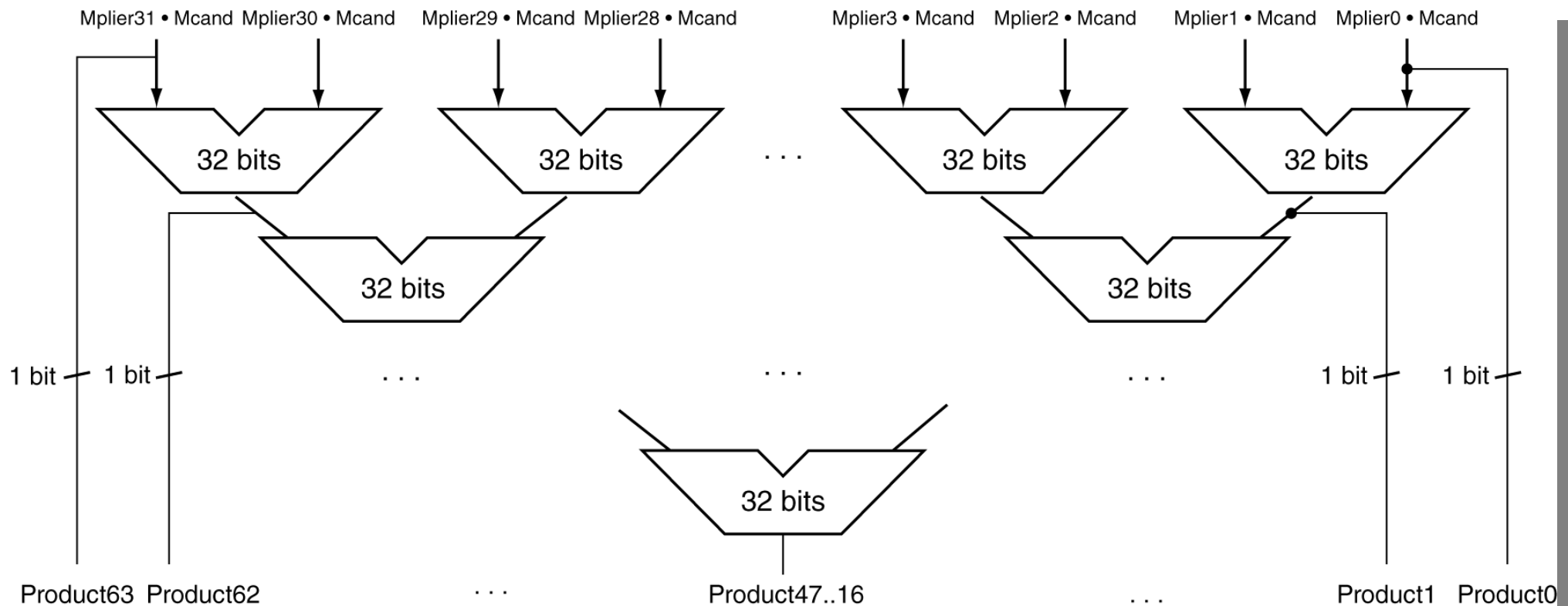

# Optimized Divider

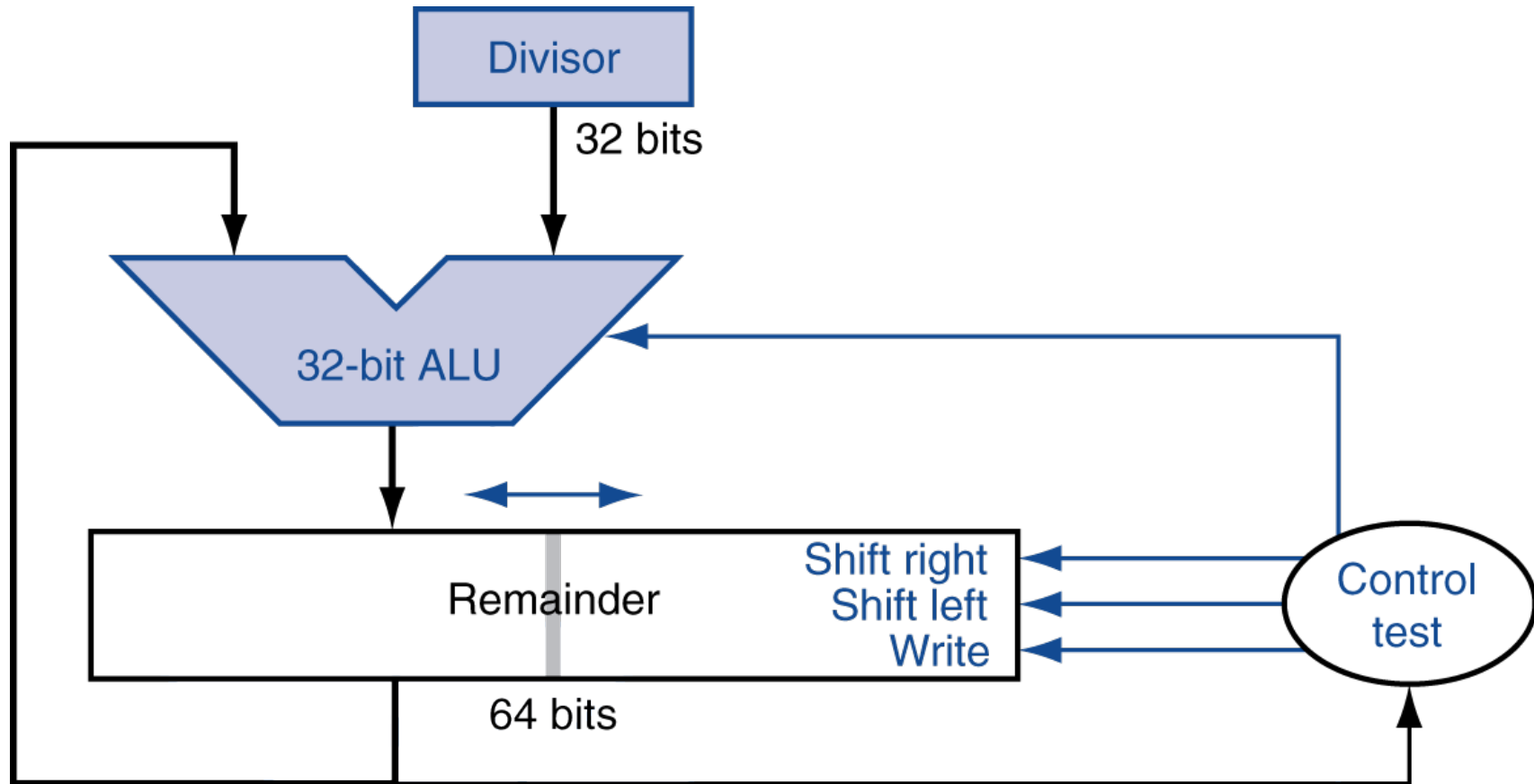

- One cycle per partial-remainder subtraction
- Looks a lot like a multiplier!
  - Same hardware can be used for both

# Faster Division

- Can't use parallel hardware as in multiplier
  - Subtraction is conditional on sign of remainder
- Faster dividers (e.g. SRT division) generate multiple quotient bits per step
  - Still require multiple steps